

Lab experiment: Part3: Opamp circuits

1. Connect the circuits shown in Fig.1. Use $R_1=1k$ and $R_2=10k$.

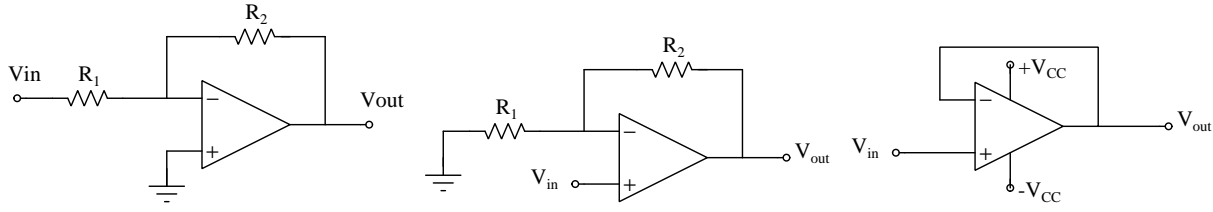


Figure 1: Basic OPAMP circuits

2. Apply input sinusoidal signal of 1Vp-p, 1kHz. Observe the input and output voltage waveform in each case.
3. Comment on these waveforms.
4. Connect the circuit shown in Fig.2.

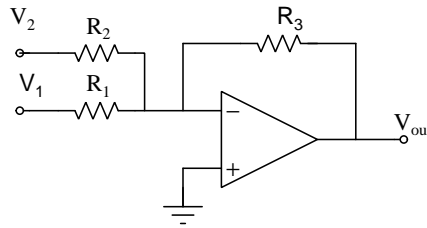


Figure 2: OPAMP adder

5. Use $R_1=R_2=R_3=10k\Omega$.
6. Set $V_1=2V$ DC and $V_2=1V$ DC and measure V_{out} .
7. Now set $V_2 = 1V_{pp}$, 1kHz and observe V_{out} with reference to V_{in} .
8. Connect the circuit shown in Fig. 3.

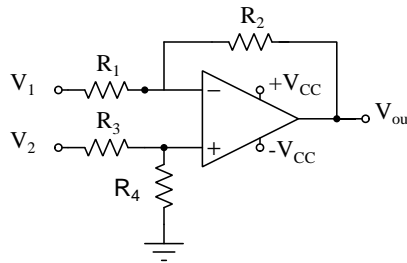


Figure 3: OPAMP subtractor

9. Use $R_1=R_2=R_3=R_4=10k\Omega$.
10. Repeat step 6 and 7 for this circuit.