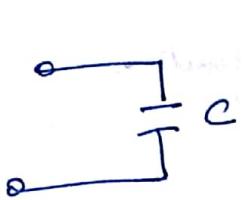


BODEE PLOTS


Transfer function: input \rightarrow output



$$i(t) = \frac{dV(t)}{dt} \quad \text{After taking Laplace trans pos}$$

$$i(s) = CS V(s)$$
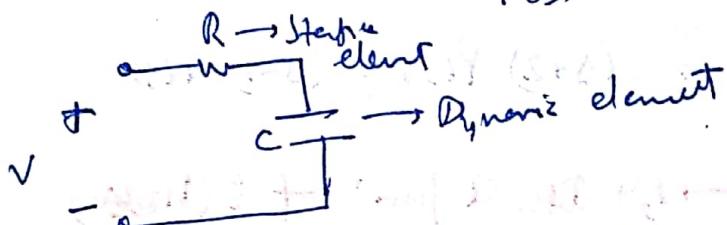
$$\text{Impedance} = \frac{V(s)}{i(s)} = \frac{1}{SC} = Z(s)$$



$$Z(s) = R + \frac{1}{SC} = \frac{V(s)}{i(s)} = \text{Transfer function}$$

$$V_R = iR$$

$$CDVC = iR$$

$$iR + VC = V$$

$$RC \frac{dV_C}{dt} + V_C = V \xrightarrow{\text{Take Laplace trans}}$$

$$\Rightarrow V(s) = (RCs + 1)V_C(s)$$

$$\boxed{\frac{V_C(s)}{V(s)} = \frac{1}{1 + RCs}}$$

$$\boxed{Y(s) = \frac{i(s)}{V(s)} = \frac{SC}{1 + RCs}} \Rightarrow \begin{array}{l} \text{Admittance} \\ \text{Transfer function} \end{array}$$

$$\boxed{V_C(s) = \frac{i(s)}{CS}}$$



$$y(t) = G(s) u(t)$$

output \downarrow
 $\frac{Y(s)}{U(s)} = G(s)$ \Rightarrow Transfer function

Inputs \downarrow

$$\text{if } G(s) = \frac{s-1}{s+2}$$

$$\frac{Y(s)}{U(s)} = \frac{s-1}{s+2} \Rightarrow (s+2) Y(s) = (s-1) U(s)$$

$\dot{y} + 2y = u - u$ $\rightarrow u, y$ are "fun" of t (here)

\rightarrow For linear systems (principle of superposition)
 Time invariance is involved

$$\begin{aligned} u_1 &\rightarrow y_1 \\ u_2 &\rightarrow y_2 \\ u_1 \text{ (delayed)} &\rightarrow y_1 \text{ (delayed)} \end{aligned} \quad \begin{aligned} u_1 + u_2 &\rightarrow y_1 + y_2 \\ k u_1 + l u_2 &\rightarrow k y_1 + l y_2 \end{aligned}$$

Invariance w.r.t time

\rightarrow for linear systems, exponentials are "eigenfunctions".

$$\begin{bmatrix} A \\ \vdots \end{bmatrix} \begin{bmatrix} v \\ \vdots \end{bmatrix} = \begin{bmatrix} w \\ \vdots \end{bmatrix}$$

$$\begin{bmatrix} 2 & 0 \\ 0 & 5 \end{bmatrix} \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$

(2×2) \times (2×1) (2×1)

Scaling of v by a factor of 2

$$e^{at} \rightarrow [G(s)] \rightarrow ce^{at}$$

$\sin \omega$ & \cos are also exponentials

$$\sin \omega = \frac{e^{i\omega} - e^{-i\omega}}{2i} ; \cos \omega = \frac{e^{i\omega} + e^{-i\omega}}{2}$$

$$G(s) = \frac{s-1}{s+3} = \frac{Y(s)}{U(s)}$$

Output
Input

$$\text{Let } U(t) = e^{-8t} \quad \Rightarrow \quad Y(t) = -Ce^{-8t}$$

$$G(s) = \frac{Y(s)}{U(s)} = \frac{s-1}{s+3}$$

$$y + 3y = u - u$$

$$-8Ce^{-8t} + 3Ce^{-8t} = -8e^{-8t} + e^{-8t}$$

$$-5C = 0$$

$$\boxed{C = 0/5}$$

$$\therefore Y(t) = \frac{9}{5} e^{-8t}$$

Ex. Given $U(t)$ find $y(t)$

particular soln

$$Y = \frac{9}{5} e^{-8t} + Ce^{-3t} \quad G(s) = \frac{s-1}{s+3}$$

to algos:

$$\therefore U(t) = e^{at}$$

$$\text{output } y(t) = g(a)e^{at}$$

Assuming

Homogeneous soln


$$g(s) = \frac{n(s)}{d(s)}$$

$$U(t) \rightarrow \boxed{G(s)} \rightarrow y(t)$$

$$\frac{Y(s)}{U(s)} = G(s) = \frac{1}{(s+3)(s+5)}$$

$$\mathcal{L}(s) = 1 \quad \Rightarrow \quad \mathcal{L}^{-1}(1) = s$$


$$Y(s) = \mathcal{L}^{-1}(G(s)U(s))$$

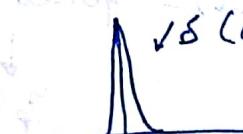

$$\frac{Y(s)}{U(s)} = G(s) = \frac{1}{(s+3)(s+5)} = \frac{a}{s+3} + \frac{b}{s+5} = \frac{a}{s-(-3)} + \frac{b}{s-(-5)}$$

↓ take Laplace inverse (\mathcal{L}^{-1})

$$ae^{-3t} + be^{-5t}$$

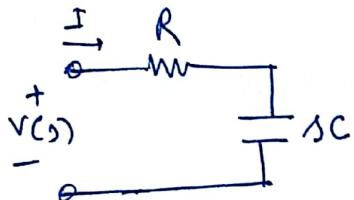


$$\frac{I(s)}{V(s)} = \frac{1/C}{1+RCS} = G(s) =$$

$$\mathcal{L}^{-1}(G(s)) = \mathcal{L}^{-1}\left(\frac{1/C}{1+RCS}\right) = \mathcal{L}^{-1}\left(\frac{1}{RC} \left(\frac{-RCS+1-1}{1+RCS}\right)\right)$$

$$= \mathcal{L}^{-1}\left(\frac{1}{R} + \frac{ae^{-t}}{1+RCS}\right)$$

$$= \frac{1}{R} + ae^{-t/R}$$

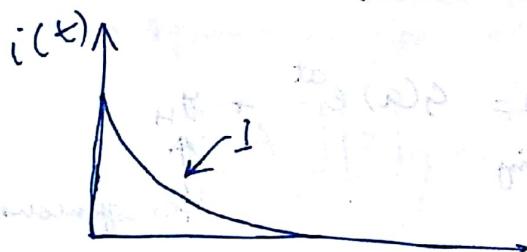

$$\mathcal{L}^{-1}\left(\frac{1}{RC} \left(1 - \frac{1}{1+RCS}\right)\right)$$

$$\mathcal{L}^{-1}\left(\frac{1}{RC} + \frac{1}{RC+RCS}\right)$$

$$u \rightarrow [G(s)] \rightarrow y$$

Output $y(t) = \text{forced response} + \text{natural response}$

$$y_p(t)$$

$$u(t) = e^{5t}$$

$$u(s) = \frac{1}{s-5}$$

$$y(s) = G(s) u(s) = \frac{SC}{(s-5)(1+RCS)}$$

$$* \quad G(T \cdot f) = g(s) = \frac{1}{s + a \cdot 0}$$

$$-e^{-st} \boxed{g(s)} \rightarrow f(t)$$

$$\text{Output} = g(-s) e^{-st}$$

$$* \quad \text{If } G(s) = \frac{1}{s + a}$$

$$e^{-st} \rightarrow \boxed{g(s)} \rightarrow h(t)$$


$$[\text{Output} = t e^{-st}]$$

$$* \quad \text{For } w = \frac{e^{j\omega t} - e^{-j\omega t}}{2j} \rightarrow \text{magnitude} \quad \text{and phase}$$

$$g(s) \Big|_{s=j\omega} = g(j\omega)$$

$$= \frac{e^{j\omega t} - e^{-j\omega t}}{2j} \rightarrow \boxed{G(s)} \rightarrow |G(j\omega)| \text{ in } (wt + \angle G(j\omega))$$


↑ scaling factor ↓ shifted by this angle

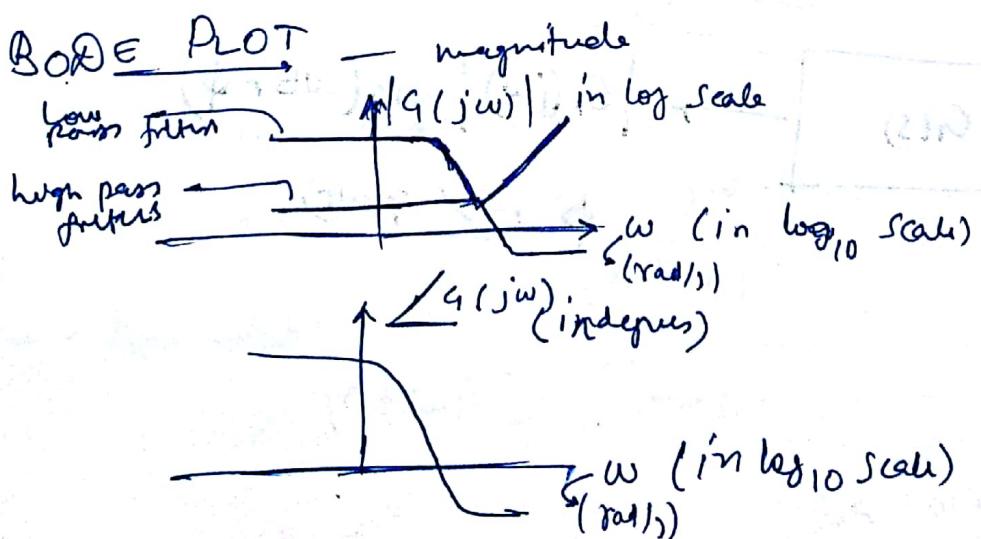

$$G(s) = \frac{1}{s + \alpha}$$


$$= \frac{1}{s - (-\alpha)}$$

Roots of denominator = poles (\times)

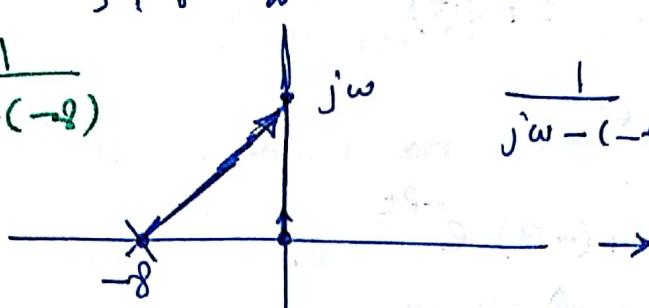

$$\frac{1}{j\omega - (-\alpha)}$$

$|G(j\omega)|$ in log scale

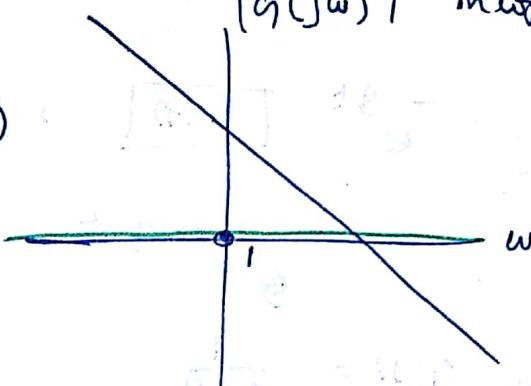


time invariant

linear "Constant Coefficient" (ordinary) differential eqn
(More variables than eq^n)




we take Laplace Transform on b.s.

$$(n(s)) V(s) = (\zeta d(s)) I(s)$$
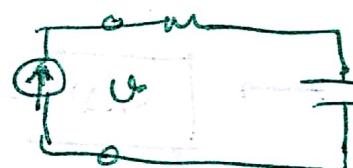
$$\frac{\text{Output}}{\text{Input}} = \frac{V(s)}{I(s)} = \frac{1}{n(s)} \cdot \frac{d(s)}{\zeta}$$




above circuit response

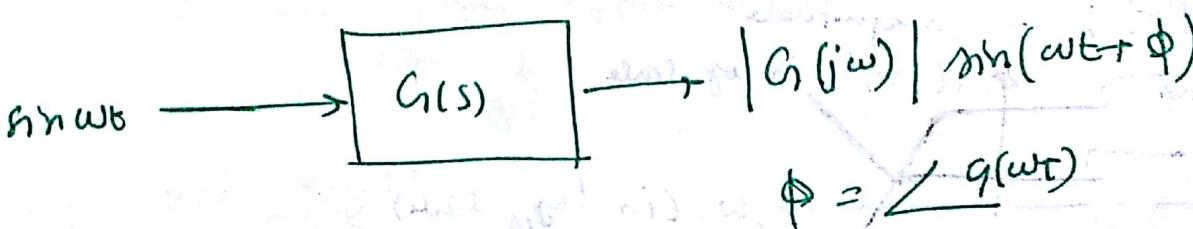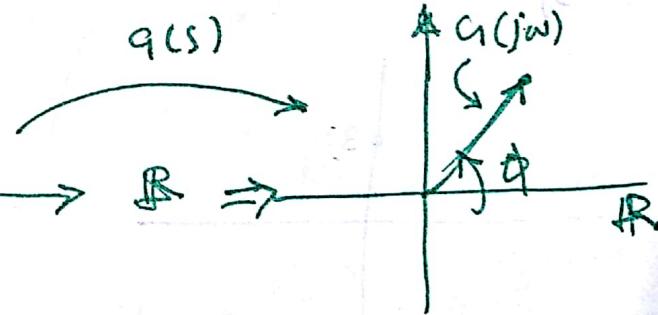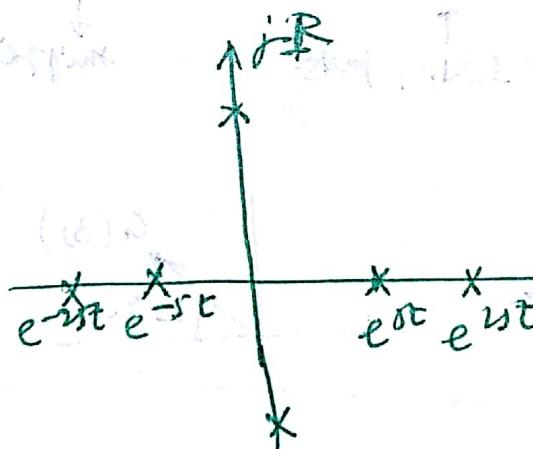


If a function is integrable, Fourier transform is defined

$$\int_{-\infty}^{\infty} |f(t)| dt < \infty$$

BODE magnitude plot

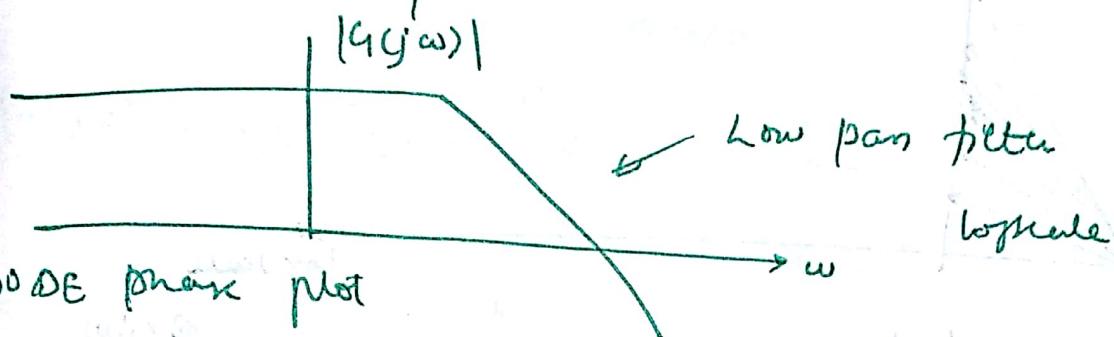

BODE phase plot

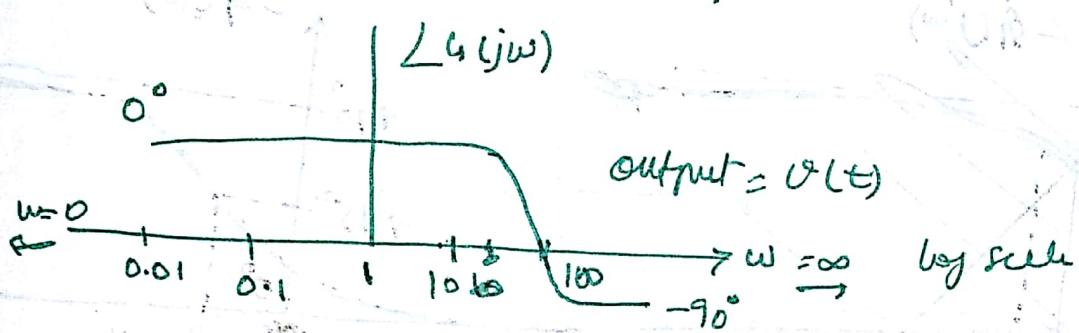


$$G(s) = \frac{(s+3)(s+8)}{(s+9)(s+6)(s+\overline{8})}$$

$$\begin{aligned} \log|G(j\omega)| &= \log|j\omega+3| + \log|j\omega+8| \\ &\quad - \log|j\omega+9| - \log|j\omega+6| - \log|j\omega+\overline{8}| \end{aligned}$$

$$\begin{aligned} \angle G(j\omega) &= \angle(j\omega+3) + \angle(j\omega+8) - \angle(j\omega+9) - \angle(j\omega+6) \\ &\quad - \angle(j\omega+\overline{8}) \end{aligned}$$

$$\rightarrow G(s) = s+8$$
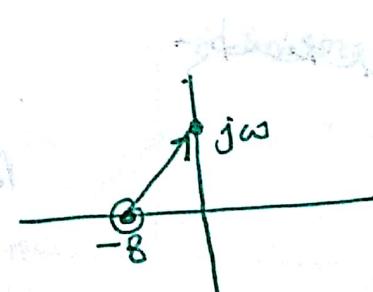
$$G(j\omega) = j\omega+8 = j\omega-(-8)$$




\rightarrow Asymptotic plot





$$|G(j\omega)| = \sqrt{\omega^2 + 64}$$

for $\omega \ll 8$ for $\omega \gg 8$

$$|G(j\omega)| \approx 8 \quad |G(j\omega)| \approx \omega$$

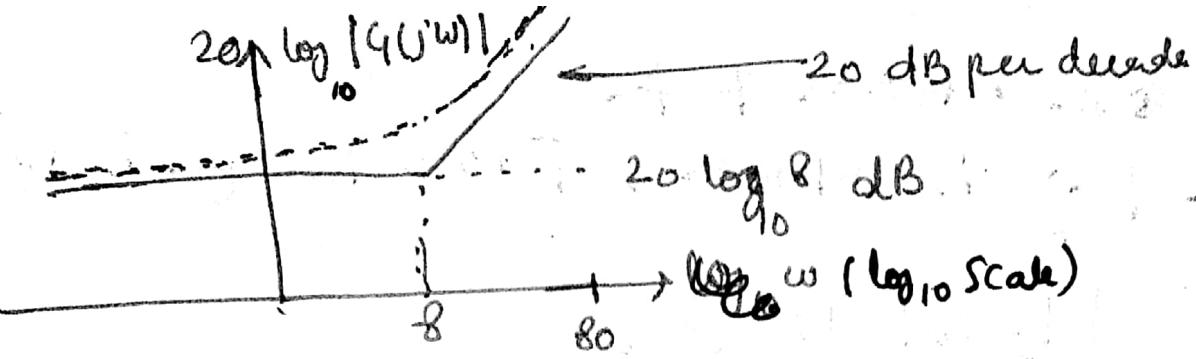


$j\omega$ ↑ higher ω

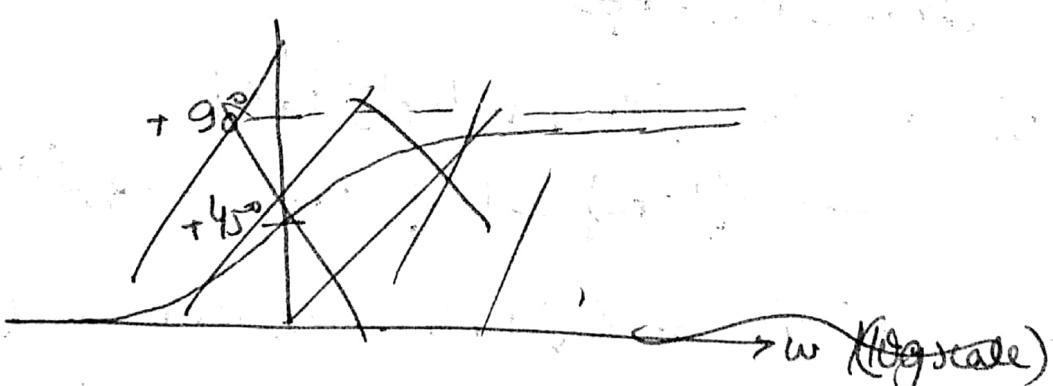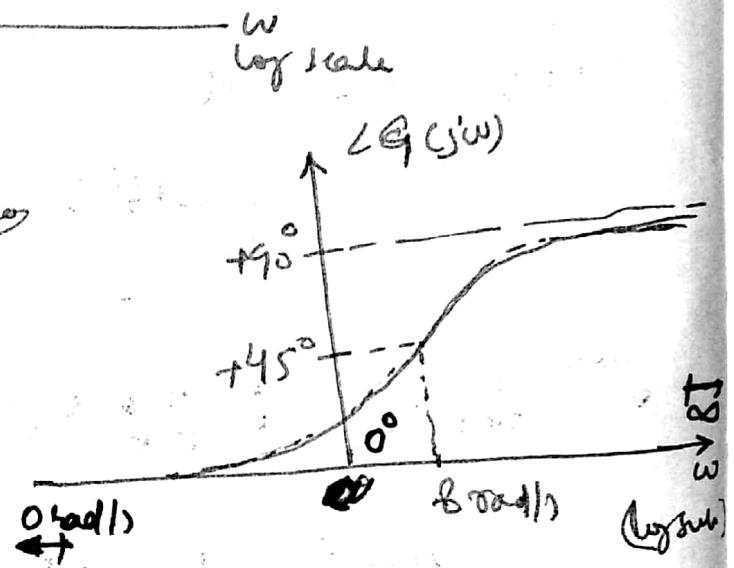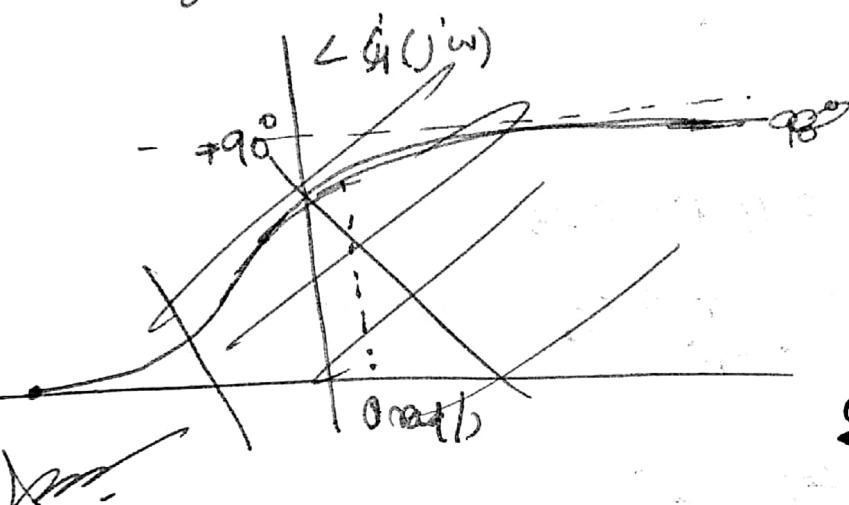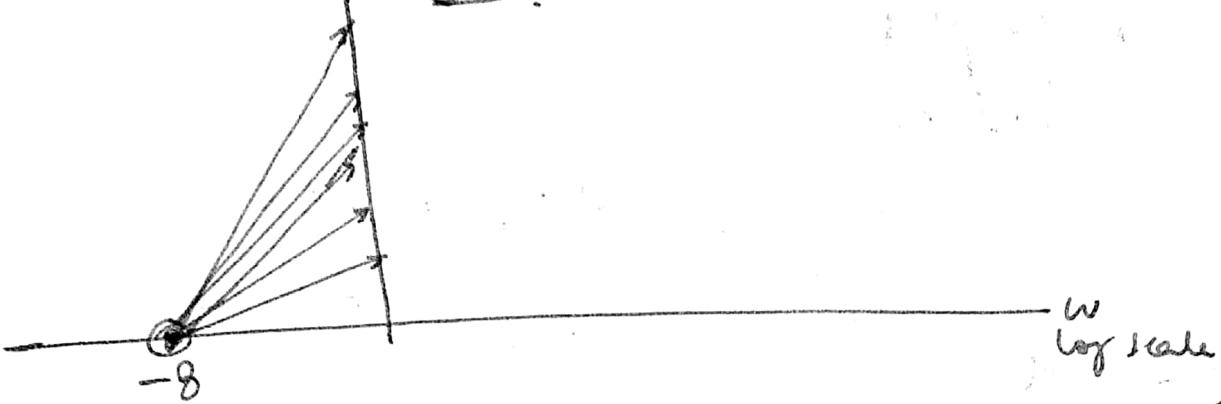



Approximation

Bode magnitude \rightarrow asymptotic approx

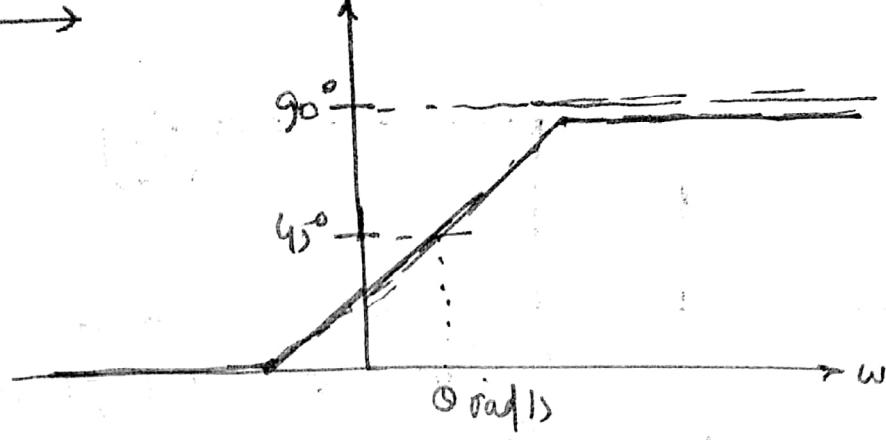Bode phase plot \rightarrow asymptotic approx




$$|G(j\omega)| = \sqrt{\omega^2 + 64} = \begin{cases} 8 & ; \omega \ll 8 \\ \omega & ; \omega \gg 8 \end{cases}$$

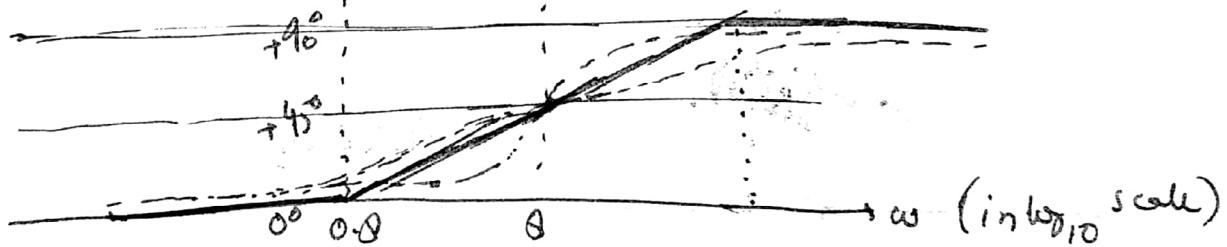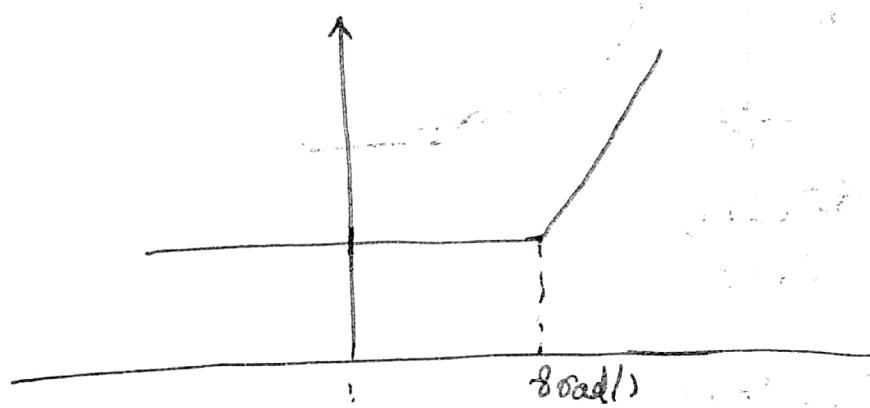


$$G(s) = \frac{30}{s+12}$$
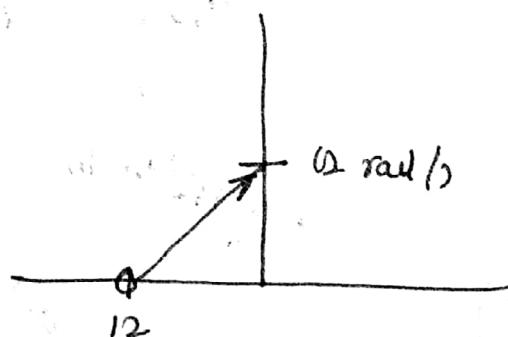
$$G(j\omega) = \frac{30}{j\omega + (-12)}$$





$$|G(j\omega)| = \frac{30}{\sqrt{\omega^2 + (12)^2}} = \begin{cases} \frac{30}{12} & ; \omega \ll 12 \\ \frac{30}{\omega} & ; \omega \gg 12 \end{cases}$$

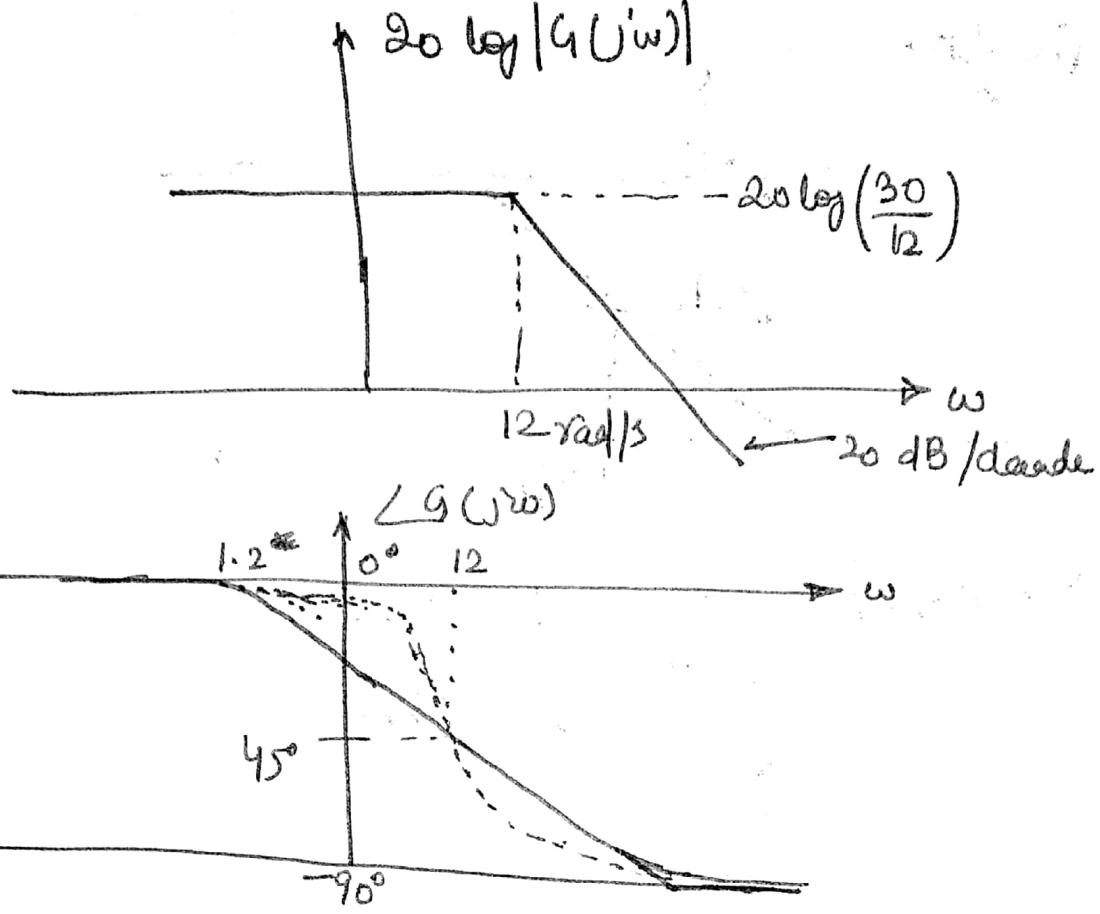


$$\text{Ex. } G(s) = \frac{45(\delta+1)}{s+20}$$
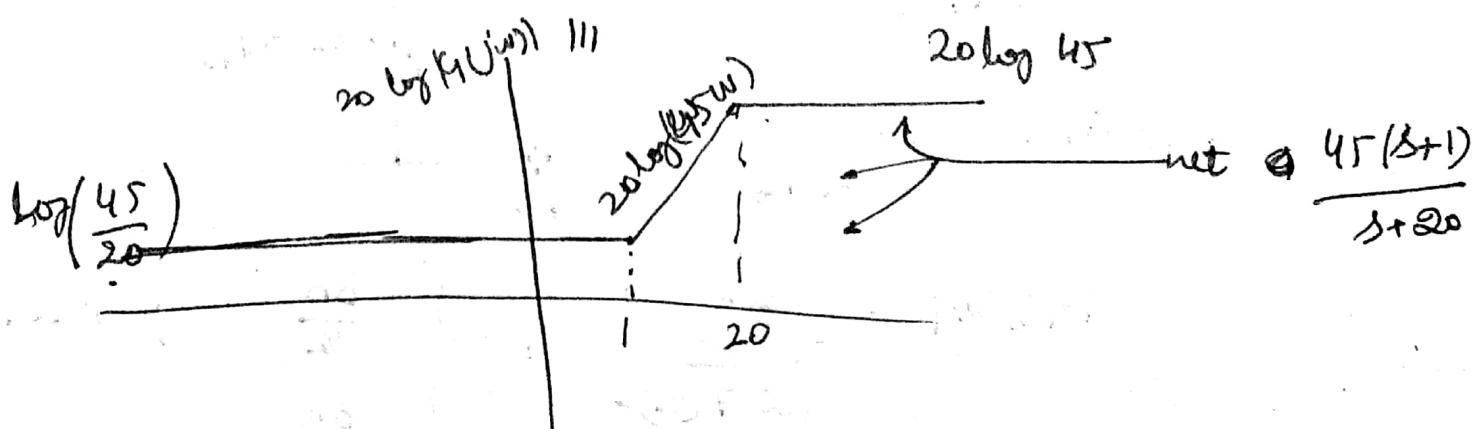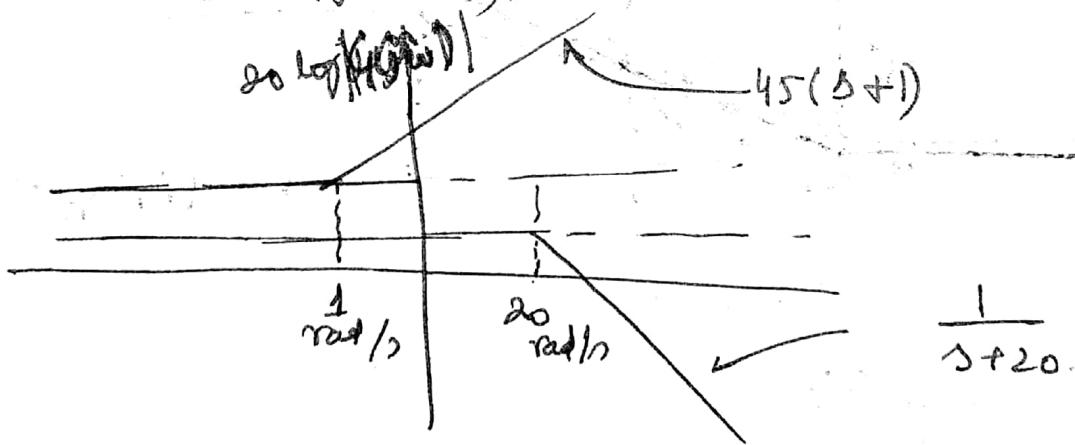
$$G(j\omega) = \frac{45(j\omega + 1)}{(j\omega + 20)}$$



2-12-23 Project

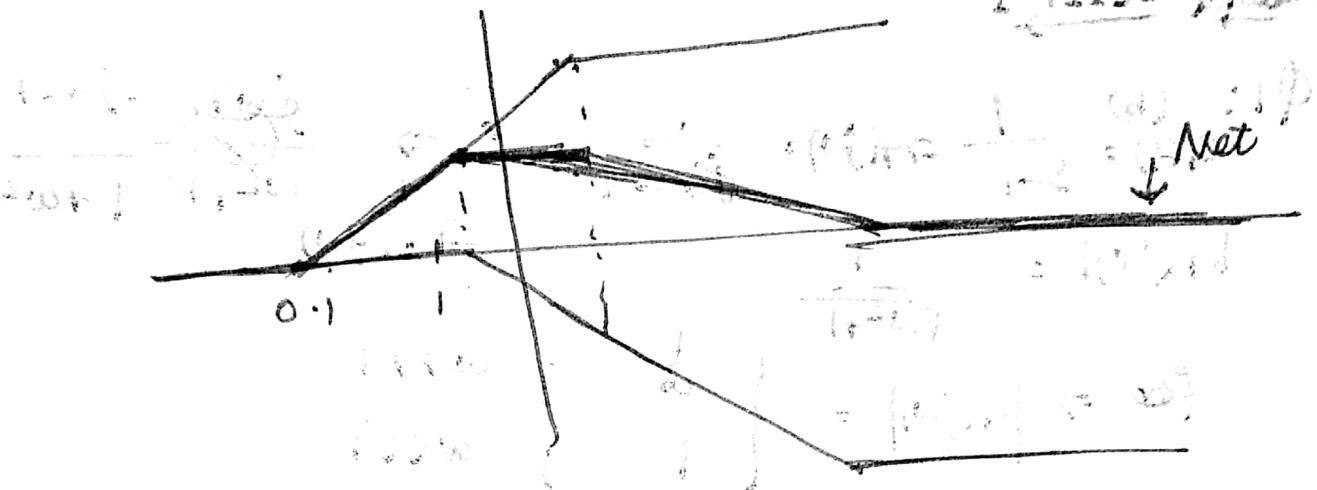


Ex. $G(s) = S$

$$G(j\omega) = j\omega$$

$$|G(j\omega)| = \omega$$

~~20 log~~ 20

$$20 \log_{10} |G(j\omega)| = 20 \log_{10} \omega$$

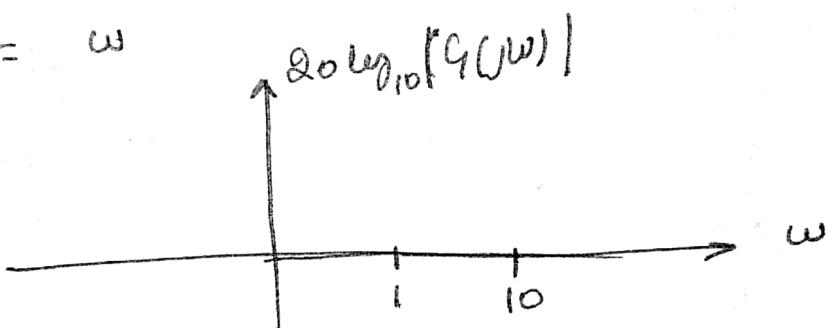


~~Ex~~ $G(s) = s^2 + 2s$



$$|2s - \omega^2| \approx 2s ; \quad \omega < \omega_r$$

$$|2s - \omega^2| \approx \omega^2 ; \quad \omega > \omega_r$$

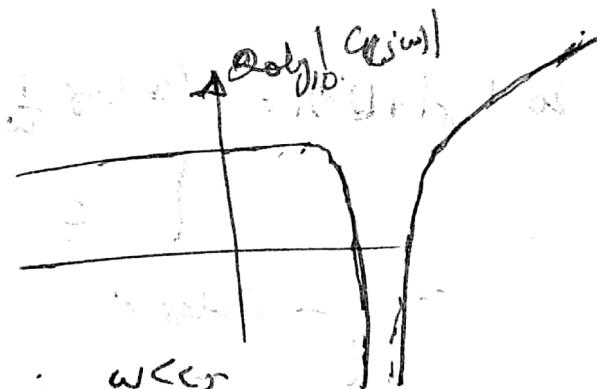


→ Chapter 7 → V.V

LAPLACE TRANSFORM

$$\mathcal{L}[f(t)] = F(s) = \int_0^\infty f(t) e^{-st} dt$$

Ex1
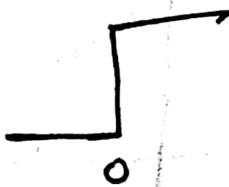
$$u(t) = \begin{cases} 0 & \text{if } t < 0 \\ 1 & \text{if } t \geq 0 \end{cases}$$



$$\mathcal{L}[u(t)] = \int_0^\infty 1 e^{-st} dt$$

$$= \int_0^\infty e^{-st} dt = \left[\frac{1}{-s} e^{-st} \right]_0^\infty$$

$$\boxed{\mathcal{L}[u(t)] = \frac{1}{s}}$$

$$\rightarrow \text{Ex 2, } f(t) = e^{at} \quad t \in [0, \infty) \quad (a > 0)$$




$$\mathcal{L}[f(t)] = \int_0^\infty e^{at} e^{-st} dt = \int_0^\infty e^{(a-s)t} dt$$

$$= \frac{1}{a-s} e^{(a-s)t} \Big|_0^\infty = \frac{1}{s-a} \quad s > a$$

$$* j^2 = -1 *$$

$$e^{(a+jb)t} \quad a, b \in \mathbb{R}$$

$$e^{jbt}$$

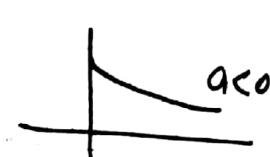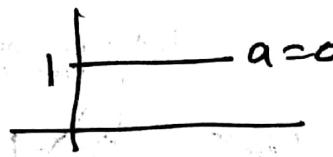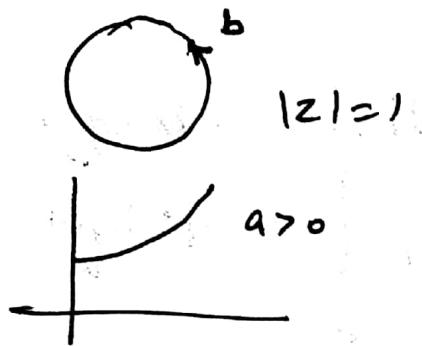


$$(a+jb)t = a \cdot \cos bt + j \sin bt$$

$$|e^{jbt}| = 1 = |\cos bt + j \sin bt| = \sqrt{x^2 + y^2}$$

$$e^{at+jbt} = e^{at} e^{jbt}$$

$$= e^{at} (\cos bt + j \sin bt)$$

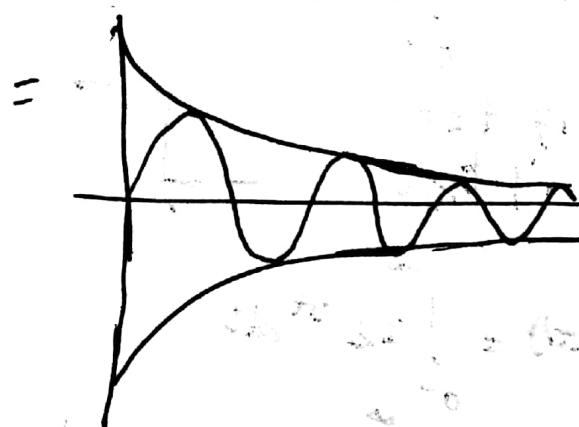

$$\xrightarrow{\text{Inverse Laplace transform}} \int_{\sigma_1 - j\infty}^{\sigma_1 + j\infty} F(s) e^{st} ds$$

Theorems for Laplace Transform

$$① \mathcal{L}[af_1 + bf_2] = aF_1(s) + bF_2(s)$$

$$② \mathcal{L}[\cos wt] = \mathcal{L}\left[\frac{e^{jw\tau} + e^{-jw\tau}}{2}\right] = \frac{s}{s^2 + w^2}$$

$$③ \mathcal{L}[\sin wt] = \frac{w}{s^2 + w^2}$$

$$\begin{aligned} ④ \mathcal{L}\left[\frac{df(t)}{dt}\right] &= \int_{0^-}^{\infty} \frac{df(t)}{dt} e^{-st} dt \\ &= \int_{0^-}^{\infty} df(t) e^{-st} = e^{-st} f(t) \Big|_{0^-}^{\infty} \\ &\quad + s \int_{0^-}^{\infty} f(t) e^{-st} dt \\ &= sF(s) - f(0^-) \end{aligned}$$

$$⑤ \mathcal{L}[\delta(t)] = \mathcal{L}\left[\frac{du(t)}{dt}\right] = 1$$

Laplace transform of δ function is 1

$$\begin{aligned} ⑥ \mathcal{L}\left[\int_0^t f(z) dz\right] &= \frac{-e^{-st}}{s} \int_{0^-}^{\infty} f(z) dz - \frac{1}{s} \int_0^{\infty} f(t) e^{-st} dt \\ &= \frac{F(s)}{s} \end{aligned}$$

$$(H) \quad L^{-1}\left[\frac{1}{s-a}\right] = e^{at}$$

$$\frac{P(s)}{Q(s)} \quad \text{assuming } \deg(Q(s)) > \deg(P(s))$$

$$\frac{P(s)}{Q(s)} = \sum_i \frac{c_i}{s-a_i}$$


$$\text{where } a_i(s) = \prod_{j \neq i} (s-a_j)$$

$$c_j = \frac{p(a_j)}{\prod_{i \neq j} (a_j - a_i)}$$

$$L^{-1}(F(s)) = \frac{1}{2\pi j} \int_{\sigma_1-j\infty}^{\sigma_1+j\infty} F(s) e^{st} ds$$

$$L^{-1}(L[f(t)]) = f(t)$$

Example Chap 7, 8

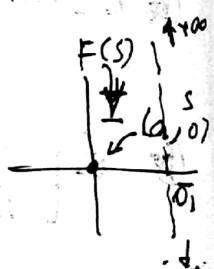


Thevenin / Norton Theorems :-

$$\begin{aligned} \uparrow i(0^-) & \left\{ \begin{array}{l} \rightarrow i(t) \\ v(t) \end{array} \right. \\ & + \end{aligned} \quad v(t) = L \frac{di(t)}{dt}$$

To solve, need $i(0^-)$

The transform circuit

$$V(s) = L(sI(s) - i(0^-))$$

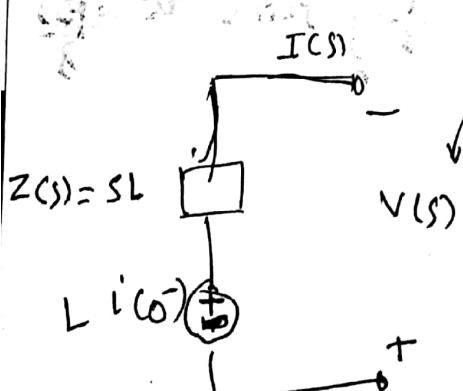

Transform circuit

$$\begin{aligned} i(t) &= \frac{1}{L} \int_{-\infty}^t v(z) dz \\ i(t) &= \frac{1}{L} \int_0^t v(z) dz + i(0^-) \\ i(s) &= \frac{V(s)}{sL} + \frac{i(0^-)}{s} \end{aligned}$$


If $v(t) = V_0$

$$I(s) = \frac{V_0}{s^2 L} + \frac{i(0^-)}{s}$$


$$= \frac{V_0 + i(0^-)sL}{s^2 L}$$

$$i(t) = i(0^-) + \frac{V_0}{L} L^{-1} \frac{1}{s^2} = i(0) + \frac{V_0}{L}$$

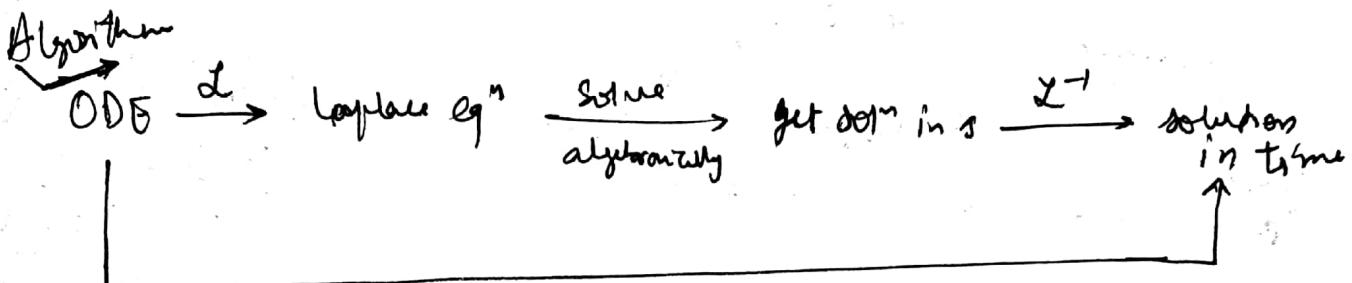
$$\int_{0^-}^{\infty} t e^{-st} dt \Rightarrow i(t) = i(0^-) + \frac{V_0 t}{L}$$



If g had solved an ODE

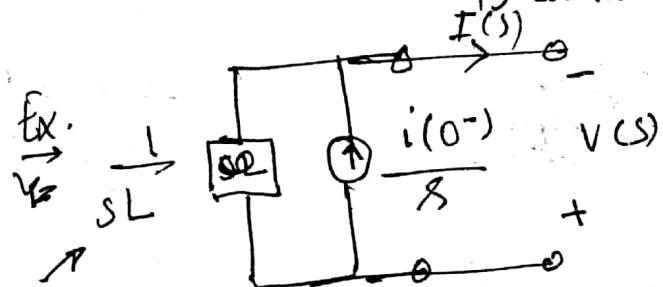

admittance

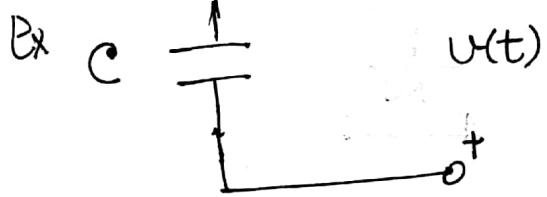



$$i(s) = \frac{1}{sL} (V(s) + L i(0^-))$$

$$i(t) = C \frac{dV}{dt}$$


$$I(s) = C (sV(s) - V(0^-))$$

$$\frac{I(s)}{Cs} = V(s) - \frac{V(0^-)}{s}$$
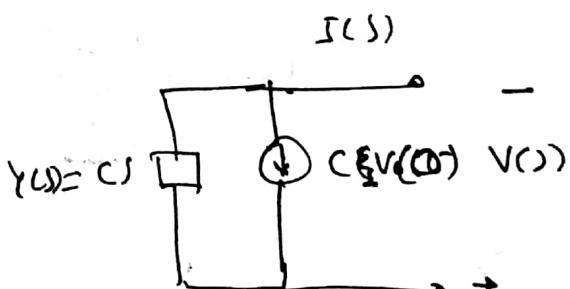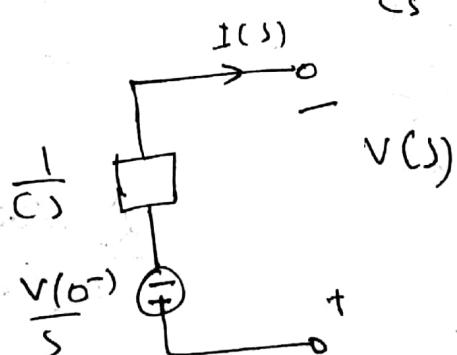
$$V(s) = \frac{C}{s} \frac{I(s)}{Cs} + \frac{V(0^-)}{s}$$



~~Ex~~ Voltage Controlled Voltage Source

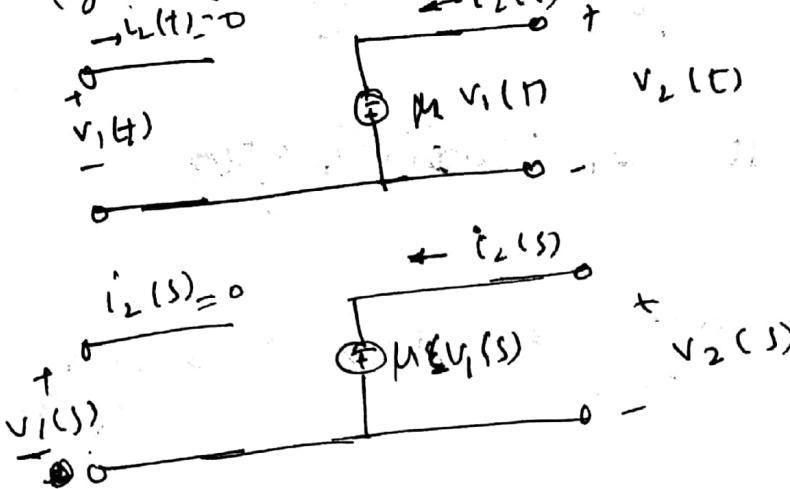

~~V~~

$$V \in i(t) R + \frac{1}{j\omega} \rightarrow j\omega$$


$$\cancel{V(v_1 s t) i(t) R - \cancel{i(t) s t}}$$

$$V_{0L} \boxed{V = i(z)}$$

$$(i) = \frac{V}{Z}$$

$$\therefore V_C = \Sigma C_i$$

$$V_C = \frac{V}{\Sigma Z_C}$$

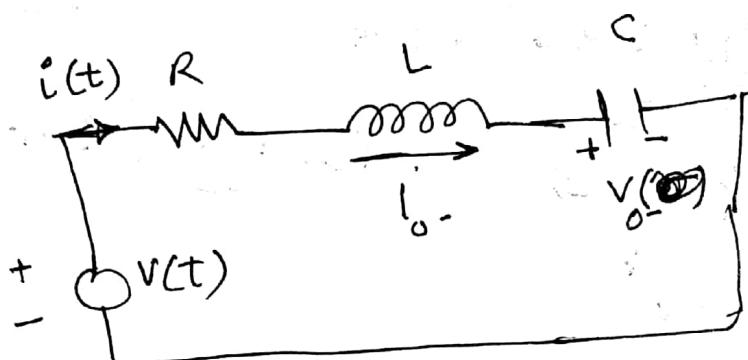


$$KVL: v(t) = R i(t) + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t) dt + V_0$$

$$\Sigma(\lambda) = R$$

$$\Sigma(j) = jL$$

$$\frac{1}{jC}$$

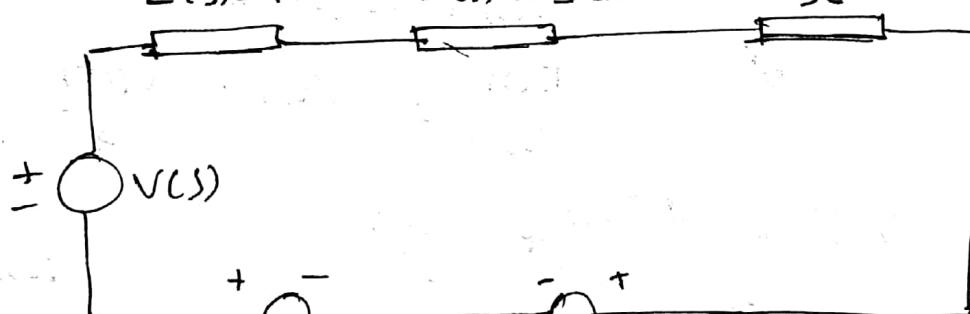


$$L i_a$$

$$\frac{V_0}{s}$$

$$\frac{\mathcal{L}[v(t)]}{\mathcal{L}[i(t)]} = \Sigma(s)$$



III

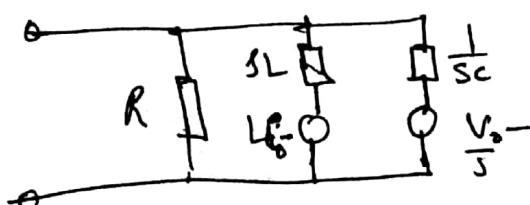



Thevenin / Norton Theorem

v.v Ch 9




2nd condition: dependent source added



Cut A should be consisting of only linear circuit sources (Independent & controlled sources are possible). 3rd condition: across capacitor & inductor are possible.

No coupling (magnetic by controlled sources).

②

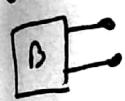


Cut B := NO coupling

Thevenin's Theorem: Under conditions ① & ②
Circuit A is equivalent to ~~three~~ external impedance Z_{Th}
by a transform voltage (V_{Th}) s.t. cut A is ~~is~~ equivalent to cut C.

Norton's Theorem:

$$I(S) = \frac{V_{Th}(S)}{Z_{Th}(S)}$$

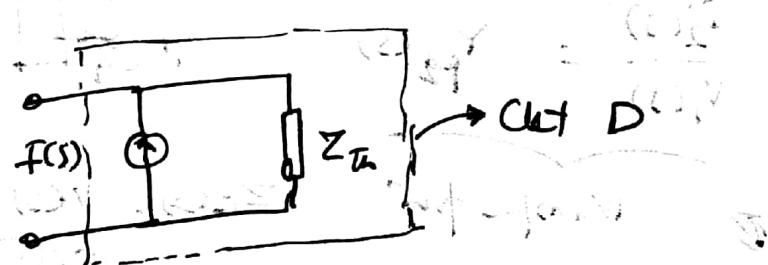

Under cond. ① & ② $\exists Z_{Th}(S)$, $I_{Th}(S) \propto S^T$
cut D is equivalent to cut A.

Theorem Norton \Leftrightarrow Thevenin

$$y(t) = A_{ext} i(t)$$

I_2 number of A = $n(\text{edges}) - n(\text{nodes}) + 1$ = no. of nodes pairs

$$R, L, C = \int R, \frac{d}{dt}, \int \rightarrow A \text{ is symmetric}$$

Controlled sources \Rightarrow Asymmetric 'A'.


① To find $Z_{Tn}(s)$, short all voltage sources, open current sources.
Use series parallel rules for combining impedances.

Reciprocity:

① Behaviour of i_m as a fun. of v_{jk} is the same as behaviour of v_{ij} as a fun. of i_m .
shown by circuits having R, L, C, transposers, uncontrolled current & voltage sources

homework:

Chapter 10

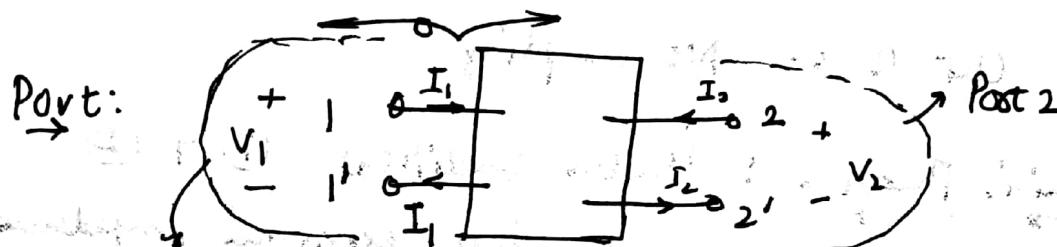


$$\frac{I_2(s)}{V_1(s)} = Y_{P2}(s)$$

$$\text{Transfer from } \frac{Z_{Tn}(s)}{V(s)} \text{ to } \frac{I(s)}{I_2(s)}$$

		(output)	
		Numerator	
		$V_2(s)$	$I_2(s)$
(Input)	$V_1(s)$	$G_{12}(s)$	$Y_{12}(s)$
	$I_1(s)$	$Z_{12}(s)$	$\alpha Y_{12}(s)$

Output / Input transfer fun.

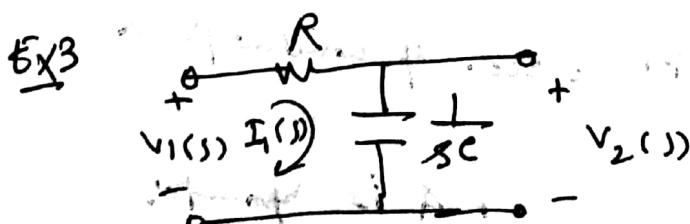

$$G_{12}(s) = \frac{V_2(s)}{V_1(s)} = \frac{\pm I_1 s c}{\pm I_1 R + \pm I_1 s c} =$$

$$\frac{1/s c}{R + 1/s c}$$

$$G_{12}(s) = \frac{1}{(R c)s + 1}$$


$$\frac{(1/R c)}{s + (1/R c)}$$

$$Y_{11}(s) = \frac{I_1(s)}{V_1(s)} = \frac{\frac{I_1(s)}{R_1}}{R_1 + \frac{1}{C_s} s} = \frac{1}{R_1 + \frac{1}{C_s} s}$$

$$= \frac{1}{R_1} \frac{1}{\left(\frac{1}{C_s} s + 1\right)}$$

$$Y_{11}(s) = \frac{s/R}{s + (1/R_C)}$$

Y₁₁(s) = V_{1(s)} V_{1(s)} = Ex 4

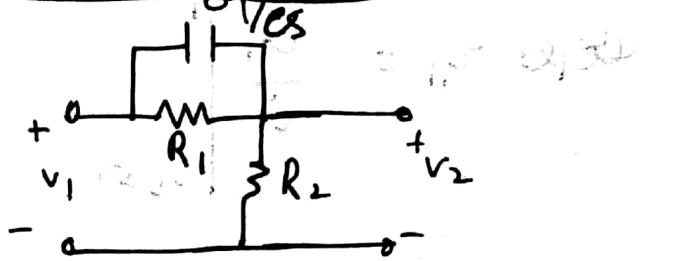

$$\Sigma = \frac{R_1/C_s}{R_1 + R_2/C_s} = \frac{R_1}{(R_1/C_s)s + 1}$$

$$v_1$$

$$v_2$$

$$G_{12} = \frac{V_2(s)}{V_1(s)} = \frac{iR_2}{\frac{1}{R_1} + iR_2}$$

$$= \frac{R_2(R_1/C_s + 1)}{R_1 + R_2(R_1/C_s + 1)}$$



Claim All transfer functions are of the form $P(s)/Q(s)$ where P & Q are polynomials

$$\text{current} = \frac{e^{j\omega t} - e^{-j\omega t}}{2j\omega}$$



Poles & Zeros

$$G_{12}(s) = \frac{s + C_1}{s + C_2}$$

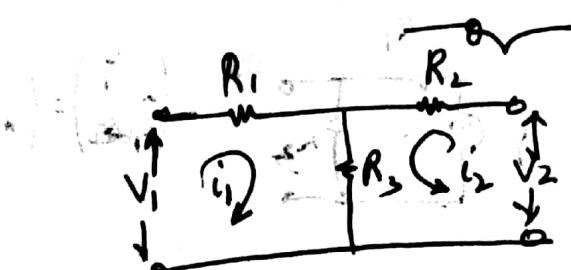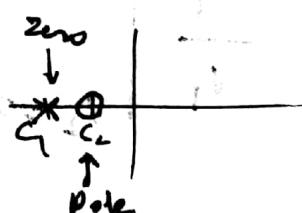

$$V_1 = i_1(R_1 + R_3) + i_2 R_2$$

$$V_2 = i_2(R_2 + R_3) + i_1 R_1$$

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} R_1 + R_3 & R_2 \\ R_2 & R_2 + R_3 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix}$$

\rightarrow Open Circuit Impedance

So,

$$\text{Defn } Z_{11} = \left. \frac{V_1}{i_1} \right|_{i_2=0}$$

$$Z_{11} = \left. \frac{V_1}{i_1} \right|_{i_2=0}$$

$$Z_{22} = \left. \frac{V_2}{i_2} \right|_{i_1=0}, \quad Z_{12} = \left. \frac{V_2}{i_1} \right|_{i_2=0}$$

Also the matrix can be written as:


$$\begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

\rightarrow Short Circuit admittance

$$Y_{11} = \left. \frac{i_1}{V_1} \right|_{V_2=0}$$

Transmission:

$$T^* = \left. \frac{i_1}{V_2} \right|_{i_2=0} = \frac{1}{R_3}$$

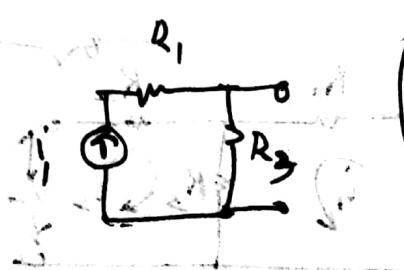

$$\begin{pmatrix} V_1 \\ I_{12} \end{pmatrix} = \begin{pmatrix} * \\ * \end{pmatrix} \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$$

Inverse Transmission

$$\begin{pmatrix} V_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ i_1 \end{pmatrix}$$

Some more examples

$$\begin{pmatrix} V_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} i_1 \\ V_2 \end{pmatrix}$$


$$h_{11} = \frac{V_1}{i_1} \Big|_{V_2=0}$$

↑ hybrid parameters

$$\begin{pmatrix} i_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ i_2 \end{pmatrix}$$

$$g_{12} = \frac{i_1}{V_1} \Big|_{i_2=0}$$

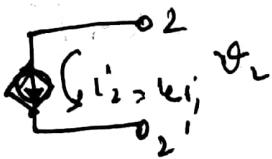Current Controlled Current Source: check can't




$$\text{So, } V_{10} = 0$$

$$i_2 = k i_1$$

$$\begin{matrix} a & \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & -k & 0 & 1 \end{pmatrix} \\ b & \begin{pmatrix} V_1 \\ i_1 \\ V_2 \\ i_2 \end{pmatrix} \end{matrix} = 0$$

$$\begin{pmatrix} V_1 \\ i_1 \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ 0 & -k \end{pmatrix} \begin{pmatrix} V_2 \\ i_2 \end{pmatrix}$$

→ Check can't:

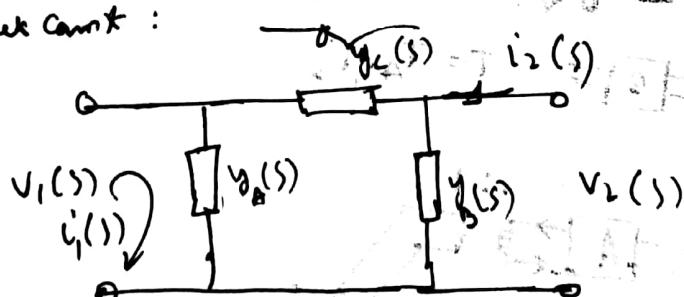

$$\begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

$$y_{11} = \frac{i_1}{V_1} \Big|_{V_2=0} = y_A + y_C$$

$$y_{12} = \frac{i_1}{V_2} \Big|_{V_1=0} = -y_C$$


$$Y_{21} = \frac{1}{V_1} \Big|_{V_2=0} = -Y_C$$

trans
vers
tions
theory

Angular
An
Anterior
Posterior
Lateral

$$Y_{22} = Y_B + Y_C$$

or

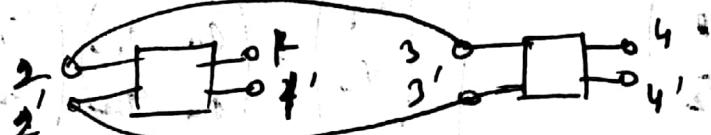


Cascade

$$\begin{pmatrix} V_1 \\ i_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ i_2 \end{pmatrix}; \quad \begin{pmatrix} V_2 \\ i_2 \end{pmatrix} = \begin{pmatrix} V_3 \\ i_3 \end{pmatrix}$$

$$\begin{pmatrix} V_3 \\ i_3 \end{pmatrix} = \begin{pmatrix} A' & B' \\ C' & D' \end{pmatrix} \begin{pmatrix} V_4 \\ i_4 \end{pmatrix}; \quad \begin{pmatrix} V_4 \\ i_4 \end{pmatrix} = \begin{pmatrix} V_5 \\ i_5 \end{pmatrix}$$

Parallel

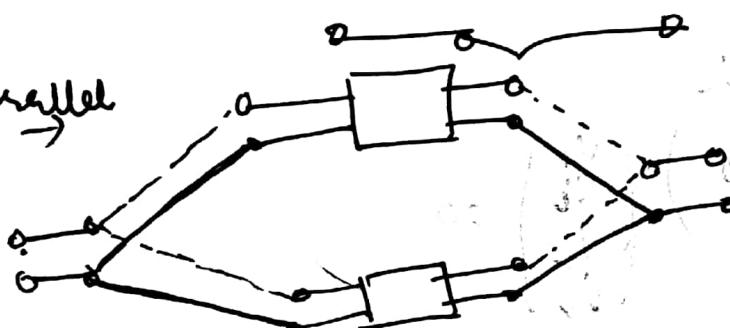

$$\begin{pmatrix} V_A \\ i_A \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_B \\ i_B \end{pmatrix}$$

→ Multiple phase images


* How does it behave?



Cascade



$$= [A \parallel B] \quad T = T_A \cdot T_B$$

Parallel

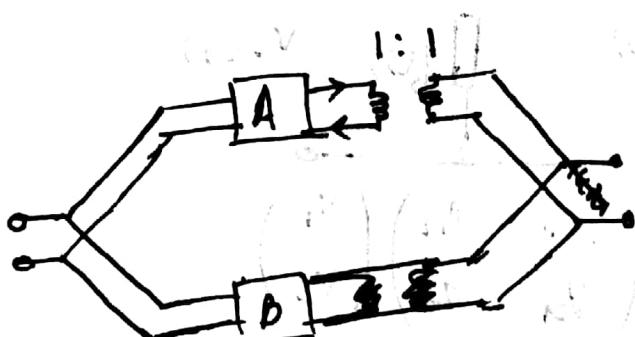


$$Y = Y_A + Y_B$$

Sources Claim : $Z = Z_A + Z_B$

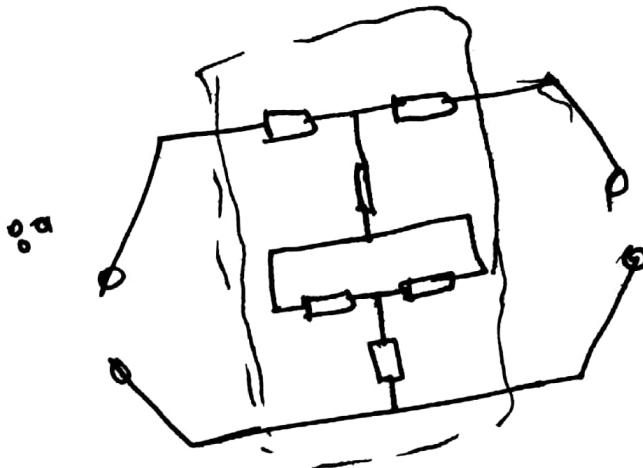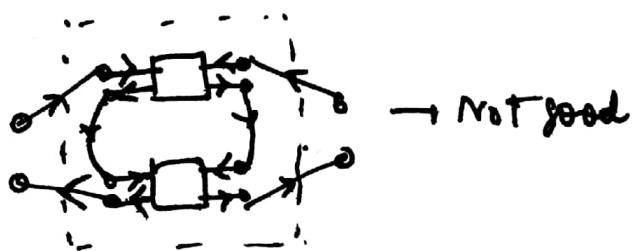

Series-parallel

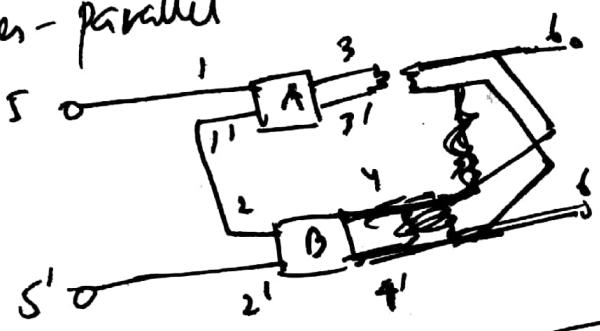

$$\begin{pmatrix} V_S \\ I_S \end{pmatrix} = \begin{pmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{pmatrix} \begin{pmatrix} I_S \\ V_L \end{pmatrix}$$

RECIPROCITY

R, C, I, Transform, Coupled inductor
1 port 2 port elect 2 port
Term 2 port elect 2 port

Chua Chap 13.6

Theorem: ① If Impedance matrix exists ; it is symmetric

② If admittance " " " " " " symmetric

③ If hybrid " " " " anti-symmetric

④ If transmission matrix exists then its determinant is 1.

(Check phone) → To see the proof of the above 4.



V_1, I_1, V_2, I_2
 $\bar{V}_1, \bar{I}_1, \bar{V}_2, \bar{I}_2$

Claim $\bar{V}_1 \bar{I}_1 + \bar{V}_2 \bar{I}_2$
 $= \bar{V}_1 I_1 + \bar{V}_2 I_2$

EE-225 Previously \rightarrow Reciprocity Theorem.

Lemma : Claim \Rightarrow Reciprocity Theorem proof.

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$\begin{pmatrix} V_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ V_2 \end{pmatrix}$$

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$


* $V_1(\text{Case 1}) I_1(\text{Case 2}) + V_2(\text{Case 1}) I_2(\text{Case 2})$
 $= V_1(\text{Case 2}) I_1(\text{Case 1}) + V_2(\text{Case 2}) I_2(\text{Case 1})$

Claim 1: $\left[V_1(1) I_1(2) + V_2(1) I_2(2) \right] \rightarrow \text{Case 1} \quad \left[V_1(2) I_1(1) + V_2(2) I_2(1) \right] \rightarrow \text{Case 2}$

To show $Z_{21} = Z_{12}$

Use (A), also see photo,
and use the defⁿ of Z_{12} & Z_{21} in different cases

In above
Case

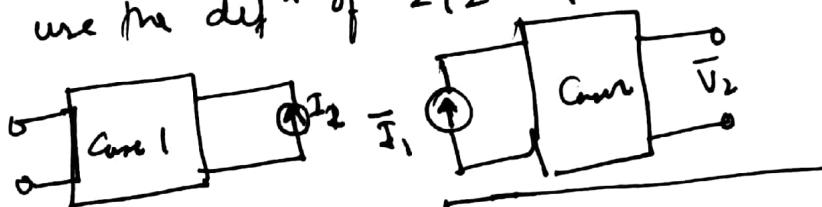

$$T = \begin{pmatrix} b & t_{11} & t_{12} \\ t_{21} & t_{22} \end{pmatrix} = \begin{pmatrix} V_1 / V_2 \Big| I_2 = 0 & \frac{-V_1}{I_2} \Big| V_2 = 0 \\ \frac{I_1}{V_2} \Big| I_2 = 0 & \frac{-I_1}{I_2} \Big| V_2 = 0 \end{pmatrix}$$




Now use the Claim (A)

Proof Of Claim: Tellegen's Theorem

Suppose the 2 port circuit corresponds to a graph with edge set E ,

$$\text{voltages } \{V_e \mid e \in E\}$$


$$\{I_e \mid e \in E\}$$

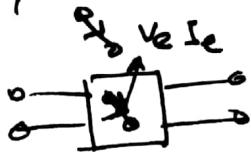

Tellegen's theorem:

$$V_1(1) I_1(2) + V_2(1) I_2(2) + \sum_{e \in E} V_e(1) I_e(2) = 0$$
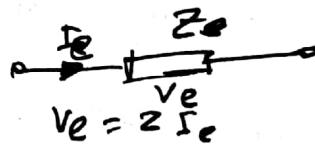
$$= V_1(2) I_1(1) + V_2(2) I_2(1) + \sum_{e \in E} V_e(2) I_e(1)$$



Claim: $\forall e \in E$

$$V_e(1) I_e(2) = V_e(2) I_e(1)$$

Proof: $\overbrace{I_e(1) Z + f_e(2)}^0 = I_e(2) Z + f_e(1)$

Sinusoidal Steady State Analysis


$$\dot{x} = f(x)$$

Steady State $\Rightarrow \{x \mid f(x) = 0\}$

$$v(t) = A \sin(\omega t) + B_1 e^{-pt} + B_2 e^{-p_2 t}$$

$$V(s) = \frac{Aw}{s^2 + \omega^2} + \frac{B_1}{s + p_1} + \frac{B_2}{s + p_2}$$
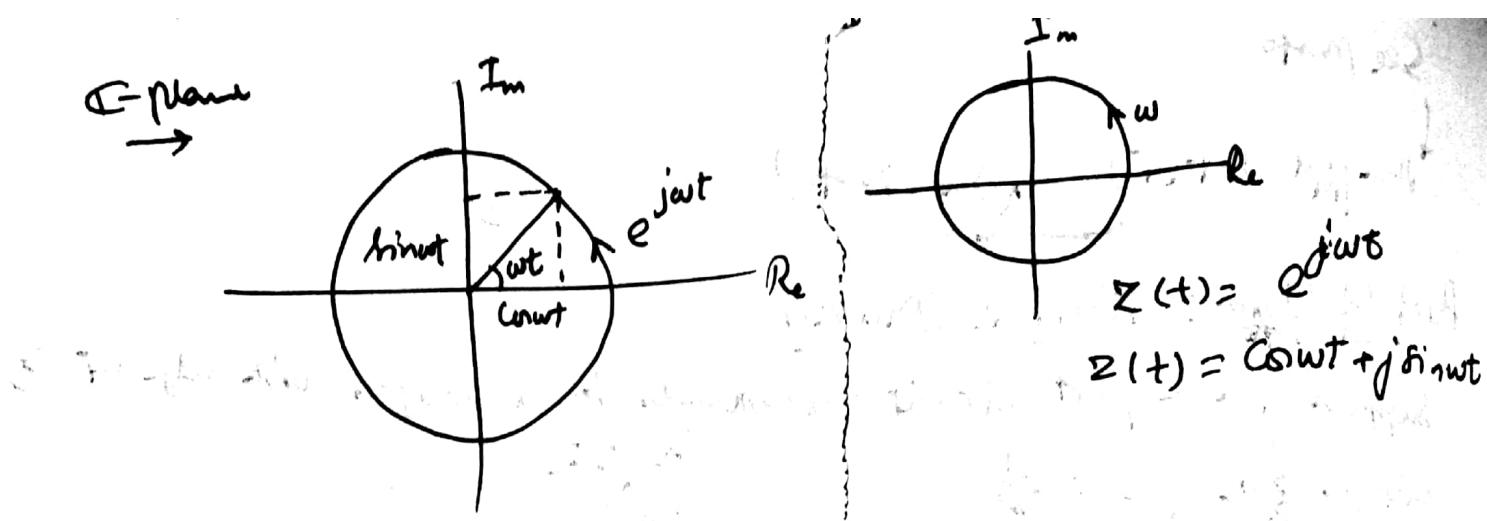
$$t > T \quad v(t) \approx A \sin \omega t$$



a general sinusoid

$$A_m \sin(\omega t + \phi)$$

\downarrow the real \mathbb{R}

If we fix ω .

$$A := A_m e^{j\phi}$$

$$A_m \cos(\omega t + \phi) = R_e(A_m e^{j\omega t})$$


$$1) R_e(A e^{j\omega t}) = R_e(B e^{j\omega t}) \Leftrightarrow A = B$$

$$\begin{aligned} 2) & a_1 R_e(A_1 e^{j\omega t}) + a_2 R_e(A_2 e^{j\omega t}) \\ &= R_e((a_1 A_1 + a_2 A_2) e^{j\omega t}) \quad \forall a_1, a_2 \in \mathbb{R} \end{aligned}$$


$$3) \frac{d}{dt} (R_e(A e^{j\omega t})) = R_e(j\omega A e^{j\omega t})$$

→ Sinusoidal Steady State at the freq. ω .

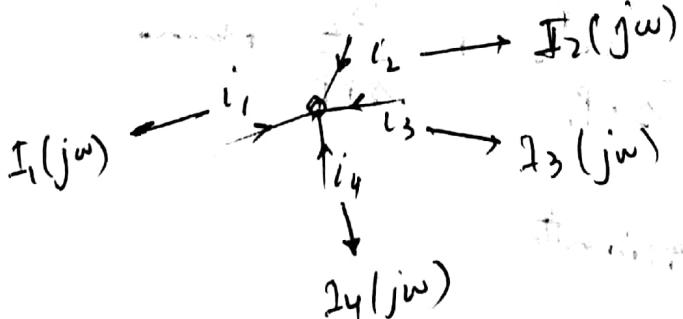at mean $\Rightarrow v_e(t), i_e(t), v_n(t)$ are sinusoidal at the same ω .


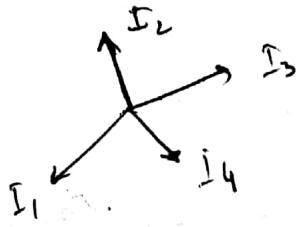
$$KCL: I_1(t) + I_2(t) + I_3(t) + I_4(t) = 0$$



$$I_1 + I_2 + I_3 + I_4 = 0$$

$$V = Z I$$

$$I = V v$$


\rightarrow Capacitors

$$i = C \frac{dV}{dt}$$


$$\Rightarrow I = C j \omega V$$

$$\Rightarrow I = (j \omega C) V$$
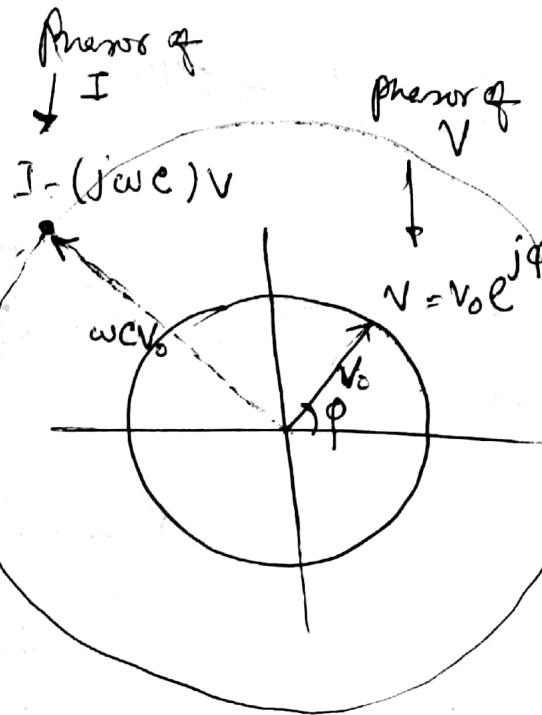
$$I = j \omega C V_0 e^{j(\pi/2 + \phi)}$$



\rightarrow Inductors

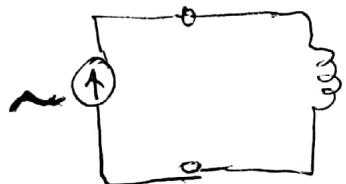


$$i(t) = A_m \cos(\omega t + \phi)$$

$$V = L \frac{di}{dt}$$

$$v(t) = j \omega A_m \sin(\omega t + \phi)$$
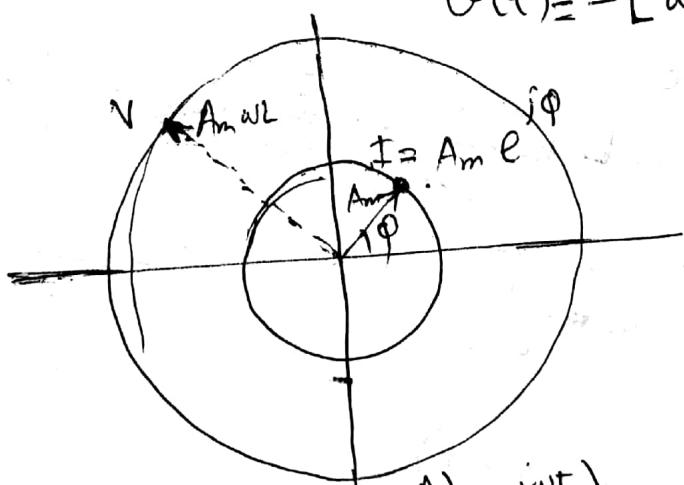
$$v(t) = -L \omega A_m \sin(\omega t + \phi)$$




$$v(t) = R_e (A_m \omega L e^{j(\pi/2 + \phi)} e^{j\omega t})$$

$$= \omega L A_m \cos(\omega t + \frac{\pi}{2} + \phi)$$

$$= -\omega L A_m \sin(\omega t + \phi)$$

DRIVING POINT

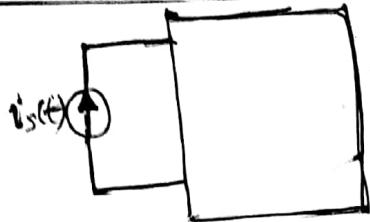


$$i_s(t) = A_m \cos(\omega t + \phi)$$

$$\text{driving pt. impedance} = Z(j\omega) = \frac{V}{I_s}$$

When we wait for quite some time the transient die down

driving pt.
admittance

$$\Rightarrow V_s(t)$$

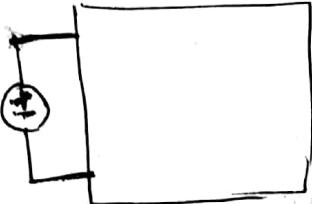


REVERSE

$$v_s(t)$$

$$Y(j\omega) = \frac{I}{V_s} = \frac{1}{Z(j\omega)}$$

driving pt.
admittance

EX RLC:

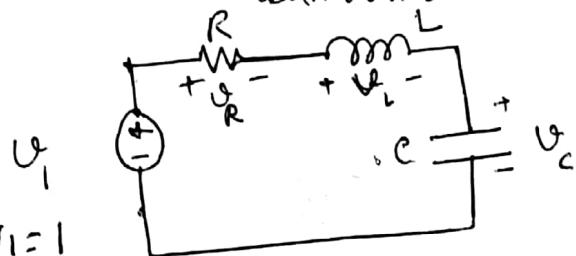

$$V_1 = \text{constant}, V_1 = 1$$

$$V_1 = V_R + V_L + V_C$$

$$Z(j\omega) = R + j\omega L + \frac{j}{\omega C} = R + j(\omega L - \frac{1}{\omega C})$$

$$I = \frac{V_1}{Z} = \frac{1}{R + j\omega L - \frac{j}{\omega C}}$$

$$\begin{aligned} & \cancel{\frac{\omega C}{j}} \cancel{\frac{Z}{R}} \quad \cancel{\frac{\omega L - \frac{1}{\omega C}}{R}} \\ & \theta = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right) \end{aligned}$$

$$i_s(t) = A \cos(\omega t + \phi)$$

$$A = I_1$$


$$\phi = -\tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

$$I = \cancel{V_1} \frac{V_1}{ZL} = \frac{V_1}{ZL}$$

$$= \left| \frac{V_1}{Z} \right| \angle -\theta$$

$$= \frac{\cos \theta}{|Z|} - \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

Simple Harmonic Oscillator

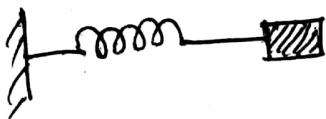

$$m \ddot{x} = -kx$$



$$m \ddot{\theta} = -\theta$$

LC oscillations

$$V_C + V_L = 0$$



$$\Rightarrow \cancel{V_C} = -\cancel{V_L}$$

$$V_C = -V_L$$

as ~~in case~~

$$c \frac{dV_C}{dt} = i$$

↓

$$-c \frac{dV_L}{dt} = i$$

$$-cL \frac{di}{dt^2} = i$$

$$V_L = L \frac{di}{dt}$$

~~$$\frac{dV_L}{dt} = L \frac{d^2i}{dt^2}$$~~

$$\frac{dV_L}{dt} = L \frac{d^2i}{dt^2}$$