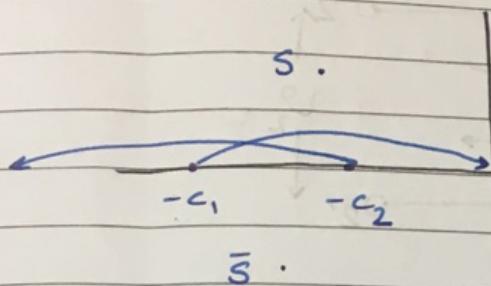


Poles & Zeros

classmate

Date _____

Page _____



Thinking of transfer functions as conformal mappings.

$$\text{or } G_{12}(s) = \left(\frac{s + c_1}{s + c_2} \right)$$


$$f(z, t) = z(1-t) + tG_{12}(s)$$

25-10-17


Lec - 24

→ Last time: Two-port Systems, Reciprocity thm.

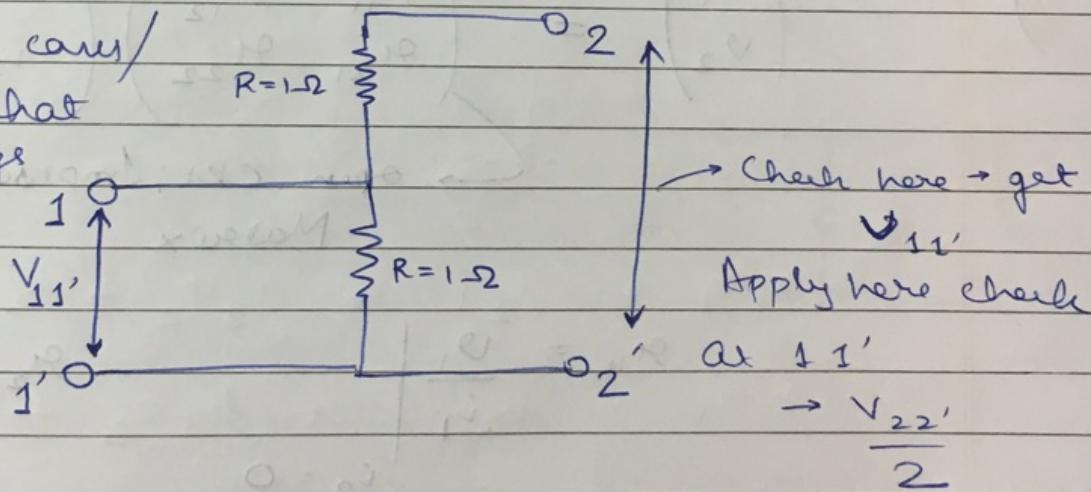→ Exception case/
this is not what
Reciprocity says




→ Today: Examples of 2 port Networks

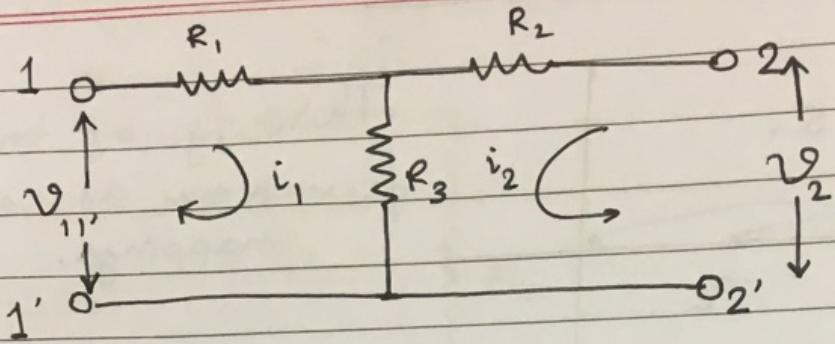

2)

$$v_1, v_2, i_1, i_2$$

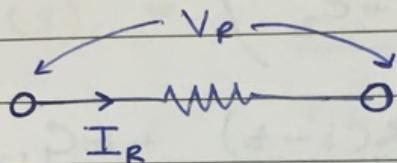

$$V_R - RI_R = 0$$

$$v_1 = i_1 (R_1 + R_3) + i_2 R_3$$

$$v_2 = i_2 (R_2 + R_3) + i_1 R_3$$

3)

$$\begin{pmatrix} v_1 \\ v_2 \end{pmatrix} = \begin{pmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix}$$

open circuit Impedance Matrix

$$g_{11} = \frac{v_1}{i_1} \quad |_{i_2=0}$$

$$g_{21} = \frac{v_2}{i_1} \quad |_{i_2=0}$$

4)

$$g_{12} = \frac{v_1}{i_2} \quad |_{i_1=0}$$

$$g_{22} = \frac{v_2}{i_2} \quad |_{i_1=0}$$

Short ckt admittance

$$2) \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix}$$


$$\left| \begin{array}{c} \frac{i_1}{v_1} \\ v_2 = 0 \end{array} \right| = \frac{R_2 + R_3}{R_2 R_3 + R_1 (R_2 + R_3)}$$

$$\frac{1}{R_2 R_3 + R_1} = \frac{1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} = \frac{R_2 + R_3}{R_2 R_3 + R_1 (R_2 + R_3)}$$

$$3) \begin{pmatrix} v_1 \\ i_1 \end{pmatrix} = \begin{pmatrix} ? \\ ? \end{pmatrix} \begin{pmatrix} v_2 \\ i_2 \end{pmatrix}$$

Transmission Mat.

$$\text{Trans} \quad \left| \begin{array}{c} i_1 \\ v_2 \\ i_2 = 0 \end{array} \right| = \frac{1}{R_3} \quad 0v_2 + xi_2$$

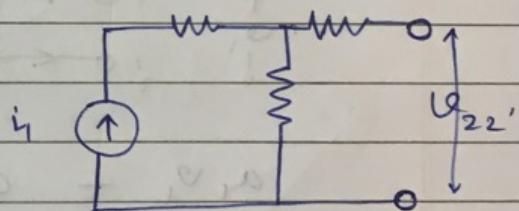

4) Inverse transmission Hypered para.

$$\begin{pmatrix} v_2 \\ i_2 \end{pmatrix} = \begin{pmatrix} R_{22'} & R_{21} \\ R_{12} & R_{11} \end{pmatrix} \begin{pmatrix} v_1 \\ i_1 \end{pmatrix}$$

5)

Hybrid


$$\begin{pmatrix} v_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} i_1 \\ v_2 \end{pmatrix}$$

6)

$$\begin{pmatrix} i_1 \\ v_2 \end{pmatrix} = \begin{pmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{pmatrix} \begin{pmatrix} v_1 \\ i_2 \end{pmatrix}$$

$$g_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0}$$



Linear two port (Resistor)

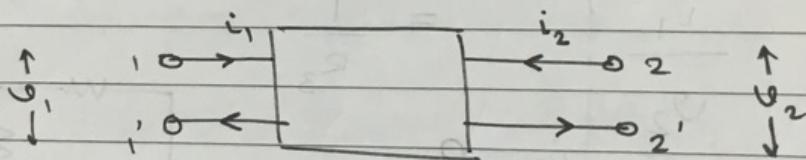

$$a_1 v_1 + a_2 i_1 + a_3 v_2 + a_4 i_2 = 0$$

$$b_1 v_1 + b_2 i_1 + b_3 v_2 + b_4 i_2 = 0$$

Current - controlled current source

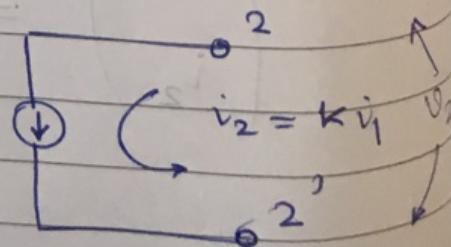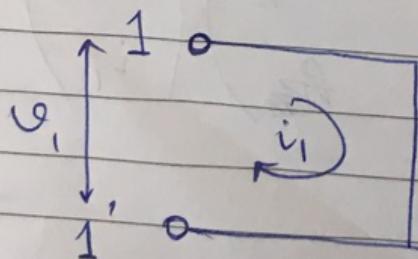

We have equations

$$\begin{aligned} v_1 &= 0 && \text{(Shorted)} \\ i_2 &= k i_1 \end{aligned}$$


$$a \begin{pmatrix} v_1 & i_1 & v_2 & i_2 \\ 1 & 0 & 0 & 0 \\ b & 0 & -k & 0 & 1 \end{pmatrix} \begin{pmatrix} v_1 \\ i_1 \\ v_2 \\ i_2 \end{pmatrix} = 0$$

$$-s \begin{bmatrix} 0 & 0 \\ 0 & 1/k \end{bmatrix} \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

$$\begin{pmatrix} v_1 \\ i_1 \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ 0 & -k \end{pmatrix}^{-1} \begin{pmatrix} 0 & 0 \\ 0 & -1 \end{pmatrix} \begin{pmatrix} v_2 \\ i_2 \end{pmatrix}$$

$$\begin{bmatrix} 1 & 0 \\ 0 & -k \end{bmatrix} \begin{pmatrix} v_1 \\ i_1 \end{pmatrix}$$
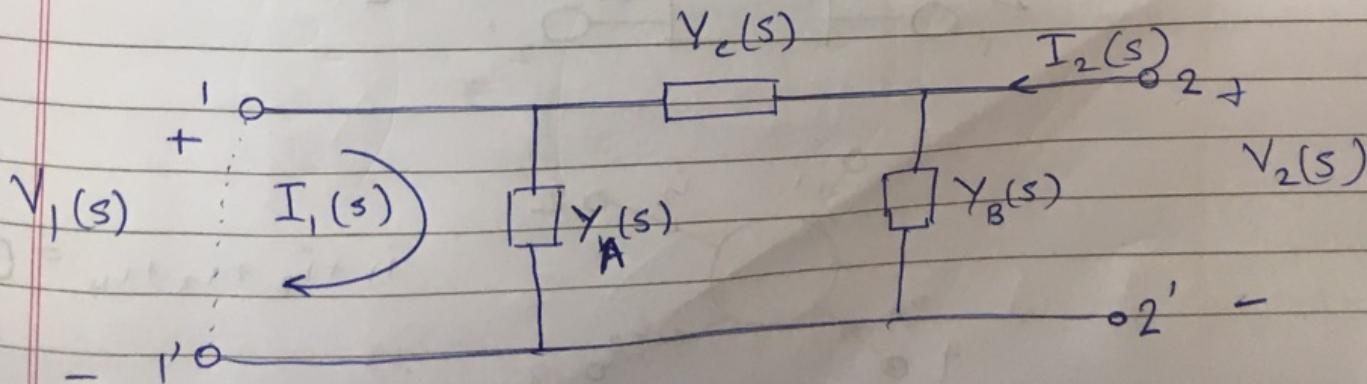
$$\begin{bmatrix} 1 & 0 \\ 0 & -k \end{bmatrix} \begin{pmatrix} v_1 \\ i_1 \end{pmatrix} = \begin{pmatrix} 0 & 0 \\ 0 & -1 \end{pmatrix} \begin{pmatrix} v_2 \\ i_2 \end{pmatrix}$$



$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

$$Y_{11} = \frac{I_1}{V_1} \quad \left| \begin{array}{l} V_2 = 0 \\ V_1 \neq 0 \end{array} \right. \quad = Y_A + Y_c$$



Admittance
add in parallel

$$Y_{12} = \frac{I_1}{V_2} \quad \left| \begin{array}{l} V_2 \neq 0 \\ V_1 = 0 \end{array} \right. \quad = -Y_c$$

$$Y_{21} = \frac{I_2}{V_1} \quad \left| \begin{array}{l} V_1 \neq 0 \\ V_2 = 0 \end{array} \right. \quad = -Y_c$$

$$Y_{22} = Y_B + Y_c$$

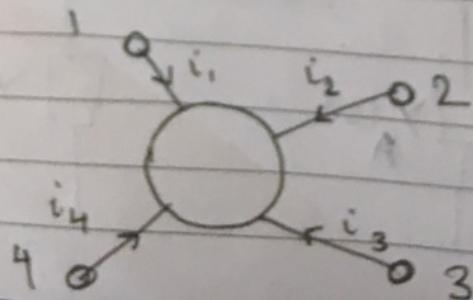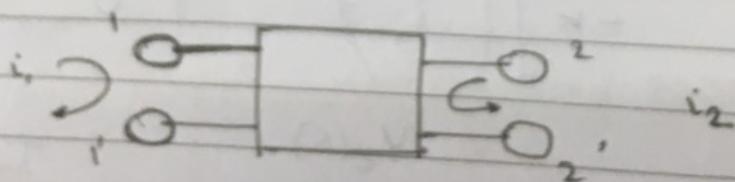
→ 2 port Network √
 4 port 4 terminal
 device



$$i_1 + i_2 + i_3 + i_4 = 0$$

→ Combination of 2 port Networks

(1) Cascading

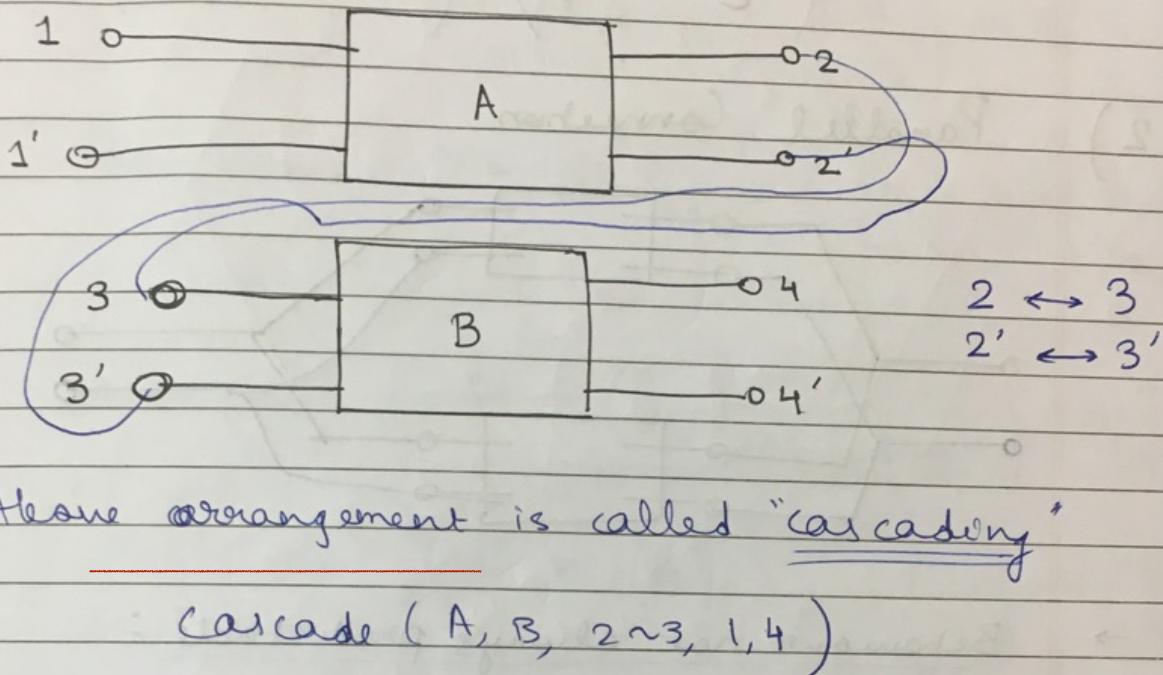

Hint: Transmission Matrix

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$$


$$\begin{pmatrix} V_2 \\ I_2 \end{pmatrix} = \begin{pmatrix} V_3 \\ -I_3 \end{pmatrix}$$

$$\begin{pmatrix} V_3 \\ I_3 \end{pmatrix} = \begin{pmatrix} A' & B' \\ C' & D' \end{pmatrix} \begin{pmatrix} V_4 \\ I_4 \end{pmatrix}$$


$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \left(\quad \right) \begin{pmatrix} V_4 \\ I_4 \end{pmatrix}$$

$$= \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} A' & B' \\ -C' & -D' \end{pmatrix} \begin{pmatrix} V_4 \\ I_4 \end{pmatrix}$$

(2) Parallel Connection

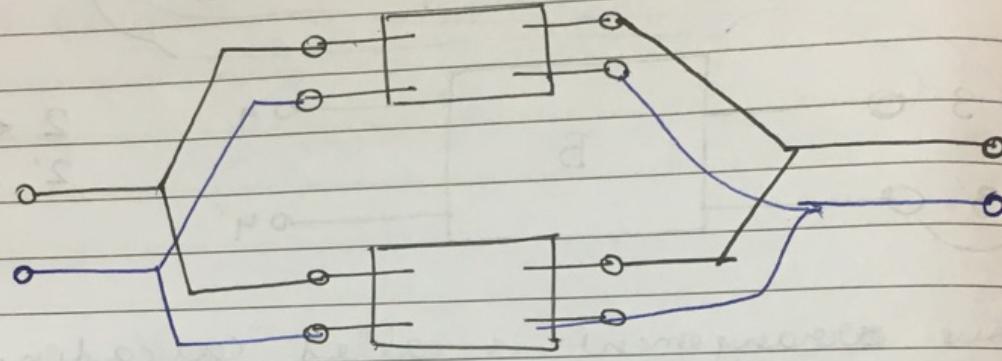

→ Behaviour not always predictable :

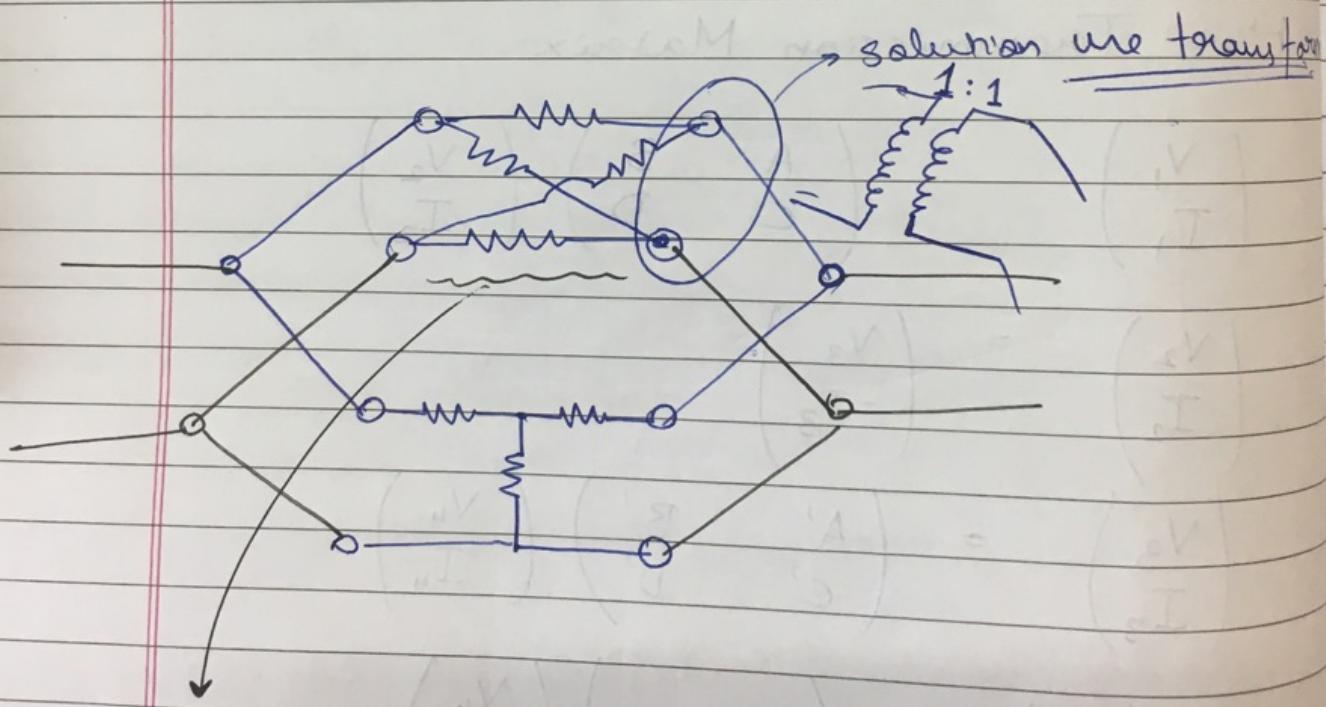

Current
will never
flow, condition
for port
worked

Last time

→ Linear 2-port


Impedance $Z = (Z_{ij})_{2 \times 2}, \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = Z \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$

Admittance $Y = (Y_{ij})_{2 \times 2}, \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = Y \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$

Hybrid $\left\{ \begin{array}{l} H = (h_{ij})_{2 \times 2}, \begin{pmatrix} V_1 \\ I_2 \end{pmatrix} = H \begin{pmatrix} I_1 \\ V_2 \end{pmatrix} \\ H' = (h'_{ij})_{2 \times 2}, \begin{pmatrix} I_1 \\ V_2 \end{pmatrix} = H' \begin{pmatrix} V_1 \\ I_2 \end{pmatrix} \end{array} \right.$


Transmission $\left\{ \begin{array}{l} T = (t_{ij})_{2 \times 2}, \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = T \begin{pmatrix} V_2 \\ I_2 \end{pmatrix} \\ T' = (t'_{ij})_{2 \times 2}, \begin{pmatrix} V_2 \\ I_2 \end{pmatrix} = T' \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} \end{array} \right.$

→ Cascading

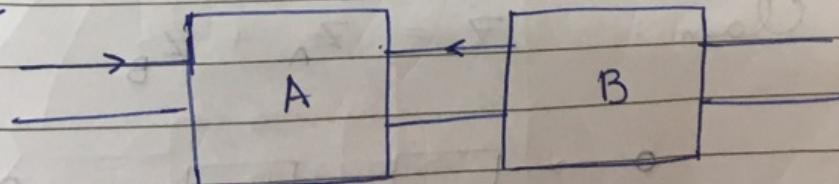

$$T = T_A \cdot T_B \quad \{ \text{Modulus signs} \}$$


→ Parallel

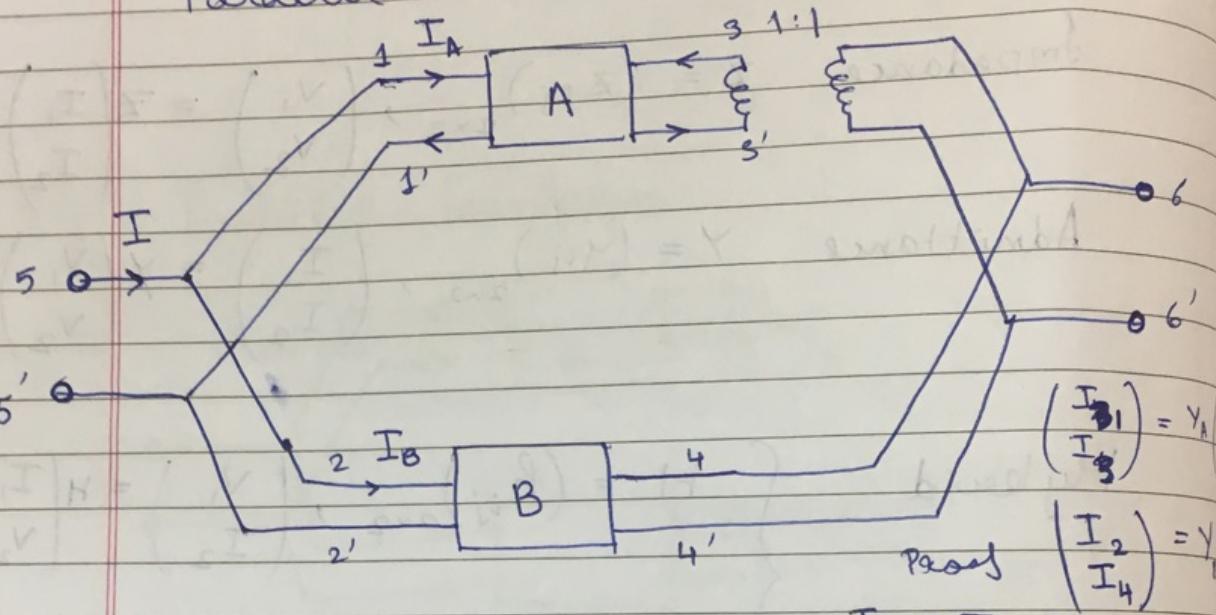


Claim: $\left(\frac{I_5}{V_b} \right) = (Y_A + Y_B) \left(\frac{N_5}{V_b} \right)$

Proof: $\left(\frac{I_2}{V_b} \right) = Y_1$
 $I_5 = I_1 + I_2$
 $I_6 = I_3 + I_4$


→ Series

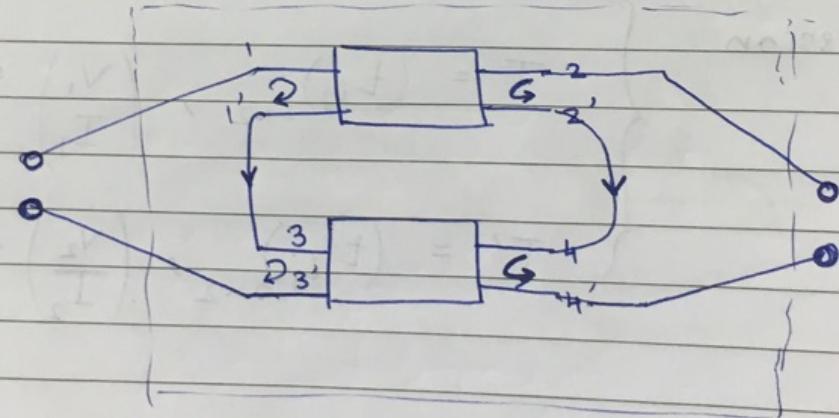


Claim: $Z = Z_A + Z_B$

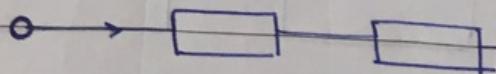


Series part

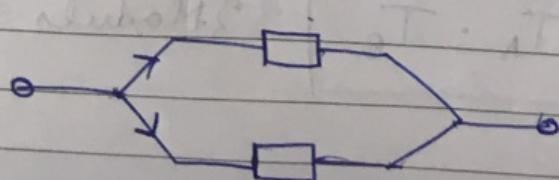

→ Case when part Nature breaks down

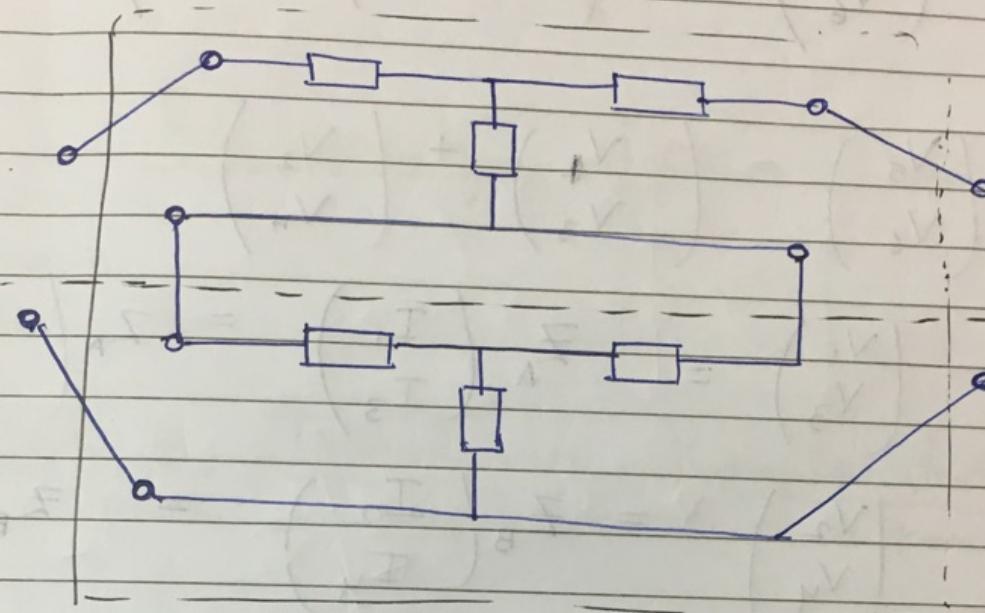

Solution : Use transformers

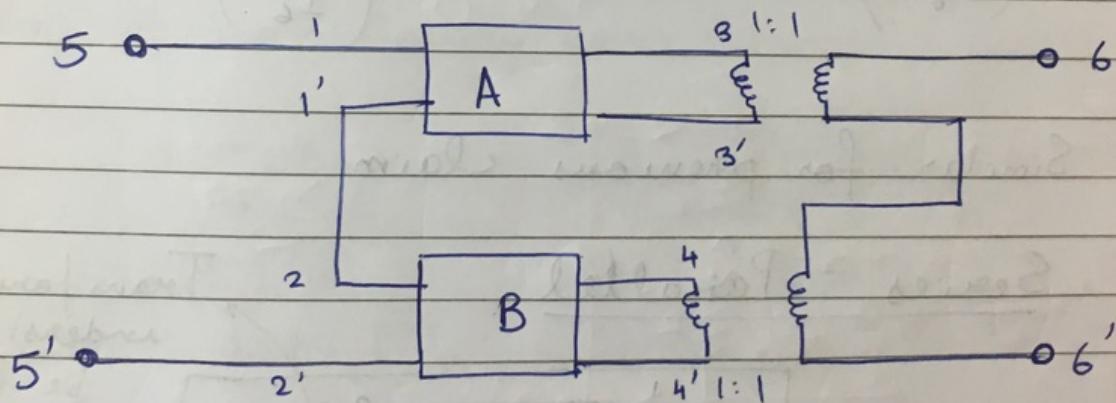

$$I_5 = I_1 = I_2$$

$$I_6 = I_3 = I_4$$

$$V_5 = V_1 + V_2$$

$$V_6 = V_3 + V_4$$

$$\begin{pmatrix} V_5 \\ V_6 \end{pmatrix} = \begin{pmatrix} \text{[redacted]} \\ \text{[redacted]} \end{pmatrix} \begin{pmatrix} I_5 \\ I_6 \end{pmatrix}$$

$$\begin{pmatrix} V_5 \\ V_6 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_3 \end{pmatrix} + \begin{pmatrix} V_2 \\ V_4 \end{pmatrix}$$


$$\begin{pmatrix} V_1 \\ V_3 \end{pmatrix} = Z_A \begin{pmatrix} I_1 \\ I_3 \end{pmatrix} = Z_A \begin{pmatrix} I_5 \\ I_6 \end{pmatrix} \rightarrow$$

$$\begin{pmatrix} V_2 \\ V_4 \end{pmatrix} = Z_B \begin{pmatrix} I_2 \\ I_4 \end{pmatrix} = Z_B \begin{pmatrix} I_5 \\ I_6 \end{pmatrix}$$

$$\begin{pmatrix} V_5 \\ V_6 \end{pmatrix} = (Z_A + Z_B) \begin{pmatrix} I_5 \\ I_6 \end{pmatrix}$$

→ Similar for previous claim

→ Series - Parallel

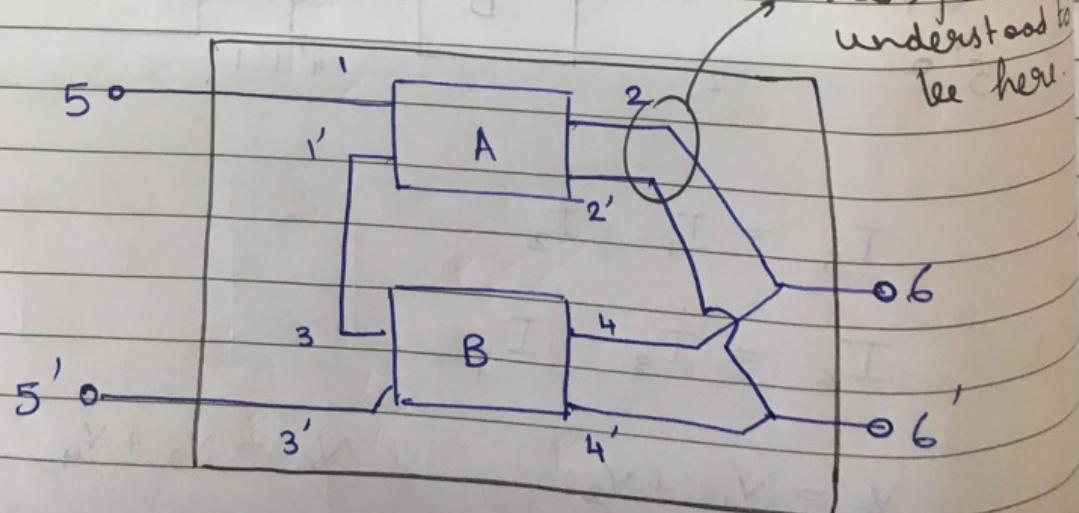


$$\begin{pmatrix} V_5 \\ I_6 \end{pmatrix} = (H_A + H_B) \begin{pmatrix} I_5 \\ V_6 \end{pmatrix}$$

Reciprocity [Ref: Chua : Chap 13.6]

Theorems

→ Valid for,

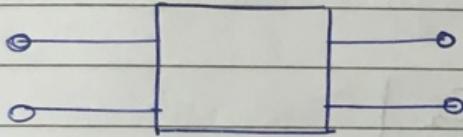R, C, L, Transformer, Coupled Inductor
1-port 2-port 2-port



Thm: If the following exist, then;

$$(1) \quad Z_{12} = Z_{21}$$


$$(3) \quad h_{21} = -h_{12}$$

$$(5) \quad \det(T) = 1 \\ = \det(T')$$

$$(2) \quad Y_{12} = Y_{21} \quad Y_{12} = Y_{21}$$

$$(4) \quad h'_{21} = -h'_{12}$$


→ Example

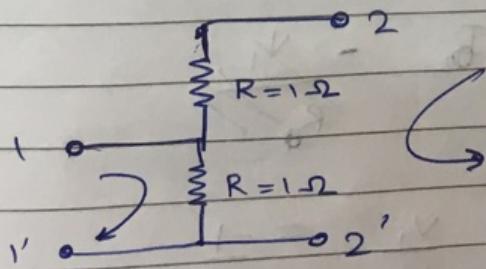

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = R$$


$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{R \times I_2}{I_2} = R$$

$$2) \quad Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

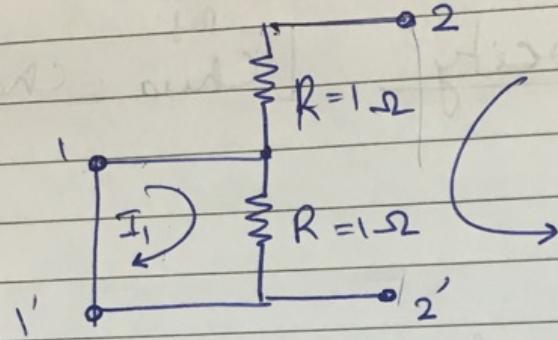

$$\therefore I_1 = -\frac{V_2}{R} \Big/ V_2 = -\frac{1}{R}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

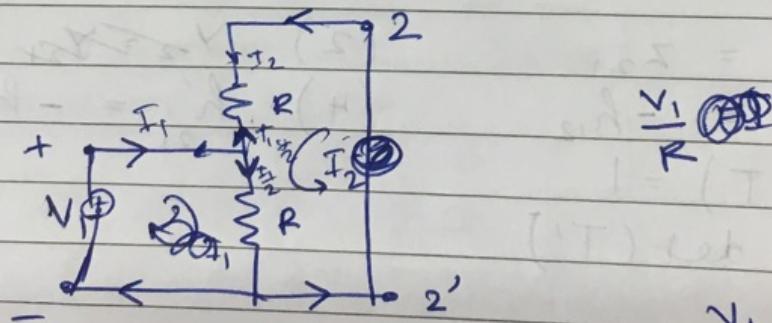

$$V_1 = I_2 R$$

$$T_2 - \frac{V_1}{R}$$

$$-\frac{1}{R} \frac{V_1}{V_1} = -\frac{1}{R}$$

3)

4)

5)

3) $h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = -\frac{1}{2}$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{1}{2}$$

4) $h'_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} = 1$

$$h'_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0} = -1$$

5) $t_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1$

$$t_{12} = \left. -\frac{V_1}{I_2} \right|_{V_2=0} = -R$$

$$\det(T) = 1$$


$$t_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{R}$$

$$t_{22} = \left. -\frac{I_1}{I_2} \right|_{V_2=0} = -2$$

$$\det T = 1$$

$$\begin{matrix} 1 & -R \\ \frac{1}{R} & 2 \end{matrix}$$

~~$$(2-1)=1$$~~

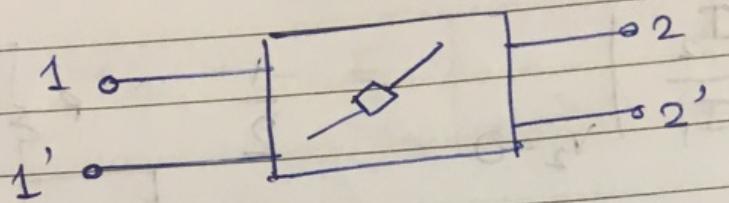

v_1, I_1, v_2, I_2

$\bar{v}_1, \bar{I}_1, \bar{v}_2, \bar{I}_2$

Claim :

$$N_1 \bar{I}_1 + N_2 \bar{I}_2$$

$$= \bar{v}_1 I_1 + \bar{v}_2 I_2$$

→ Prove using Tellegen's thm

1.11.17

Recap

- Series / Parallel / Cascade connection of 2 parts.

- Reciprocity thm

→ For a 2-port made up of R, L, C & coupled Inductors

$$Z_{12} = Z_{21}$$

$$h_{12} = -h_{21}$$


$$Y_{21} = Y_{12}$$

$$h'_{12} = -h'_{21}$$


$$\det(T) = 1, \det(T') = 1$$

Claim:

(1)

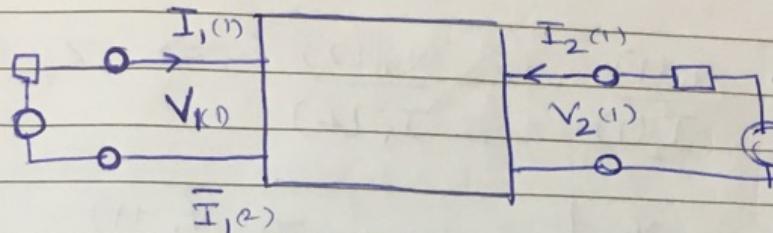Connection Method - 1

(2)

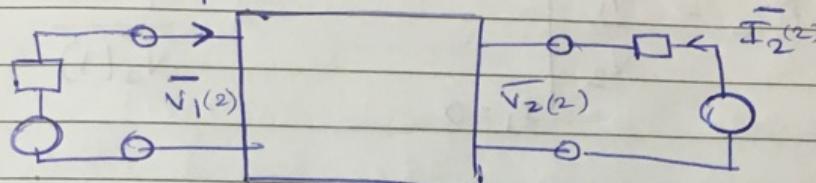

$$V_1 \bar{I}_1 + V_2 \bar{I}_2 = \bar{V}_1 I_1 + \bar{V}_2 I_2$$

$$\Rightarrow V_1 I_{1(2)} + V_2 I_{2(1)} = V_1(2) I_{1(1)} + V_2(2) I_{2(1)}$$

Lemma


Claim: Reciprocity theorem

Proof :


$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{V_1(1)}{I_2(1)}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{V_2(2)}{I_1(2)}$$

Case 1:

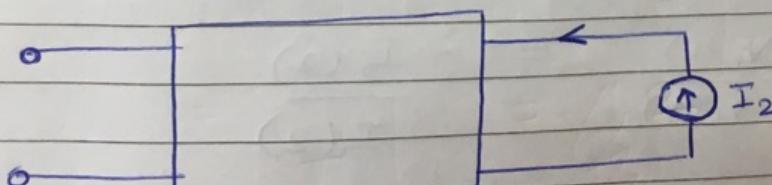

Case 2:

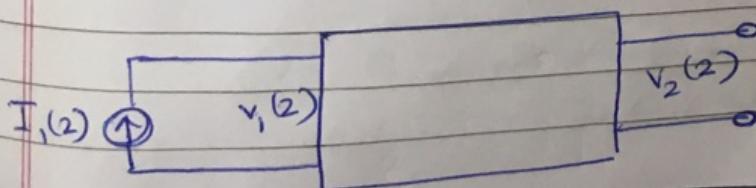



$$\Rightarrow V_1(1) I_1(2) = V_2(2) I_2(1)$$

$$\Rightarrow \frac{V_1(1)}{I_2(1)} = \frac{V_2(2)}{I_1(2)} \Rightarrow Z_{12} = Z_{21}$$

$$h_{12} = \left| \begin{array}{l} \frac{V_1}{V_2} \\ I_1=0 \end{array} \right| = \frac{V_1(1)}{V_2(1)}$$

$$h_{21} = \left| \begin{array}{l} \frac{I_2}{I_1} \\ V_2=0 \end{array} \right| = \frac{I_2(2)}{I_1(2)}$$

Case 1:

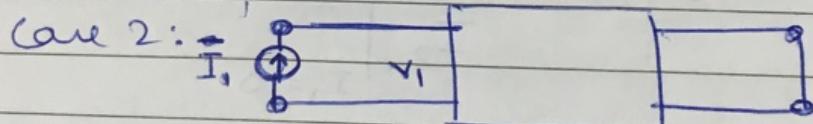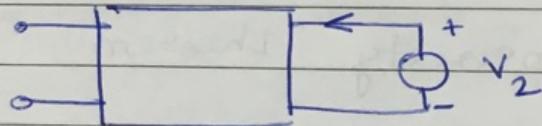

from claim



$$V_1(1) I_1(2) = -V_2(2) I_2(2)$$

$$\frac{V_1(1)}{V_2(1)} = -\frac{I_2(2)}{I_1(2)}$$

$$\Rightarrow h_{12} = -h_{21}$$

using
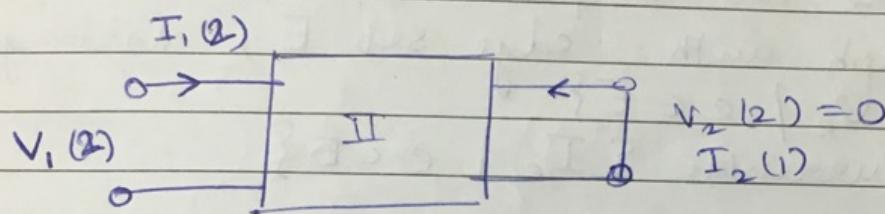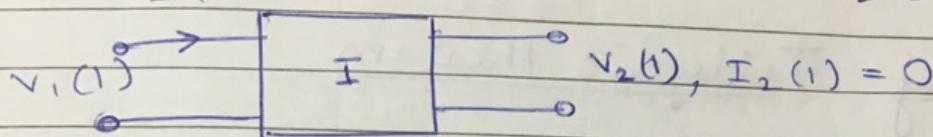
$$T = \begin{pmatrix} \frac{V_1}{V_2} & -\frac{V_1}{I_2} \\ \frac{I_1}{V_2} & -\frac{I_1}{I_2} \end{pmatrix} \quad \begin{array}{l} I_2=0 \\ V_2=0 \end{array} \quad \begin{array}{l} I_2=0 \\ V_2=0 \end{array}$$



$$T = \begin{pmatrix} \frac{V_1(1)}{V_2(1)} & -\frac{V_1(2)}{I_2(2)} \\ \frac{I_1(1)}{V_2(1)} & -\frac{I_1(2)}{I_2(2)} \end{pmatrix}$$


$$\det T = \frac{-V_1(1) I_1(2)}{V_2(1) I_2(2)} + \frac{V_1(2) I_1(1)}{I_2(2) V_2(1)} = 1$$

$$= \frac{V_1(2) I_1(1) - V_1(1) I_1(2)}{V_2(1) I_2(2)}$$

Willy Claim ; $V_1^{(1)} I_1(2) + V_2(1) I_2(2) = V_1(2) I_1(1)$

$$\Rightarrow \frac{V_1(2) I_1(1) - V_1(1) I_1(2)}{V_2(1) I_2(2)} = 1$$

→ Proof of Claim

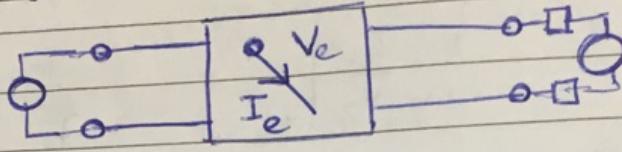

Using Tellegen's theorem

- Suppose the 2-port circuit corresponds to a graph with edge set E , voltages $\{V_e | e \in E\}$ and currents $\{I_e | e \in E\}$

- Applying Tellegen's thm:

$$V_1(1) I_1(2) + V_2(1) I_2(2) + \sum_{e \in E} V_e(1) I_e(2)$$

$$= 0 = V_1(2) I_1(1) + V_2(2) I_2(1) + \sum_{e \in E} V_e(2) I_e(1)$$

- We want to prove our claim.

3.11.17 →

$\mathcal{Z}_e = I_e Z_e$

General edge

Claim: $\forall e \in E$

$$V_e(1) I_e(2) = V_e(2) I_e(1)$$

$$\text{Pf} \quad v_e(1) = I_e(1) z_0, \quad v_e(2) = I_e(2) z_0$$

$$I_e(1) z_0 I_e(2) = L.H.S = I_e(2) z_0 I_e(1) \\ = R.H.S$$

Hence proved

Chap 12: Mesh analysis

Sinusoidal Steady State Analysis

$$\dot{x} = f(x)$$

$$\text{Steady State} \Rightarrow \{x \mid f(x) = 0\}$$

$$V(s) = \frac{A\omega}{s^2 + \omega^2} + \frac{B_1}{s + p_1} + \frac{B_2}{s + p_2}$$

$$v(t) = \underbrace{A \sin(\omega t)}_{\text{Recurrent}} + \underbrace{B_1 e^{-p_1 t} + B_2 e^{-p_2 t}}_{\text{Transient}}$$

$$t > T, v(t) \approx ? = A \sin(\omega t)$$

~~$$V(s) = \frac{A\omega}{s^2 + \omega^2}$$~~

3.11.17

Recap

→ Reciprocity theorem

- Sinusoidal Steady State Analysis

$$A_m \cos(\omega t + \phi) \quad \epsilon [0, 2\pi) \\ \epsilon R > 0$$

→ Fix ω :

$$A = A_m e^{j\phi} \\ A_m \cos(\omega t + \phi) = \operatorname{Re}(A e^{j\omega t})$$

$$1) \quad \operatorname{Re}(A e^{j\omega t}) = \operatorname{Re}(B e^{j\omega t})$$

\Downarrow

$$A = B$$

$$2) \quad a_1 \operatorname{Re}(A_1 e^{j\omega t}) + a_2 \operatorname{Re}(A_2 e^{j\omega t})$$


$$= \operatorname{Re}((a_1 A_1 + a_2 A_2) e^{j\omega t}) \quad \forall a_1, a_2$$

$$3) \quad \frac{d}{dt} (\operatorname{Re}(A e^{j\omega t})) = \operatorname{Re}(j\omega A e^{j\omega t})$$

Interchangeable.

Sinusoidal Steady State at frequency

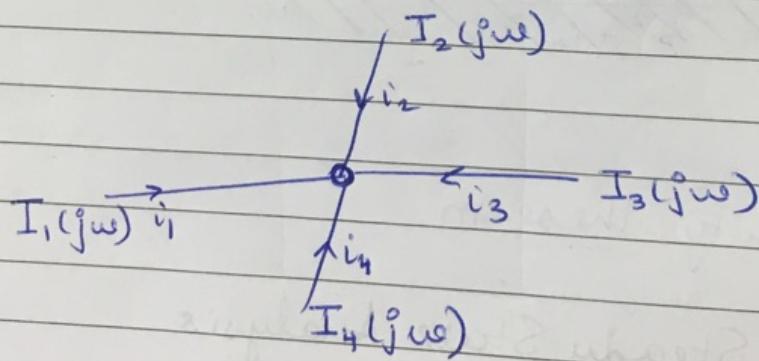- All $v_e(t)$, $i_e(t)$, $v_n(t)$ are sinusoids at the same ω
- $e \equiv \text{edge}$ $n \equiv \text{node}$



$$\text{KCL: At } \text{ node } i_1(t) + i_2(t) + i_3(t) + i_4(t) = 0$$

$$\Rightarrow \frac{I_1 + I_2 + I_3 + I_4}{V} = 0$$


$$I = Y V$$

$$\dot{I} = C \frac{dV}{dt}$$

$$I - (j\omega C)V \Rightarrow V = j\omega C$$


→ I is V oscillated by $j\omega C$
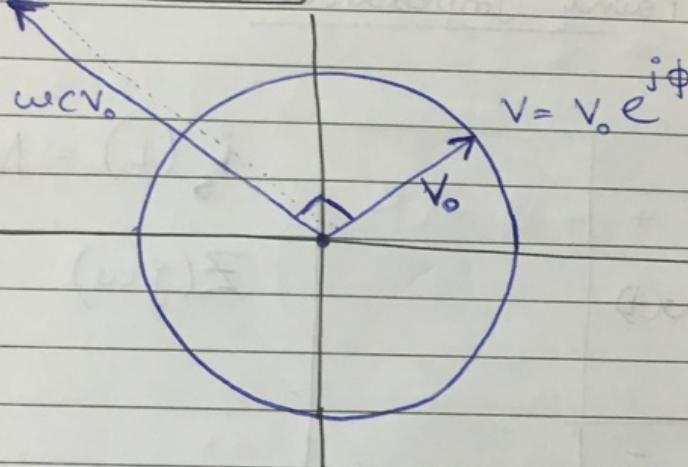
$$I = V_0 \omega C e^{j(\frac{\pi}{2} + \phi)}$$



→ Admittances: $\frac{1}{j\omega C}$, $j\omega L$, R

$\rightarrow Q$

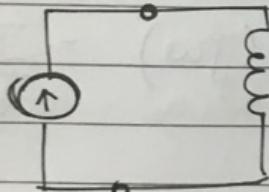


$$V = L \frac{di}{dt}$$

$$i(t) = A_m \cos(\omega t + \phi)$$

$$v(t) = -(j\omega L) A_m \sin(\omega t + \phi)$$

using Phasors

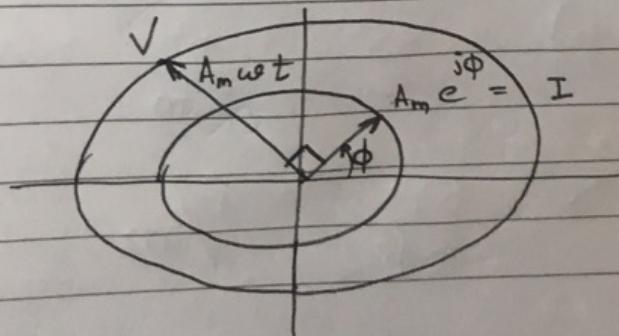


$$V(t) = \operatorname{Re} \left(A_m \omega L e^{j(\frac{\pi}{2} + \phi)} e^{j\omega t} \right)$$

$$= \omega L A_m \cos \left(\omega t + \frac{\pi}{2} + \phi \right)$$

$$= -\omega L A_m \sin (\omega t + \phi)$$

Q→


→ Driving Point Impedance

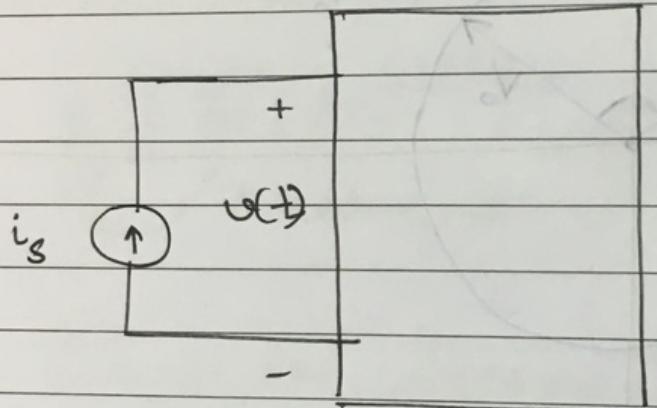

$$i_s(t) = A_m \cos(\omega t)$$

$$Z(j\omega) = \frac{V}{I_s}$$

→ Driving Point Admittance

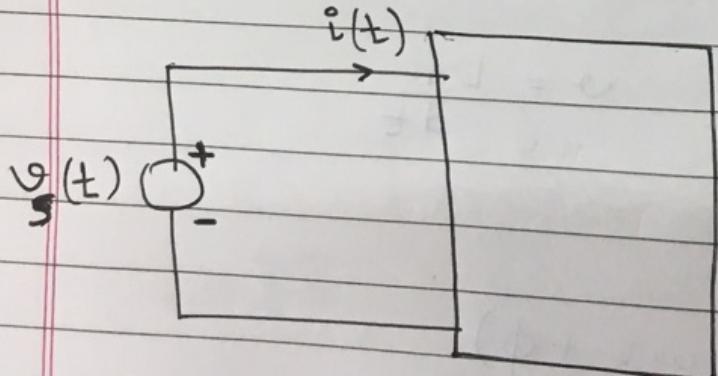


$$Y(j\omega) = \frac{I}{V_s}$$

$$= \frac{1}{Z(j\omega)}$$

$m\theta = -\infty$

Q →

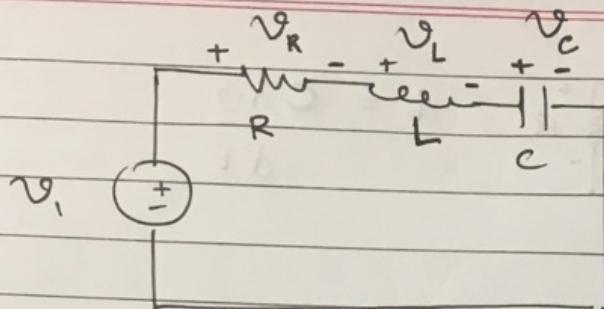

$$V_1 = \cos(\omega t)$$

$$V_1 = 1$$

$$Z(j\omega) = R + j\omega L + \frac{1}{j\omega C}$$

$$I_1 = \frac{V_1}{Z} = \frac{\Phi V_1}{R + j\omega L - \frac{j}{\omega C}}$$

$$i_1(t) = A \cos(\omega t + \Theta_1)$$

$$A = 1$$



$$\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\Theta = -\tan^{-1} \left(\frac{\omega L - 1/\omega C}{R} \right)$$

→ Analogy with Mechanics

SHM


$$m\ddot{\theta} = -\theta$$

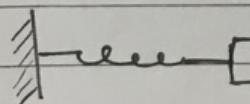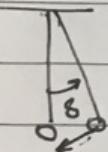

$$m\ddot{x} = -kx$$

$$\left\{ \begin{array}{l} \ddot{x} = -x = \dot{y} \\ y = \dot{x} \\ \dot{x} = y \\ \dot{y} = -x \end{array} \right\}$$


Basic SHM \approx

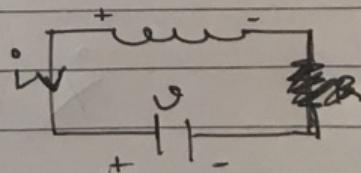

(No R)

$$C = L = R = 1$$

Page

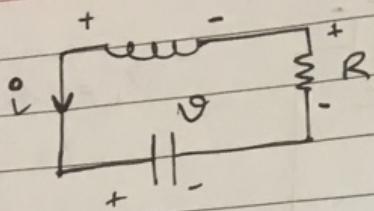

$$i = \frac{C dv}{dt}$$

$$v = -L \frac{di}{dt} - iR$$

$$\frac{dv}{dt} = i$$

$$\frac{di}{dt} = -v - iR$$

} just like
Damped Oscillation

→ Position & Momentum

$$\begin{cases} \dot{x} = y \\ \dot{y} = -x \end{cases} \quad \rightarrow R$$

$- \gamma y$

Damping const.

$$x = \text{position} \quad U(x) = \frac{1}{2} kx^2$$

$$y = \text{momentum}$$

→ Force

$$K(x) = m \frac{\dot{x}^2}{2} = \frac{p^2}{2m}$$

$$H(x, p) = \frac{kx^2}{2} + \frac{p^2}{2m} = \text{const.}$$

$$\dot{x} = \frac{\partial H}{\partial p} = p/m$$

$$\dot{Y} = -\frac{8H}{sX} = -k \cdot X$$

$$\begin{pmatrix} \dot{X} \\ \dot{Y} \end{pmatrix} = \begin{pmatrix} 0 & 1 \\ -1 & -\gamma \end{pmatrix} \begin{pmatrix} X \\ Y \end{pmatrix}$$

$$sX = Y$$

$$sY = -X - \gamma Y$$

$$\dot{X} = Ax \Rightarrow x(t) = e^{At}x(0)$$

$$e^A = I + A + \frac{A^2}{2!} + \dots$$

$$s^2 X = -X - \gamma s X$$

$$s^2 = -1 - \gamma s \Rightarrow s = \frac{-\gamma \pm \sqrt{\gamma^2 - 4}}{2}$$

→ Forced oscillations → Voltage source $v_s(t)$

