

## Simulation Exercise

1. Write ngspice netlist to measure I/V characteristics of RED, YELLOW, BLUE GREEN, and WHITE LED and the diode 1N914.
2. Run the simulation and plot all the characteristics on the same plot. Call this **Plot 1**.
3. Now plot a graph of  $\ln I_D$  v/s  $V_D$  for all the diodes. Call this **Plot 2**. The slope of the graph is given by

$$\frac{\ln I_{D2} - \ln I_{D1}}{V_{D2} - V_{D1}} = \frac{1}{\eta V_T} \quad (1)$$

Calculate the ideality factor  $\eta$  of each diode from the slope. Also calculate the saturation current  $I_S$  from the y-intercept.

4. Calculate the bandgap  $E_g$  for each LED using the emission wavelengths from the Figure showing emission intensity v/s wavelength of various LEDs (refer the labsheet slide no. 4) and putting them in equation (1) from the supporting document. Assume that for silicon(1N914),  $E_g = 1.1$  eV.
5. From **Plot 1**, choose a constant value of  $I_D$ , say 1 mA. For each diode, find out the value of  $V_D$  corresponding to  $I_D = 1$  mA.
6. Now plot a graph of  $V_D$  v/s  $E_g$  for all the diodes. For the chosen value of  $I_D$ , you should get one point ( $V_D, E_g$ ) on the graph for each diode and hence you can plot all five points (for the different diodes) on a single graph.
7. From the graph, try to find a relation between  $V_D$  and  $E_g$ . What is the expected correlation? Do you observe any variation? If yes, why?