

Experiment 1

Name : Devesh Kumar

Batch:Monday

Exp Date:


Name of TA/RA : Arindam Sardar

Roll No:16d070044

Table No:20

Part 1: RC circuits

 1. Input and output waveforms for $R=1k$, $C=1\mu F$, $V_{in} = 10 V_{p-p}$, 50Hz sinusoidal signal.



There is phase shift between v_{in} (ch1) and v_c (ch2)



2. Frequency response

dB v/s log frequency plot

Indicate the axes and scales properly
Show the cut-off frequency

Φ v/s log frequency plot

Frequency	Vc	Vr	Phase(Capacitor)	Phase(Resistor)
50	4.55	0.4	-18.4	70.3
75	4.1	0.9	-27.4	62.1
100	3.5	1.4	-33.1	55.7
250	1.43	3.5	-45	45.2
400	0.67	4.3	-60	29.2
550	0.38	4.6	-74	15.3
700	0.24	4.7	-78	12.1
850	0.16	4.8	-80	9.8
1000	0.11	4.8	-81	8.7
5000	0.005	4.9	-89.9	0.1
10000	0.001	4.9	-89.95	0.05
20000	0	5	-89.7	0.1
50000	0	5	-89.9	0.05

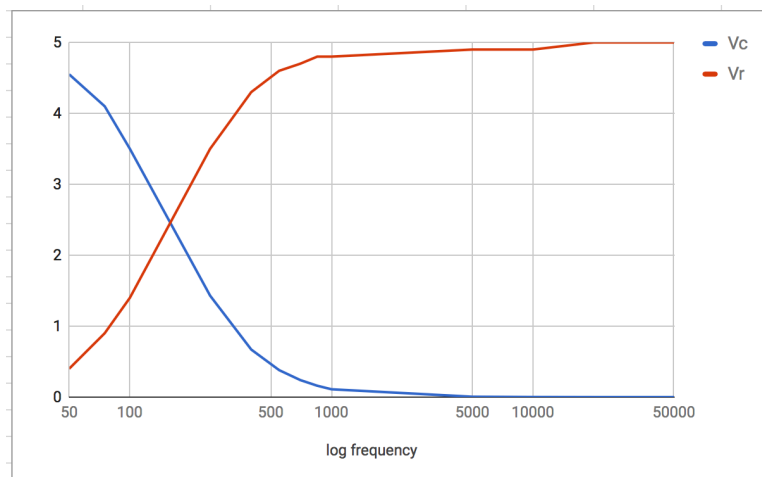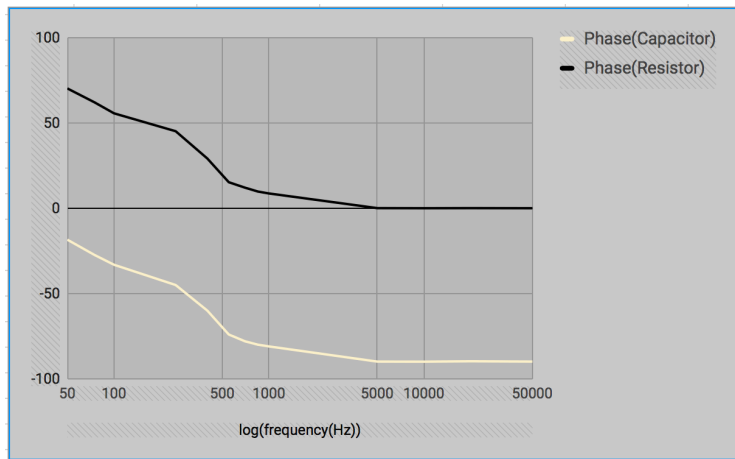


Experiment 1

3. Comment on the plots:


V_p decreases with increase in frequency in both the cases. Thus the sign of v_p in resistor is opposite to that of v_p in capacitor

V_{dp} is directly proportional to frequency in case of resistor. It only allows wave with high frequency to pass through. V_{dp} is inversely promotional to frequency in case of capacitor.

 
4. Response of RC circuit to square wave input: <<Specify R,C and input signal amplitude, and frequency clearly>



5. Effect of varying frequency on the output voltage :

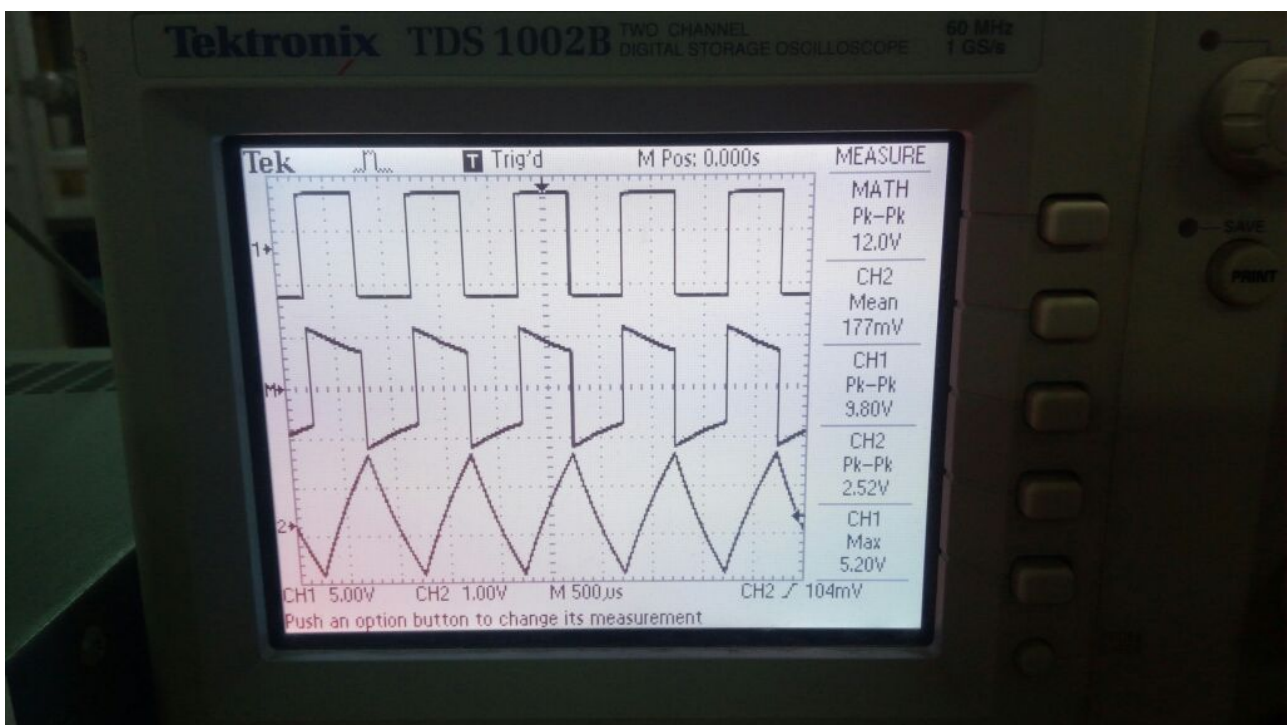


Experiment 1

 


V out through capacitor (f 1000hz).as frequency increases capacitor gets less time accumulate charge so it takes more time to reach v_{in} . If frequency is low then capacitor to is max value .

6. Response of RC circuit to square wave input with DC offset: <<Specify R,C and input signal amplitude, offset, and frequency clearly>>

 


Experiment 1

8. Effect of varying frequency on the output voltage

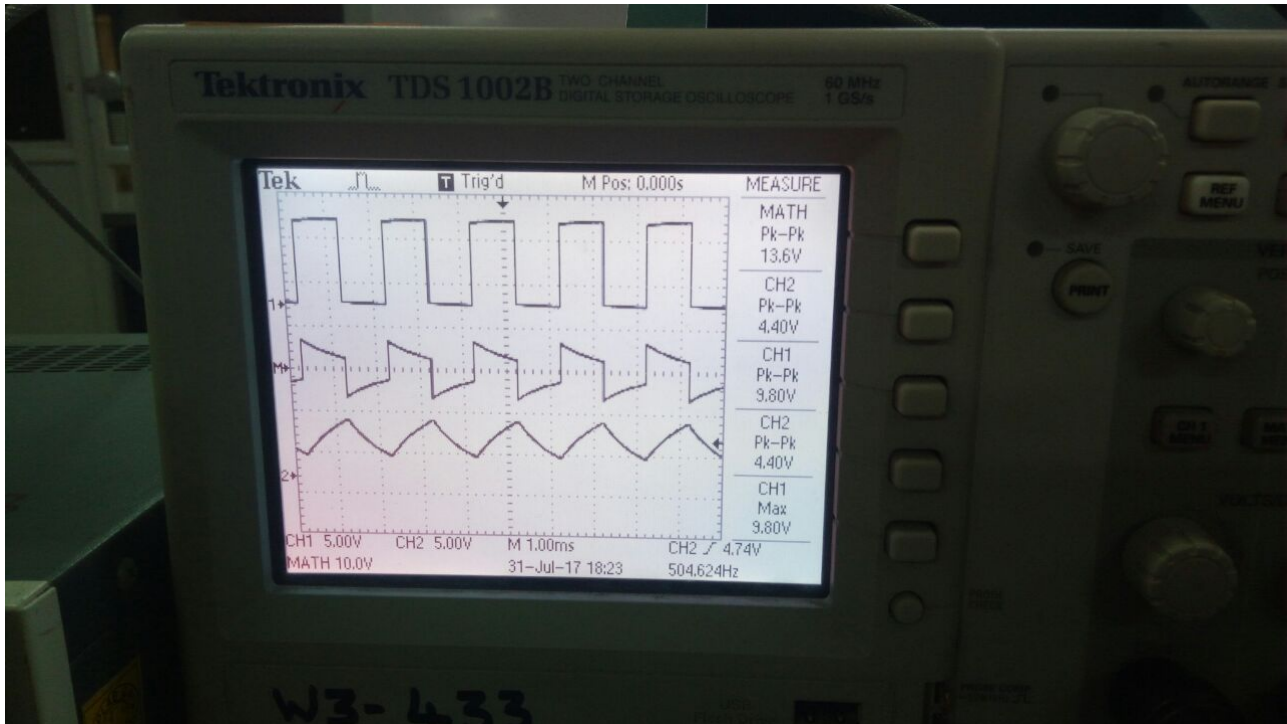

Experiment 1

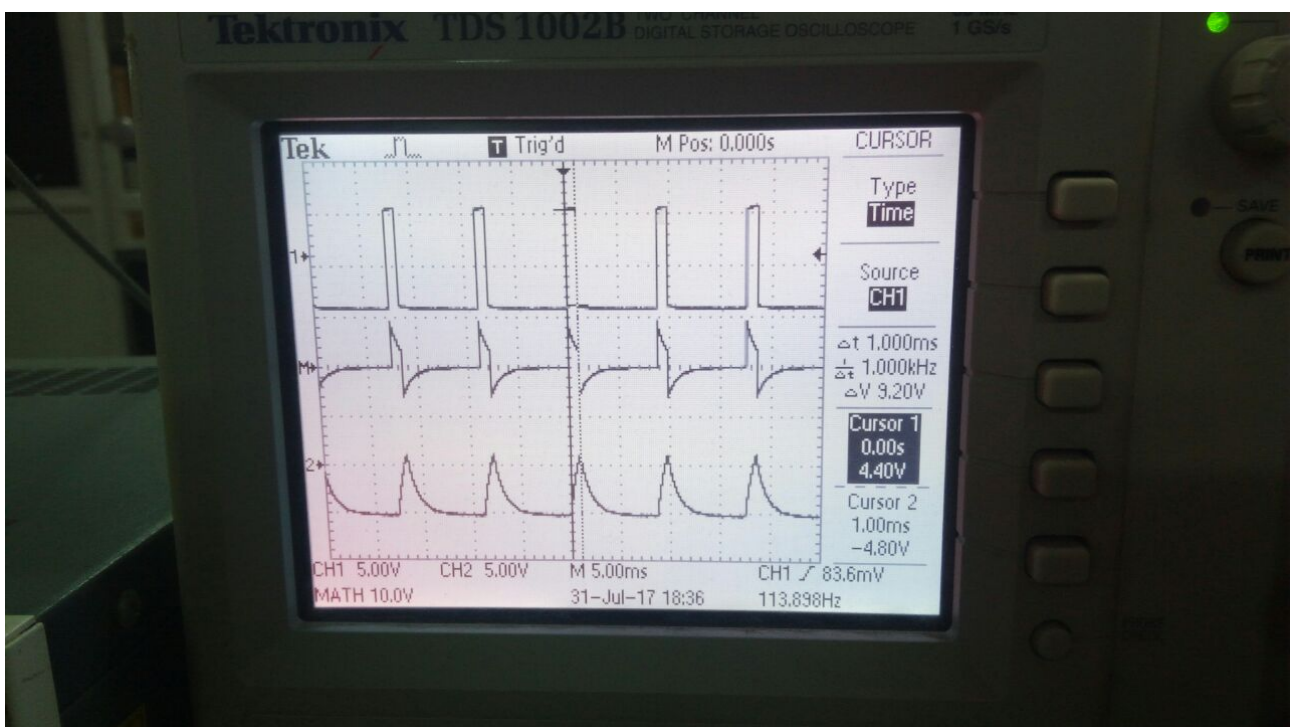9. Change the duty cycle of the input voltage to 10 % and observe the input output waveforms.




In all the graph ch1 is v_{in} , ch 2 is v across capacitor, $m=V_{in}-V_c$ i.e voltage across resistor


Experiment 1

PART 2: RECTIFIER

 1. Connect the half wave rectifier circuit shown in Fig.1. Observe the input and output waveforms for $V_s = 10V_{pp}$, 500Hz sinusoidal signal, $R_L = 1K$ and for 1N914 diode.



2. Now connect a capacitor of $4.7 \mu F$ across the load resistor R_L . Observe the input and output voltage waveform.

 

Experiment 1

3. Comment on these waveforms.

When v_{in} is positive, diode conducts in normal way. As v_{in} decreases the capacitor must discharge with time constant $\tau = RC$. Thus it discharges slowly as we increase R or C .

When v_{out} equal to v_{in} then conduction happens again and capacitor charges



4. Vary the value of capacitor to $10\mu F$, $47\mu F$, and $100\mu F$ and observe the effect.

Repeat for $R_L = 10K$. Tabulate the readings in each case to estimate the ripple factor in Table 1 below.

Note: V_{R-PP} is peak-to-peak value of ripple voltage.

R_L	C	V_{rpp}	V_{dc}	r
1	4.7	1.28	2.8	0.1344537815
1	10	0.72	2.98	0.07106198184
1	47	0.16	3	0.01568627451
10	4.7	0.4	3.93	0.02993563838
10	10	0.16	3.94	0.01194386384

Experiment 1

  

Experiment 1

PART 3:CE AMPLIFIER

1. Wire up the circuit. Make sure that C_B , C_C , C_E are sufficiently large for the signal frequency of 5 kHz to be in the mid-band region.

$$R_e = 2k\ \text{ohm} \quad R_c = 3k\ \text{ohm} \quad R_1 = 27k\ \text{ohm}$$

2. Wire up the circuit. Make sure that C_B , C_C , C_E are sufficiently large for the signal frequency of 5 kHz to be in the mid-band region.

$$C_b = C_c = C_e = 47\mu\text{F}$$

3. Calculate A_{VL} , A_{V0} , R_i , R_o for your design


$$A_{vL} = -g_m (R_c \parallel R_L) = -30$$

$$A_{v0} = -g_m (R_c) = -120$$


$$R_{in} = r_{\pi} \parallel R_1 \parallel R_2 = 4.6k\ \text{ohm}$$

$$R_{out} = R_c \parallel R_L = 750\ \text{ohm}$$

 4. Check your calculations against measurements made with a signal frequency of 5 kHz (use oscilloscope, not multi-meter). Keep the input voltage sufficiently small so as to give an undistorted output. A voltage divider (with 1 k Ω and 47 Ω , for example) may be used.




- 5 Increase the input amplitude to a point where you begin to see some distortion at the output. Note this amplitude.

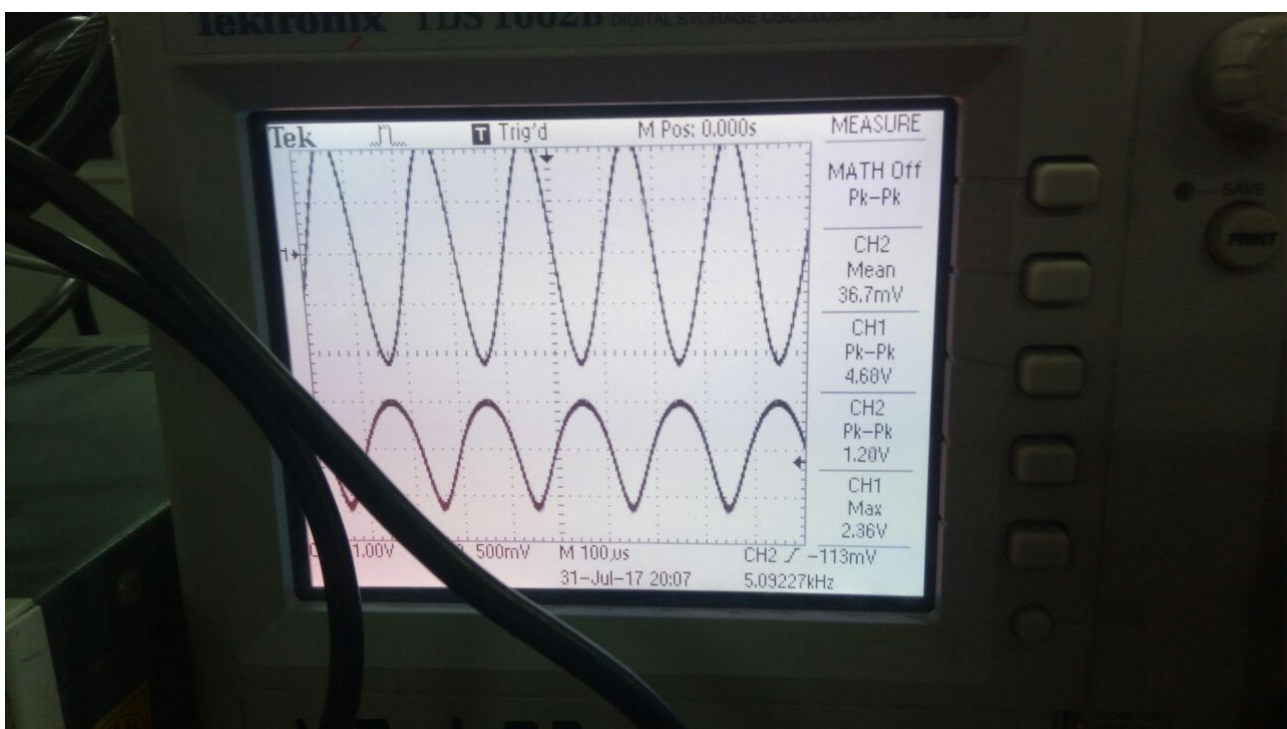

Experiment 1

6.

frequency	log(frequency)	Vin(p-p) in mV	Vout(p-p) in mV	gain	vdb
100	2	20	250	12.5	-12.04119983
1000	3	20	500	25	-6.020599913
5000	3.698970004	20	520	26	-5.679933127
10000	4	20	515	25.75	-5.763855419
50000	4.698970004	20	520	26	-5.679933127
100000	5	20	520	26	-5.679933127
500000	5.698970004	20	360	18	-8.873949985
700000	5.84509804	20	300	15	-10.45757491
1000000	6	20	280	14	-11.05683937

 

Experiment 1

- 7 Partially bypassed R_E : Replace R_E with R_{E1} and R_{E2} (see figure), keeping the other component values the same as before. Select R_{E1} and R_{E2} to obtain approximately the same bias point (as the CE amplifier) and a gain of about 10.

$$R_{E1} = 40 \text{ ohm and } R_{E2} = 1.5k \text{ ohm}$$

- 8 Calculate A_{VL} , A_{VO} , R_i , R_o for your design.

$$A_{VL} = 10.1 \quad A_{VO} = 64 \quad R_i = 36k \quad R_o = 3k$$


- 9 Wire up the amplifier and repeat the measurements you made for the CE amplifier.

Gain in Partial bypass CE-Amplifier is less

10. Plot the frequency response of the two amplifiers on the same graph (log-log plot) and comment on the salient features you observe.

frequency	log(frequency)	Vin(p-p) in mV	Vout(p-p) in mV	gain	vdb
100	2	20	150	7.5	-16.47817482
1000	3	20	186	9.3	-14.60974112
5000	3.698970004	20	186	9.3	-14.60974112
10000	4	20	186	9.3	-14.60974112
50000	4.698970004	20	190	9.5	-14.42492798
100000	5	20	170	8.5	-15.39102157
500000	5.698970004	20	150	7.5	-16.47817482
1000000	6	20	130	6.5	-17.72113295

|gain|

 

Experiment 1