

1. Design a counter which goes through the sequence

$$000 \rightarrow 010 \rightarrow 100 \rightarrow 001 \rightarrow 011 \rightarrow 101 \rightarrow 111$$

2. Design a 2 bit multiplier ckt using (a) combinational circuit, (b) sequential circuit (using a shift register).

3. Design a ckt which divides the CP by n . ^{2 I/P}

4. Design a XOR gate using minimum number of NAND gates.

5. The following Boolean expression $BE + \overline{B} \overline{D} \overline{E}$ is a simplified version of the Expression

$$\overline{A}BE + BC\overline{D}E + B\overline{C}\overline{D}E + \overline{A}\overline{B}\overline{D}\overline{E} + \overline{B}\overline{C}\overline{D}\overline{E}.$$

Are there any don't care conditions? If so, what are they?


6. With the use of maps, find the simplest form in sum of products of the function $F = fg$, where f and g are given by

$$f = w\overline{x}\overline{y} + \overline{y}z + \overline{w}y\overline{z} + \overline{x}y\overline{z}$$

$$g = (w+x\overline{y}+z) (\overline{x}+\overline{y}+z) (\overline{w}+\overline{x}+\overline{z})$$

7. There are two channels in a communication system. The incoming bit streams are $A_0 A_1 A_2 A_3 \dots A_n$ and $B_0 B_1 B_2 B_3 \dots B_n$. Design a ckt such that the o/p sequence from the ckt is $A_0 B_0 A_1 B_1 A_2 A_3 \dots A_n B_n$.

8. A seven segment LED display is shown below.

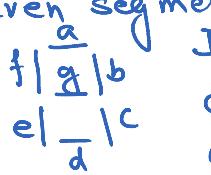 Design a combination of sequential and combinational ckt such that the LED display counts from 0 to 9 and then back to 0.

9. Implement Boolean functions using decoders, multiplexers, ROM, PLA etc.

10. Obtain an 8×1 multiplexer with a dual 4-line to 1-line multiplexer having separate enable inputs but common selection lines. Use a block diagram construction.

11. Design a 4 bit shift register such that when an input $x=0$, it loads an external input at the next CP and when $x=1$, it shifts the content of the register to the right inserting 0 in the MSB.

12. Think of practical real problem and then try to find a solution using digital circuits.