


Digital Electronics

(EE221)

Lecture - 2

Boolean Operations

- Single variable operation
 - NOT

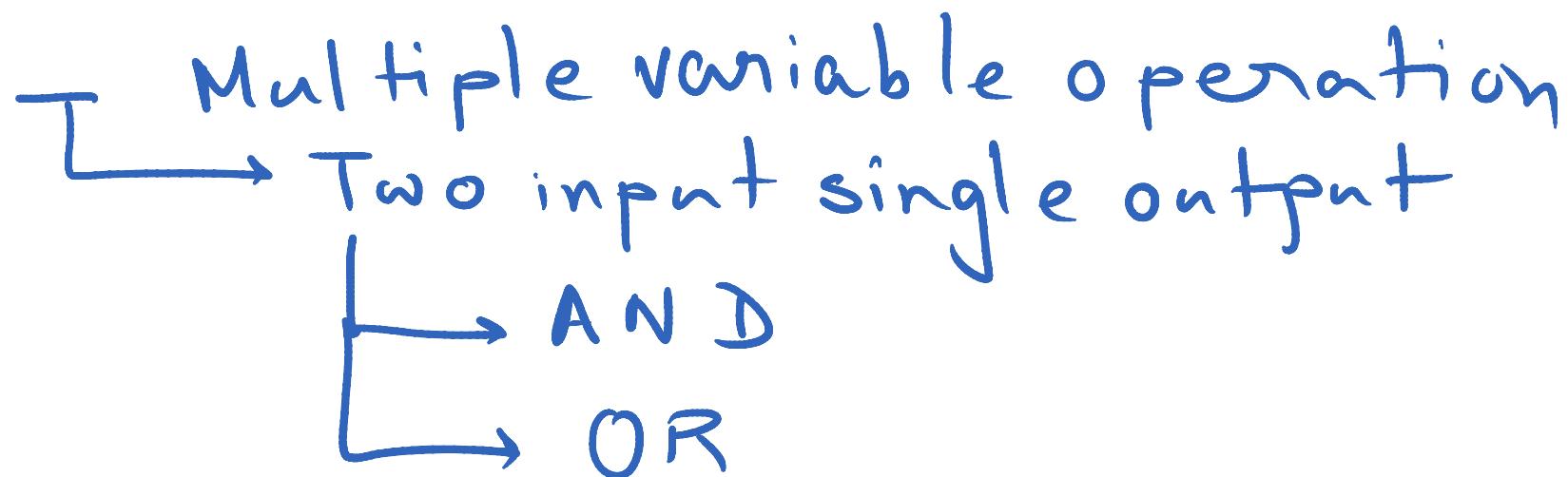

NOT, AND, OR → Fundamental to Boolean Algebra.

Variable and Signals

Variable → Binary variable

↳ '0' or '1'

↳ High or Low

Variable → Mathematical/Logical representation of an electrical signal

Example -

$0-2.5 \rightarrow$ Logical '0' / Low

$2.5-5.0 \rightarrow$ logical '1' / high

Variables and Signals

Variables are represented in letters - A, B, C

Variables can take only two values
- '0' or '1'.

Any operation on variable(s) will finally lead to '0' or '1'.

We will mostly talk about variables.

NOTE: Variable state is measured through electrical voltage and current values

NOT Operation


Representation -

$$\text{NOT}(A) \Leftrightarrow \bar{A}$$

Logic symbol -



VENN Diagram

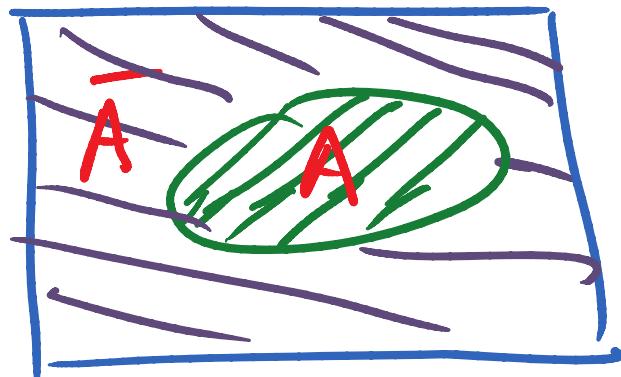

NOT \Leftrightarrow Inversion

Implemented through
inverter circuit.

$$A=0, \bar{A}=1$$

$$A=1, \bar{A}=0$$


TRUTH TABLE

{All possible inputs}

| A | B | C | D | ... | Output 1 | Output 2 | ... |
|---|---|---|---|-----|----------|----------|-----|
| 0 | 0 | 0 | 0 | ... | 1 | 1 | ... |
| 0 | 0 | 0 | 1 | ... | 0 | 1 | ... |


TRUTH TABLE for NOT gate -

| A | \bar{A} |
|---|-----------|
| 0 | 1 |
| 1 | 0 |

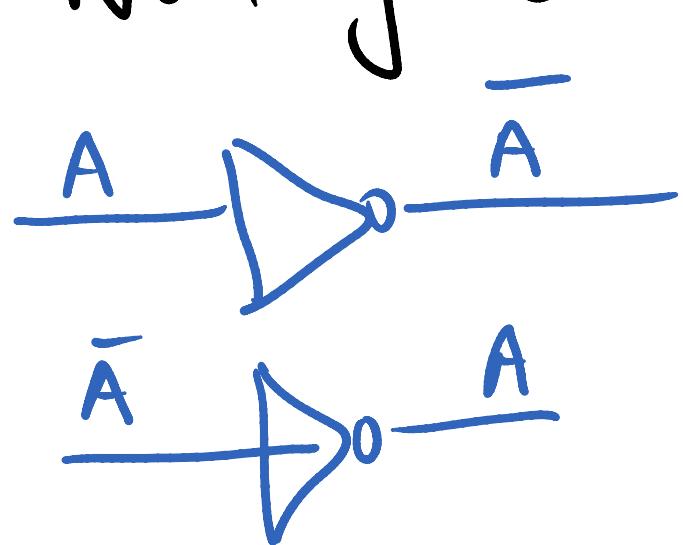


Buffer Gate

- * Symbol -

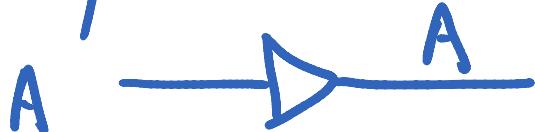


* Will be discussed later

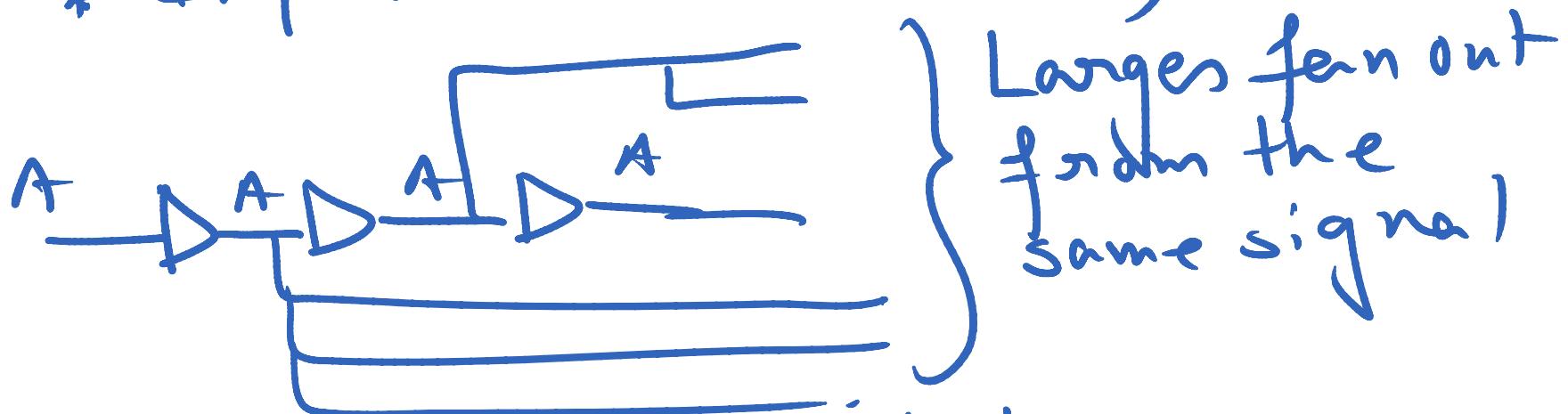- * Improves signal level strength
- * Improves noise immunity



- * Actual Implementation

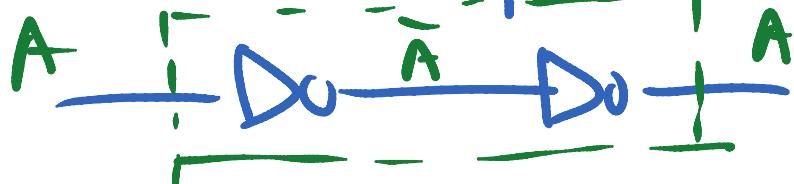


AND Operation

Representation —

$$\text{AND}(AB) = A \cdot B = AB$$


Symbol —

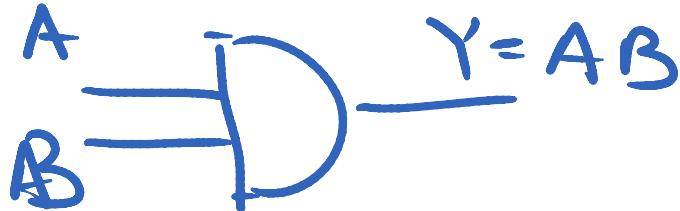

Truth table —

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

VENN Diagram —

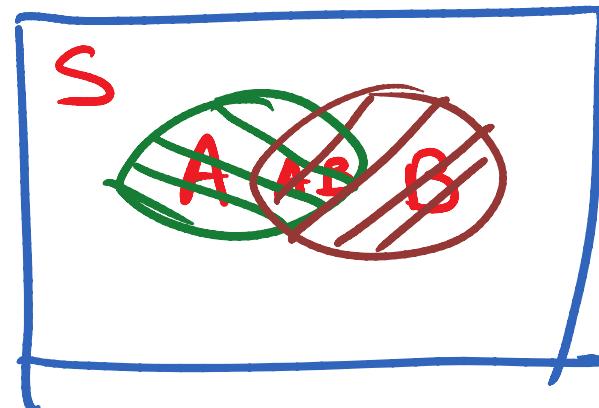

$$\begin{aligned} Y &= AB \\ Y &= \overline{\overline{A}} \overline{\overline{B}} + \overline{A} \overline{B} + A \overline{B} \\ Y &= \overline{\overline{A}} \overline{\overline{B}} + \overline{A} \overline{B} + A \overline{B} \end{aligned}$$

Multiple Input AND operation.


| A | B | C | | Y | |
|---|---|---|--|---|----------------|
| 0 | 0 | 0 | | 0 | 2^N Number |
| 0 | 0 | 1 | | 0 | of combination |
| 0 | 1 | 0 | | 0 | for N variable |
| 0 | 1 | 1 | | 0 | input . |
| 1 | 0 | 0 | | 0 | $Y = ABC$ |
| 1 | 0 | 1 | | 0 | |
| 1 | 1 | 0 | | 0 | |
| 1 | 1 | 1 | | 1 | |

OR Gate

- Representation

$$\text{OR } (AB) = A + B$$

- Symbol

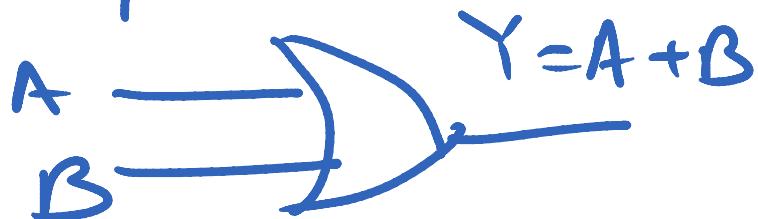


- Truth Table

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

$$Y = A + B$$
$$\bar{Y} = \bar{A} \bar{B}$$

VENN Diagram

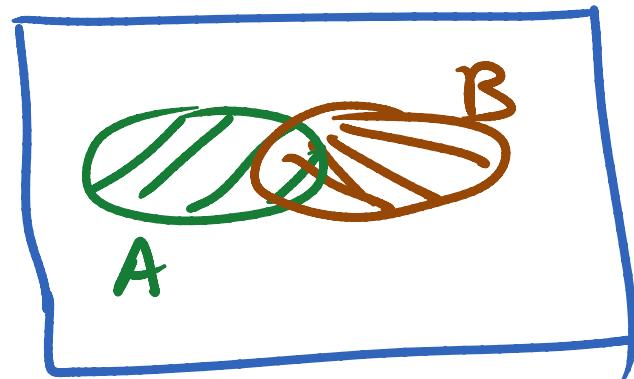

Identity Operation

By Definition -

$$A + A = 1, A + 0 = A$$

| A | \bar{A} | Y | $A+1=1$ |
|---|-----------|---|---------|
| 0 | 1 | 1 | |
| 1 | 0 | 1 | |

$$\bar{A}$$




$$A \cdot \bar{A} = 0, A \cdot 0 = 0$$

| A | \bar{A} | Y | $A \cdot 0 = A$ |
|---|-----------|---|-----------------|
| 0 | 1 | 0 | |
| 1 | 0 | 0 | |


$$\bar{A}$$



AND and OR

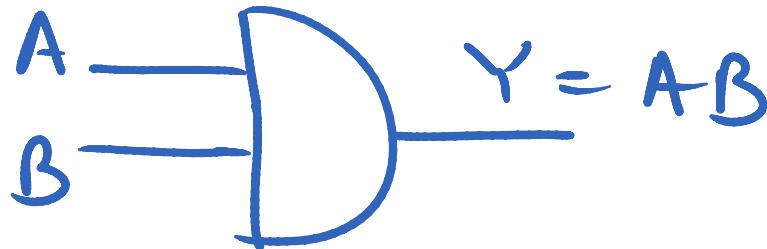

$$\bar{Y} = \overline{AB}$$

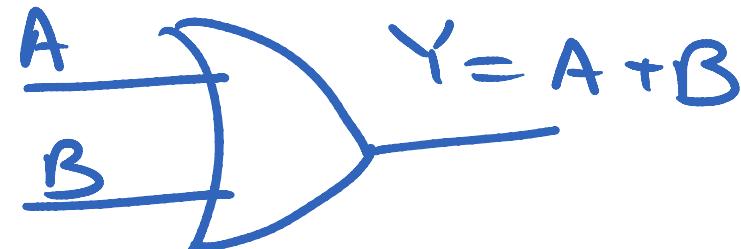

$$\bar{Y} = \overline{A+B}$$

$$\bar{Y} = \overline{\overline{A}\overline{B}} + \overline{A}\overline{B} + \overline{A}\overline{B}$$

$$= \overline{\overline{A}\overline{B}}$$

$$\overline{A+B} = \overline{\overline{A}\cdot\overline{B}}$$

Any operation/function can be implemented in its regular form or dual form

Postulates for Algebraic Structure

1) Closure -

A set S is closed w.r.t a binary operator if for every pair of elements in S , the binary operator specifies a rule for obtaining a unique element in S .

2) Associative Law -

$$(x * y) * z = x * (y * z), x, y, z \in S$$

3) Commutative Law -

$$x * y = y * x \quad \forall x, y \in S$$

4) Identity element -

$$e * x = x * e = x, \quad \forall x \in S$$

5) Inverse -

$$x * y = e, \quad \forall x, y \in S$$

6) Distributive Law -

$$x * (y * z) = (x * y) * (y * z)$$

Huntington Postulates (1904)

George Boole (1854) - Boolean Algebra

- 1) Closure w.r.t the operators +
closure w.r.t the operator .
- 2) Identity element w.r.t +,
 $0+x = x+0 = x$
Identity element w.r.t $\bar{\cdot}$:
 $1 \cdot x = x \cdot 1 = x$
- 3) Commutative, $x+y = y+x$
 $x \cdot y = y \cdot x$
- 4) \therefore distributive over + $x \cdot (y+z) = x \cdot y + x \cdot z$
'+' distributive over \cdot : $x+(y \cdot z) = (x+y) \cdot (x+z)$

5) Associative -

$$x + (y + z) = \underline{(x + y)} + z$$

$$x \cdot (y \cdot z) = \underline{(x \cdot y)} \cdot z$$

6) Inverse ,

$$x + \bar{x} = 1$$

$$x \cdot \bar{x} = 0$$

Two valued Boolean algebra
having a set of two elements
1 and 0, two binary operators with
operation rules AND and OR, and
a complement operator NOT.

Duality Principle

- Huntington postulates have been listed pairs
- One part is obtained if the binary operator and identity elements are interchanged

Basic Theorems

$$P \quad x + 0 = x$$

$$x \cdot 1 = x$$

$$P \quad x + \bar{x} = 1$$

$$x \cdot \bar{x} = 0$$

$$T \quad x + x = x$$

$$x \cdot x = x$$

$$T \quad \frac{x+1}{(\bar{x})} = 1$$

$$x \cdot 0 = x$$

$$T \quad (\bar{x}) = x$$

$$P \quad x + y = y + x$$

$$x \cdot y = y \cdot x$$

$$P \quad (x+y) + z = (x+y) + z$$

$$(x \cdot y) \cdot z = x \cdot (y \cdot z)$$

$$P \quad x \cdot (y+z) = x \cdot y + x \cdot z$$

$$x + y \cdot z = (x+y) \cdot (x+z)$$

$$T \quad \frac{(x+y)}{x+y} = \frac{\bar{x}}{x} \frac{\bar{y}}{y}$$

$$\frac{x \cdot y}{x \cdot (x+y)} = \frac{\bar{x}}{x} + \frac{\bar{y}}{y}$$

Proof of the Theorems

$$\begin{aligned}x+x &= (x+x) \cdot 1 \\&= (x+x) \cdot (x+\bar{x}) \\&= x + x \cdot \bar{x} \\&= x + 0 \\&= x\end{aligned}$$


$$x \cdot x = x \quad [\text{By duality}]$$

Proof of the Theorems

$$\begin{aligned} x+1 &= 1 \cdot (x+1) \\ &= (x+\bar{x}) (x+1) \\ &= x + \bar{x} \cdot 1 \\ &= x + \bar{x} \\ &= 1 \quad [\text{By duality}] \\ x \cdot 0 &= 0 \end{aligned}$$

De Morgan's Law -
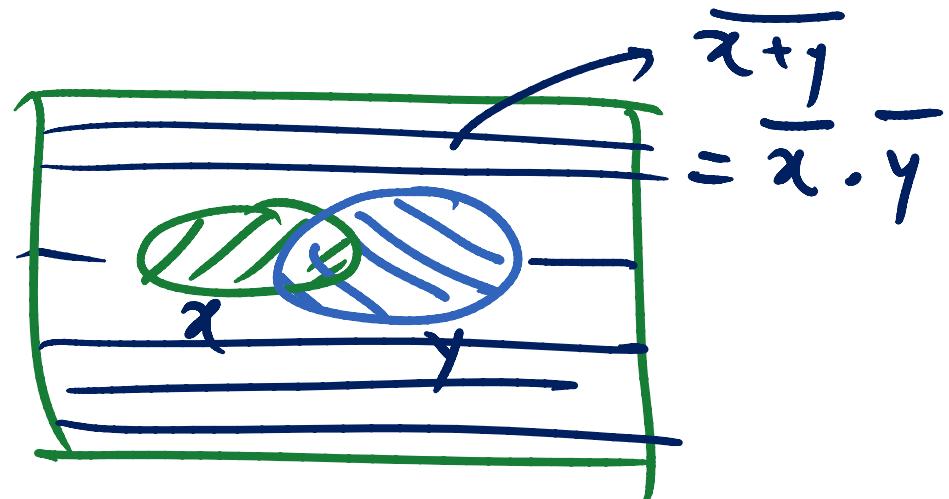
$$\overline{x+y} = \overline{x} \cdot \overline{y}$$



| $x \ y$ | $x+y$ | $\overline{x+y}$ | \bar{x} | \bar{y} | $\bar{x}\bar{y}$ |
|---------|-------|------------------|-----------|-----------|------------------|
| 0 0 | 0 | 1 | 1 | 1 | 1 |
| 0 1 | 1 | 0 | 1 | 0 | 0 |
| 1 1 | 1 | 0 | 0 | 0 | 0 |
| 1 0 | - | 0 | 0 | 1 | 0 |

$$\overline{x \cdot y} = \overline{x} + \overline{y} \quad [\text{By Duality}]$$

Boolean Functions

* An expression formed with binary variables

$$F_1 = xy + \bar{x}yz + \bar{y}z$$

$$F_2 = xy + yz + zx$$

$$F_3 = ABCD + A\bar{B} + C\bar{D} + A\bar{C}$$

⋮


Truth Table

Any Boolean function can be represented in truth table.


| x | y | z | | F_1 | F_2 | F_3 |
|------------------------------|---------------------------------------|---|------|-------|-------|-------|
| All Possible combinations | values of the function (0,1) | | | . | . | 1 |
| | | | | . | . | 1 |
| | | | | . | . | 1 |
| | | | | 1 | | |

Implementation of Boolean function using Logic gates -

$$F_1 = x \bar{y} z$$

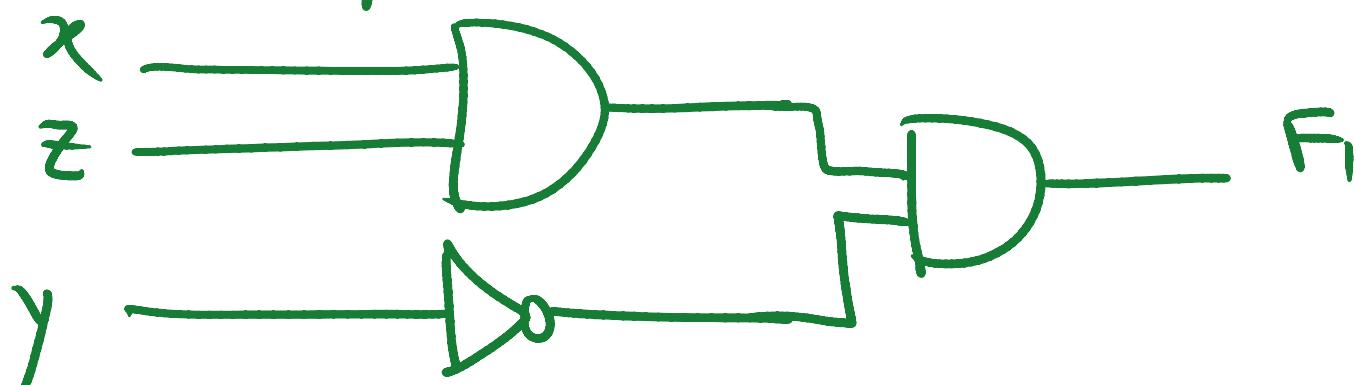

$$F_2 = x \bar{y} + \bar{x} \bar{y}$$

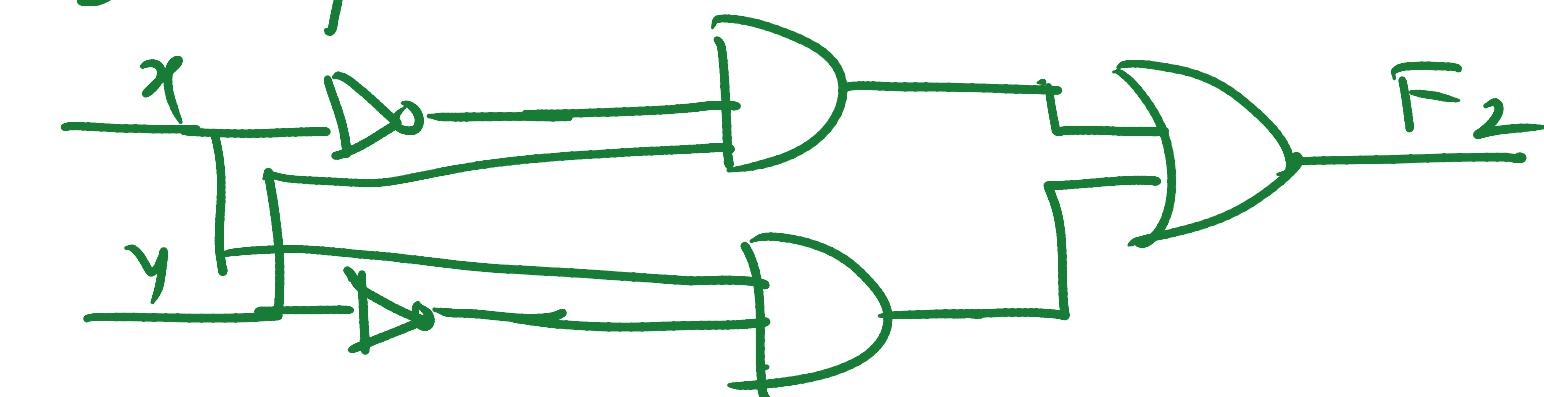

Minimization of Boolean function

- Minimize the Boolean function for less costly hardware implementation
- Simplified implementation

$$\begin{aligned} F &= \bar{x}\bar{y}z + \bar{x}yz + xy\bar{z} \\ &= \bar{x}z(\bar{y} + y) + xy\bar{z} \\ &= \bar{x}z + xy \quad \left[\text{Trial approach} \right] \end{aligned}$$

Complement of a Function -

$$\overline{A+B+C} = \bar{A}\bar{B}\bar{C}$$

$$\overline{A \cdot B \cdot C} = \bar{A} + \bar{B} + \bar{C}$$

- (i) Take the dual of the function
- (ii) Complement each literal

$$F_1 = \bar{x}y\bar{z} + \bar{x}\bar{y}z$$

$$\text{Dual } (F_1) = (\bar{x} + y + \bar{z}) \cdot (\bar{x} + \bar{y} + z)$$

$$\overline{F_1} = (x + \bar{y} + z) \cdot (x + y + \bar{z})$$

Dual of a function

$$F_2 = x(\bar{y}\bar{z} + yz)$$

$$\text{Dual}(F_2) = x + (\bar{y} + \bar{z}) \cdot (y + z)$$

$$\bar{F}_2 = \bar{x} + (y + z)(\bar{y} + \bar{z})$$

Any function can be implemented
in its regular form or its
complement form

Canonical and Standard Forms —

| x | y | z | Min Term | Designation |
|-----|-----|-----|-------------------------|-------------|
| 0 | 0 | 0 | $\bar{x}\bar{y}\bar{z}$ | m_0 |
| 0 | 0 | 1 | $\bar{x}\bar{y}z$ | m_1 |
| 0 | 1 | 0 | $\bar{x}y\bar{z}$ | m_2 |
| 0 | 1 | 1 | $\bar{x}yz$ | m_3 |
| 1 | 0 | 0 | $xy\bar{z}$ | m_4 |
| 1 | 0 | 1 | xyz | m_5 |
| 1 | 1 | 0 | $\bar{x}yz$ | m_6 |
| 1 | 1 | 1 | xyz | m_7 |

Any Boolean function can be represented as sum of min terms.

Canonical and Standard Forms

$$\begin{aligned}F_1 &= A + \overline{B} C \\&= A(B + \overline{B}) + (A + \overline{A})\overline{B}C \\&= AB(C + \overline{C}) + A\overline{B}(C + \overline{C}) \\&\quad + A\overline{B}C + \overline{A}\overline{B}C \\&= ABC + AB\overline{C} + A\overline{B}C + A\overline{B}\overline{C} \\&\quad + A\overline{B}C + \overline{A}\overline{B}C \\&= m_7 + m_6 + m_5 + m_4 \\&\quad + m_1\end{aligned}$$

Canonical and Standard Forms

| x | y | z | Max term | Designation |
|-----|-----|-----|---------------------------|-------------|
| 0 | 0 | 0 | $x+y+z$ | M_0 |
| 0 | 0 | 1 | $x+y+\bar{z}$ | M_1 |
| 0 | 1 | 0 | $\bar{x}+y+z$ | M_2 |
| 0 | 1 | 1 | $\bar{x}+y+\bar{z}$ | M_3 |
| 1 | 0 | 0 | $\bar{x}+y+z$ | M_4 |
| 1 | 0 | 1 | $\bar{x}+y+\bar{z}$ | M_5 |
| 1 | 1 | 0 | $\bar{x}+\bar{y}+z$ | M_6 |
| 1 | 1 | 1 | $\bar{x}+\bar{y}+\bar{z}$ | M_7 |

Implementation through product of Max terms.

Canonical and Standard Forms

$$\begin{aligned} F &= xy + \bar{x} z \\ &= (\underline{xy + \bar{x}}) (\underline{xy + z}) \\ &= (\underline{x + \bar{x}}) (\underline{y + \bar{x}}) \cdot (\underline{x + z}) (\underline{y + z}) \\ &= (\underline{\bar{x} + y}) (\underline{x + z}) (\underline{y + z}) \\ &= (\underline{\bar{x} + y + z\bar{z}}) (\underline{x + z + y\bar{y}}) (\underline{y + z + z\bar{z}}) \\ &= (\underline{x + y + z}) (\underline{x + \bar{y} + z}) (\underline{\bar{x} + y + z}) \\ &= M_0 \underline{M_2} M_4 M_5 \end{aligned}$$

Canonical Forms -

* Any function can be implemented either as sum of minterms or product of maxterms

$$F(A, B, C) = \sum (1, 2, 7, 8)$$

$$F(x, y, z) = \overline{\prod} (2, 6, 7)$$

Conversion Between Canonical Forms -

$$\bar{m}_j = M_j$$

$$F = \sum(0, 2, 4, 5)$$




$$\Rightarrow \bar{F} = \sum(1, 3, 6, 7)$$

$$\Rightarrow F = \prod(1, 3, 6, 7)$$


Sum of Min terms \rightarrow AND-OR Implementation


Product of Maxterms \rightarrow OR-AND Implementation

Basic Logic Family -

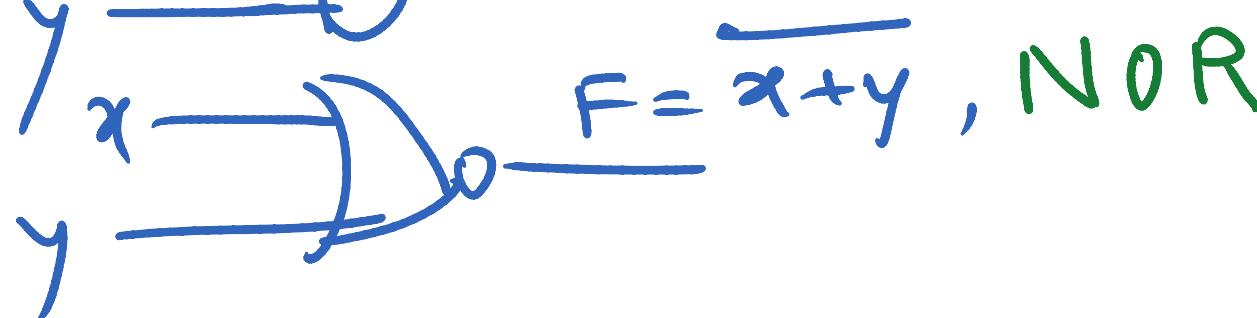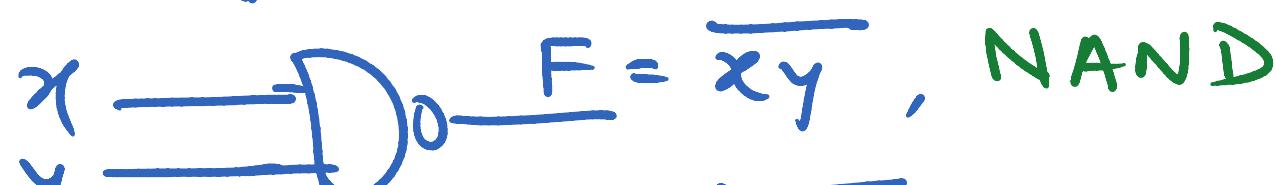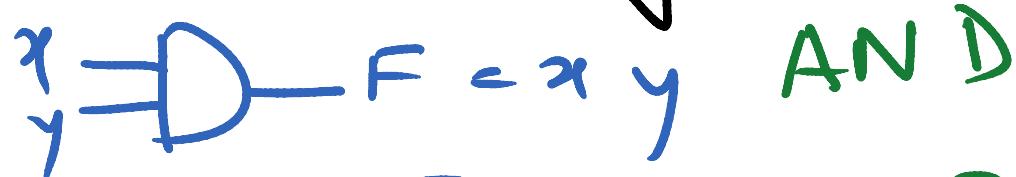

Basic Logic Families -

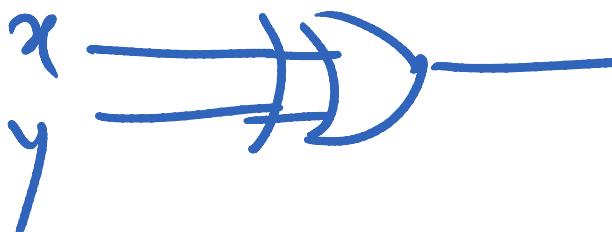
$$F = x\bar{y} + \bar{x}y \text{ Exclusive OR}$$
$$= x \oplus y$$

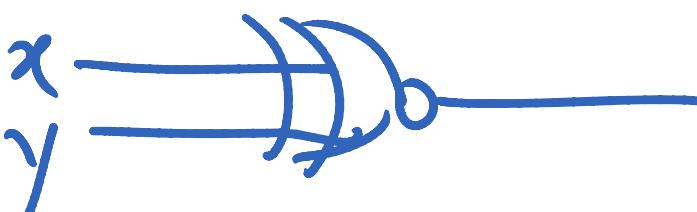
$$F = xy + \bar{x}\bar{y} \text{ Exclusive NOR}$$
$$= x \ominus y$$

- NAND and NOR gates are called universal gates
- Minimum number of such gates are to be used for implementation

Reference —

Digital Logic and Computer
Design - M. Morris Mano ,
PHI India
ISBN - 81 - 203 - 0417 - 9