

# Lecture 11

## Digital Circuits (I)

### THE INVERTER

#### Outline


- Introduction to digital circuits
  - The inverter
- NMOS inverter with resistor pull-up

#### **Reading Assignment:**

Howe and Sodini; Chapter 5, Sections 5.1-5.3
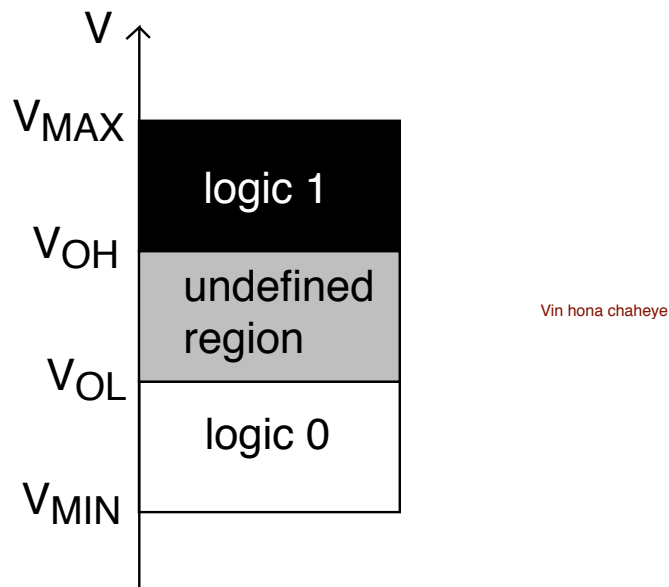
# 1. Introduction to digital circuits: the inverter

In digital circuits, digitally-encoded information is represented by means of two distinct voltage ranges:




## The Static Definition

- **Logic 0:**  $V_{MIN} \leq V \leq V_{OL}$
- **Logic 1:**  $V_{OH} \leq V \leq V_{MAX}$
- **Undefined logic value:**  $V_{OL} \leq V \leq V_{OH}$


Logic operations are performed using *logic gates*.

Simplest logic operation of all: *inversion*  $\Rightarrow$  inverter

# Ideal inverter

 

 Circuit representation and ideal transfer function:




Define *switching point* or *logic threshold* :

- $V_M \equiv$  input voltage for which  $V_{OUT} = V_{IN}$ 
  - For  $0 \leq V_{IN} < V_M \Rightarrow V_{OUT} = V^+$
  - For  $V_M < V_{IN} \leq V^+ \Rightarrow V_{OUT} = 0$

Ideal inverter returns well defined logical outputs (0 or  $V^+$ ) even in the presence of considerable noise in  $V_{IN}$  (from voltage spikes, crosstalk, etc.)

$\Rightarrow$  signal is *regenerated*!


## “Real” inverter

 

In a real inverter, valid logic levels defined as follows:

- Logic 0:
  - $V_{MIN} \equiv$  output voltage for which  $V_{IN} = V^+$
  - $V_{OL} \equiv$  smallest output voltage where slope = -1
- Logic 1:
  - $V_{OH} \equiv$  largest output voltage where slope = -1
  - $V_{MAX} \equiv$  output voltage for which  $V_{IN} = 0$

Two other important voltages:

 

**Define:**


$V_{IL} \equiv$  smallest input voltage where slope = -1

$V_{IH} \equiv$  highest input voltage where slope = -1

If range of output values  $V_{OL}$  to  $V_{OH}$  is *wider* than the range of input values  $V_{IL}$  to  $V_{IH}$ , then the inverter exhibits some noise immunity. ( $|Voltage\ gain| > 1$ )

Quantify this through *noise margins*.

## Chain of two inverters:

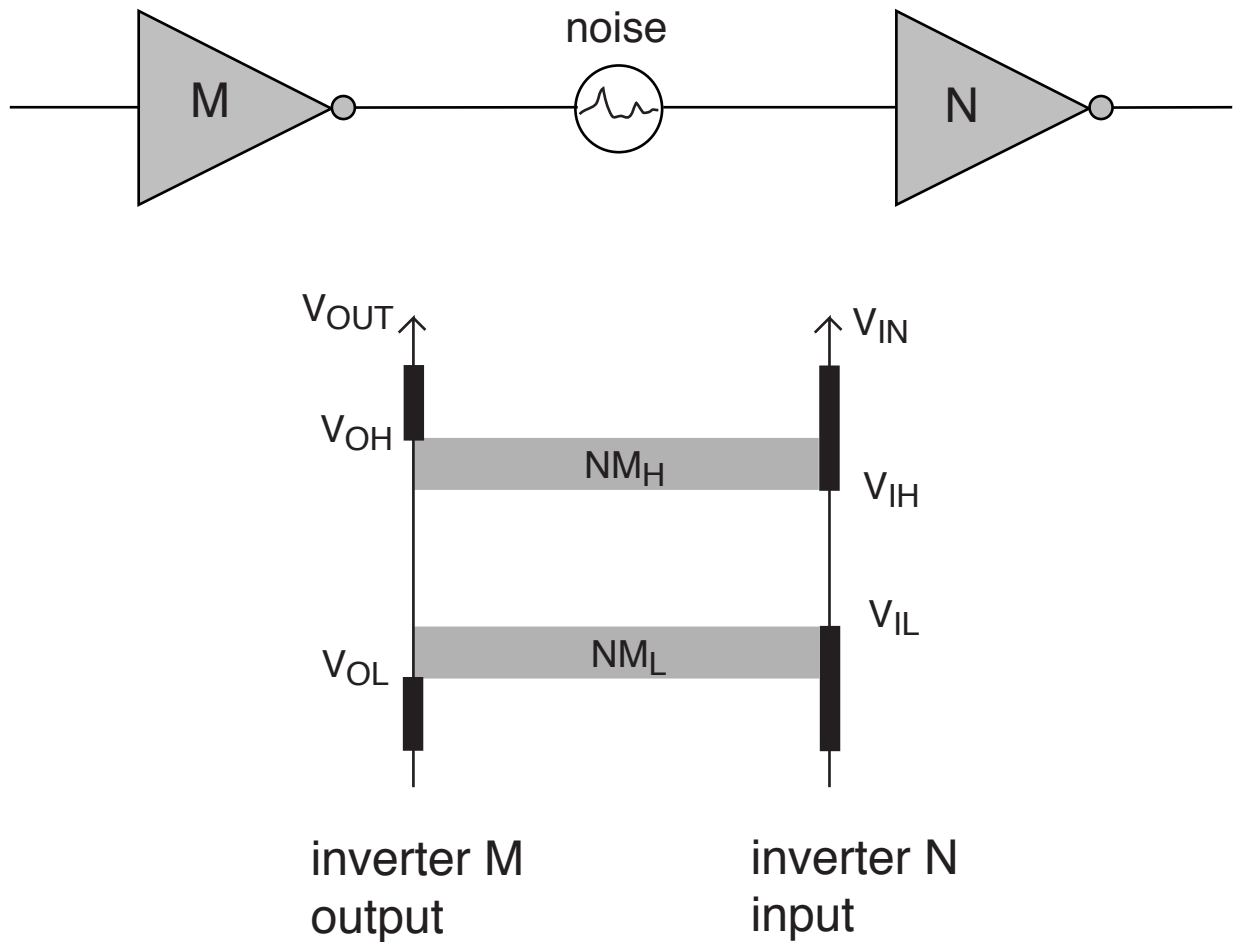

Define *noise margins*:

$$NM_H \equiv V_{OH} - V_{IH}$$

$$NM_L \equiv V_{IL} - V_{OL}$$


noise margin high

noise margin low

## Simplifications for hand calculations: Logic levels and noise margins

It is hard to compute points in transfer function with slope = -1.


Approximate in the following way:

 

- Assume  $V_{OL} \approx V_{MIN}$  and  $V_{OH} \approx V_{MAX}$
- Trace tangent of transfer function at  $V_M$ 
  - Slope = small signal voltage gain ( $A_v$ ) at  $V_M$
- $V_{IL} \approx$  intersection of tangent with  $V_{OUT} = V_{MAX}$
- $V_{IH} \approx$  intersection of tangent with  $V_{OUT} = V_{MIN}$

# Transient Characteristics

Inverter switching in the time domain:

 

$t_R$   $\equiv$  *rise time* between 10% and 90% of total swing

$t_F$   $\equiv$  *fall time* between 90% and 10% of total swing

$t_{PHL}$   $\equiv$  *propagation delay from high-to-low* between 50% points


$t_{PLH}$   $\equiv$  *propagation delay from low-to-high* between 50% points

**Propagation delay :** 
$$t_P = \frac{1}{2} (t_{PHL} + t_{PLH})$$



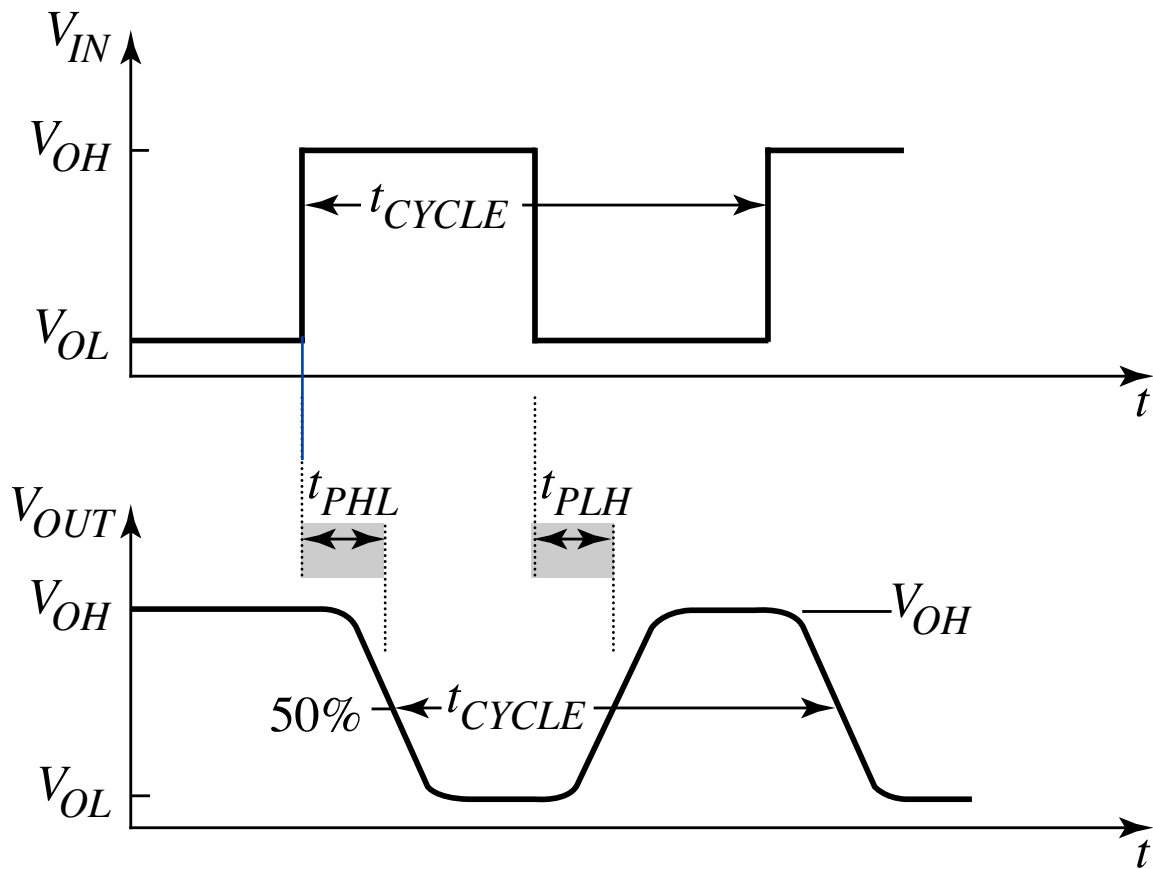
## Simplifications for hand calculations: Propagation delay

- Consider input waveform is an ideal square wave
- Propagation delay times = delay times to 50% point



- SPICE essential for accurate delay analysis
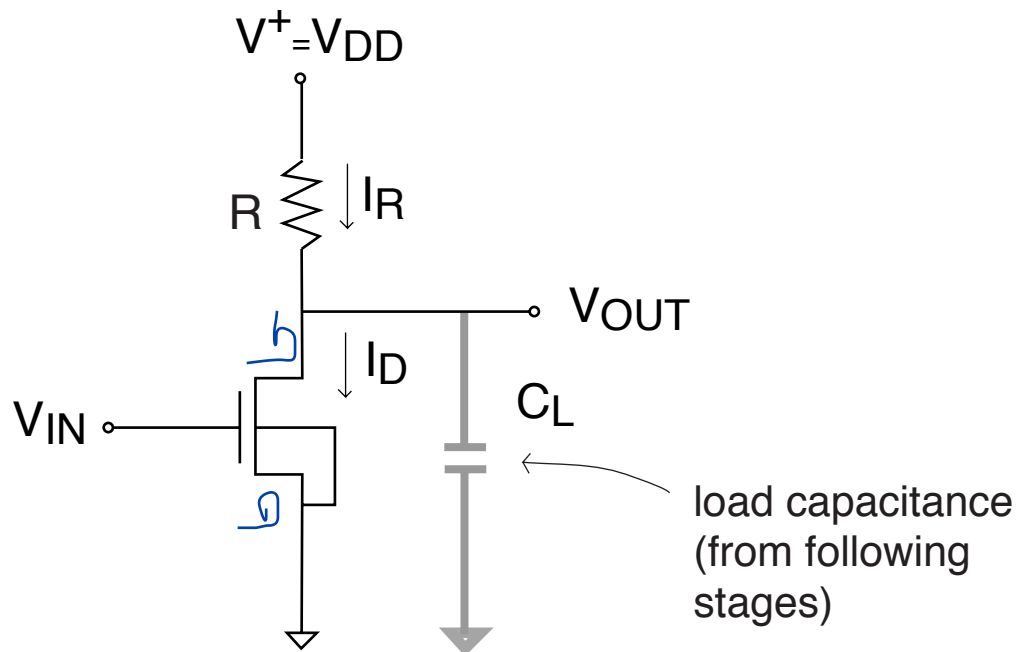
## 2. NMOS inverter with “pull-up” resistor




Essential features:

- $V_{BS} = 0$  (typically not shown)
- $C_L$  summarizes capacitive loading of the following stages (other logic gates, interconnect lines, etc.)

Basic Operation:

 
- If  $V_{IN} < V_T$ , MOSFET is **OFF**
  - $\Rightarrow V_{OUT} = V_{DD}$
- If  $V_{IN} > V_T$ , MOSFET is **ON**
  - $\Rightarrow V_{OUT}$  small
  - Value set by resistor / nMOS divider




Transfer function obtained by solving:

$$I_R = I_D$$


Can solve graphically: I–V characteristics of load:

 

 
Overlap I–V characteristics of resistor pull-up on I–V characteristics of transistor:



Transfer function:

 

## Logic levels:

 

For  $V_{MAX}$ , transistor is cut-off,  $I_D = 0$ :

$$V_{MAX} = V_{DD}$$


For  $V_{MIN}$ , transistor is in linear regime; solve:

$$I_D = \frac{W}{L} \mu_n C_{ox} \left( V_{DD} - \frac{V_{MIN}}{2} - V_T \right) V_{MIN} = I_R = \frac{V_{DD} - V_{MIN}}{R}$$



For  $V_M$ , transistor is in saturation; solve:

$$I_D = \frac{W}{2L} \mu_n C_{ox} (V_M - V_T)^2 = I_R = \frac{V_{DD} - V_M}{R}$$

## Noise Margins:

 

  Small signal equivalent circuit model at  $V_M$   
(transistor in saturation):



$$A_v = \frac{v_{out}}{v_{in}} = -g_m (r_o // R) \approx -g_m R$$

# What did we learn today?

## Summary of Key Concepts

- Logic circuits must exhibit immunity to noise in the input signal
  - *Noise margins*
- Logic circuits must be *regenerative*
  - Able to restore clean logic values even if input is noisy.
- *Propagation delay*: time for logic gate to perform its function.
- Concept of *load line*: graphical technique to visualize transfer characteristics of inverter.
- First-order solution (by hand) of inverter figures-of-merit easy if *regions of operation* of transistor are correctly identified.
- For more accurate solutions, use SPICE (or other CAD tool).