

Lab experiment: Part 1: RC circuits

1. Connect the RC circuit shown in Fig.1. Observe input and output voltage waveforms for $V_{in} = 10V_{pp}$, $50Hz$ sinusoidal signal, $R=1K\Omega$ and $C=1\mu F$.

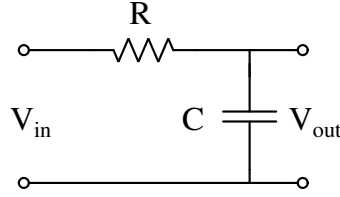


Figure 1: RC circuit-1

2. Vary the frequency of V_{in} from $50Hz$ to $50kHz$ with appropriate steps and measure V_{out} and phase difference between V_{out} and V_{in} keeping the magnitude of V_{in} constant.
3. Plot the frequency response (log magnitude and phase w.r.t. log frequency).
4. Comment on these plots.
5. Now apply a square wave input of $10V_{PP}$ and $100Hz$ that varies from $-5V$ to $+5V$.
6. Observe the input and output waveforms for $100Hz$, $500Hz$, $1kHz$, $5kHz$, $10kHz$, $50kHz$, and $100kHz$.
7. Explain your observations.
8. Now add a DC offset of $+5V$ so that V_{in} varies from 0 to $10V$.
9. Observe the input and output waveforms for $100Hz$, $1kHz$, $10kHz$, and $100kHz$.
10. Change the duty cycle of the input voltage to 10% and observe the input output waveforms.
11. Modify the circuit as shown in Fig.2. and repeat the steps 1 to 10 for this circuit.
12. Explain your observations.

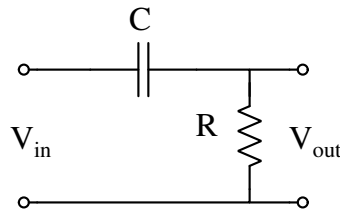


Figure 2: RC circuit-2